

(T)EE2026

Digital Fundamentals

Gate-level Design & Minimization

Prof. Massimo Alioto

Dept of Electrical and Computer Engineering

Email: *massimo.alioto@nus.edu.sg*

Outline

- Gate-level logic design
- Karnaugh map
- Boolean function simplification using K-Map
- Gate-level implementation

Gate-Level Logic Design

- Step 1 (simplify the Boolean function)
 - Simplify the Boolean function to be implemented
 - Methods of simplification
 - Postulates and theorem
 - Karnaugh Map
- Step 2
 - Implement the simplified Boolean function using logic gates
 - Minimize the gate counts
- Why minimization?
 - Cost, power, performance, size, reliability, ...

Karnaugh Map (K-Map)

- K-map is a diagram that consists of a number of squares
- Each square represent one minterm (or maxterm) of a Boolean function
- The Boolean function (SOP) can be expressed as a sum of minterms in the map
- n -variables Boolean function has maximum 2^n minterms

Two-variable K-map:
(maximum 4 minterms)

$$\begin{aligned} m_0 &\rightarrow 00 \rightarrow \bar{A}\bar{B} \\ m_1 &\rightarrow 01 \rightarrow \bar{A}B \\ m_2 &\rightarrow 10 \rightarrow A\bar{B} \\ m_3 &\rightarrow 11 \rightarrow AB \end{aligned}$$

		B	
		\bar{B}	B
A	\bar{A}	$\bar{A}\bar{B}$	$\bar{A}B$
	A	$A\bar{B}$	AB

squares



		B	
		0	1
A	0	00	01
	1	10	11




		B	
		0	1
A	0	m_0	m_1
	1	m_2	m_3



“0” → Literal **with** overbar
“1” → Literal **without** overbar

Truth table \rightarrow K-map

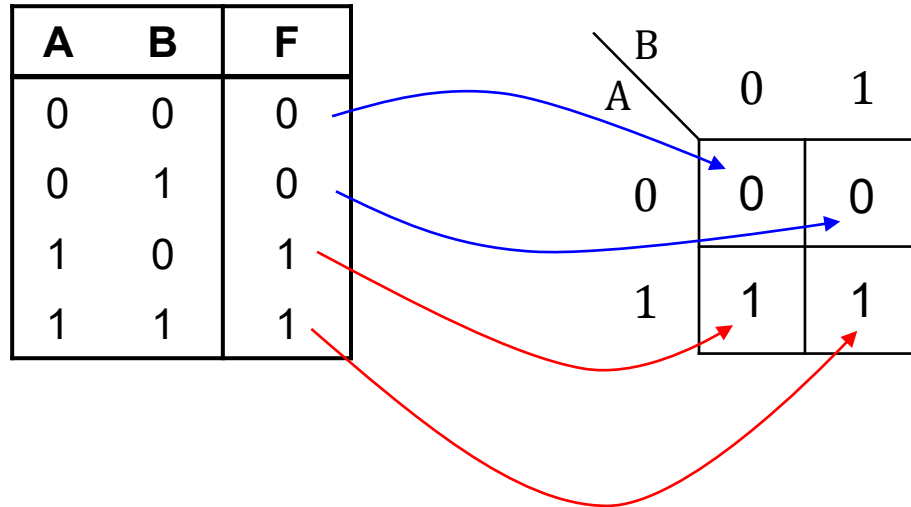


- K – map is a two-dimensional truth table
- Each row of in truth table corresponds to one square in the k-map
- If the term in a row is a *minterm* of the function ($F=1$), place a “1” in the corresponding square of the K-map, otherwise (*maxterm*), place a “0”.

Three- and four-Variable K-Maps


***Note that any two adjacent squares differ by only one literal**

Three-variable K-map

BC A		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
A		$A\bar{B}\bar{C}$	$A\bar{B}C$	ABC	$AB\bar{C}$




BC A		00	01	11	10
		000	001	011	010
1		100	101	111	110



BC A		00	01	11	10
		m_0	m_1	m_3	m_2
1		m_4	m_5	m_7	m_6

Four-variable K-map

CD AB		00	01	11	10
		0000	0001	0011	0010
01		0100	0101	0111	0110
11		1100	1101	1111	1110
10		1000	1001	1011	1010



CD AB		00	01	11	10
		m_0	m_1	m_3	m_2
01		m_4	m_5	m_7	m_6
11		m_{12}	m_{13}	m_{15}	m_{14}
10		m_8	m_9	m_{11}	m_{10}

Boolean function in K-map

Represent the following function on K-map:

$$F = \overline{A}B + AB + A\overline{B}$$

A \ B	0	1
	0	1
0	0	1
1	1	1

Place a “1” in the square that represents a minterm in the given function

Write the Boolean expression for the function in K-map:

A \ B	0	1
	0	1
0	0	1
1	1	0

$$F = ?$$

in SOP: write F as sum of the minterms (squares with “1”)

$$F = \overline{A}B + A\overline{B}$$

Boolean function in K-map (cont.)

Represent the following function on K-map:

$$F = \bar{A}BC + AB\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

BC A		BC			
		00	01	11	10
A	0	1	1	1	0
	1	0	0	0	1

$$F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + AB\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$$

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	0	0
	11	1	0	0	0
	10	0	1	1	1

Write the Boolean expression for the function in K-map:

BC A		BC			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	0	0

$$F = ? \quad F = \bar{A} \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

CD AB		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	0	0	0	1
	11	0	1	0	0
	10	0	0	0	0

$$F = ? \quad F = \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + AB\bar{C}\bar{D}$$

Boolean function in K-map (cont.)

What about Boolean function in **non-canonical form**?

Example-1:

$$F = \overline{A}B + AB\overline{C} + \overline{A}\overline{B}C$$

$$\overline{A}B = \overline{A}B(C + \overline{C}) = \overline{A}BC + \overline{A}B\overline{C}$$

BC					
A \		00	01	11	10
0	0	0	1	1	1
1	0	0	0	0	1

Or $\overline{A}B \rightarrow 01, C = 0 \text{ or } 1$

or just fill the truth table and derive the K-map

Example-2:


$$F = A + \overline{A}\overline{B}CD + B\overline{C}\overline{D}$$

CD		00	01	11	10
AB \					
00				1	
01		1			
11		1	1	1	1
10		1	1	1	1

Boolean function simplification using K-map

Boolean function (SOP) simplification using K-map

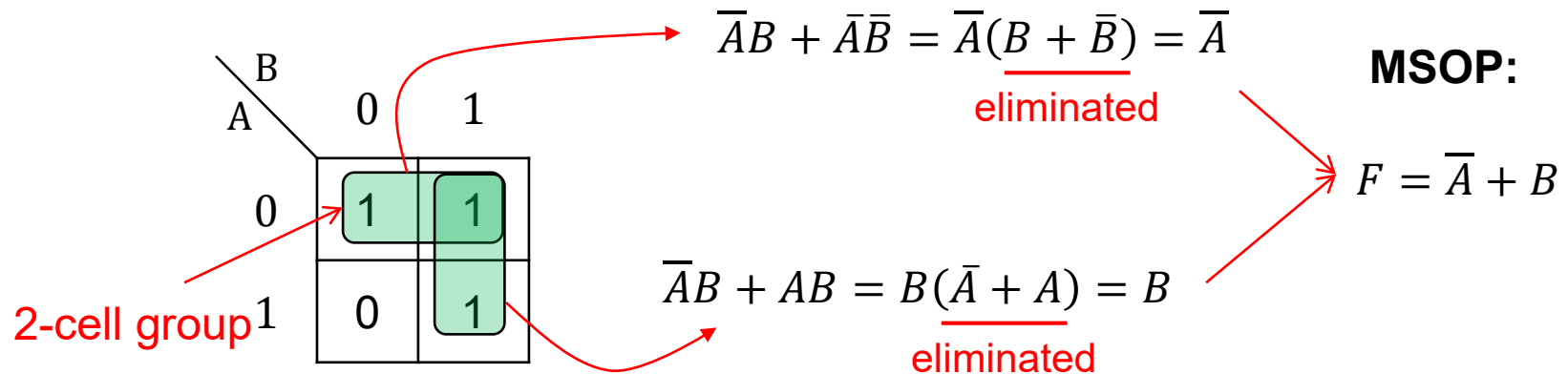Simplify: $F = \bar{A}B + AB + \bar{A}\bar{B}$



Alternatively,

$$\begin{aligned} F &= \bar{A}B + AB + \bar{A}\bar{B} \\ &= \bar{A} + AB \\ &= \bar{A} + B \end{aligned}$$

*The variable that changes value in the group is eliminated, or the variable that doesn't change value in the group remains

Boolean function (SOP) simplification using K-Map (cont.)

Three-variables:

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \underline{\bar{A}B\bar{C} + ABC}$$

$$F = \bar{A} + B\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC &\rightarrow \bar{A}\bar{B}(\bar{C} + C) + \bar{A}B(C + \bar{C}) \\ &\rightarrow \bar{A}\bar{B} + \bar{A}B \rightarrow \bar{A}(\bar{B} + B) \rightarrow \bar{A} \end{aligned}$$

$$\bar{A}B\bar{C} + ABC \rightarrow (\bar{A} + A)B\bar{C} \rightarrow B\bar{C}$$

$$F = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \underline{\bar{A}\bar{B}C + \bar{A}BC}$$

$$F = \bar{B} + \bar{A}\bar{C}$$

$$\begin{aligned} \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C &\rightarrow \bar{A}\bar{B}(C + \bar{C}) + \bar{A}\bar{B}(\bar{C} + C) \\ &\rightarrow (\bar{A} + A)\bar{B} \rightarrow \bar{B} \end{aligned}$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}BC \rightarrow \bar{A}(\bar{B} + B)\bar{C} \rightarrow \bar{A}\bar{C}$$

\bar{A} (B and C eliminated)

BC \ A	00	01	11	10
0	1	1	1	1
1	0	0	0	1

$B\bar{C}$ (A eliminated)

\bar{B} (A and C eliminated)

BC \ A	00	01	11	10
0	1	1	0	1
1	1	1	0	0

$\bar{A}\bar{C}$ (B is eliminated)

Group the adjacent cells where only one variable changes value so that it can be eliminated


Minimization (SOP) using K-Map (cont.)

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} \\ + AB\bar{C}\bar{D} + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$




$$F = \bar{B}\bar{C}\bar{D} + BD + CD$$

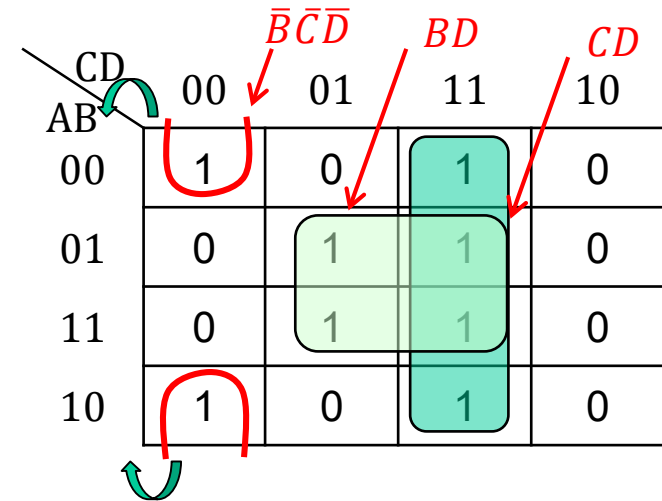

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} \\ + AB\bar{C}\bar{D} + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$



$$F = \bar{B}\bar{D} + BD$$

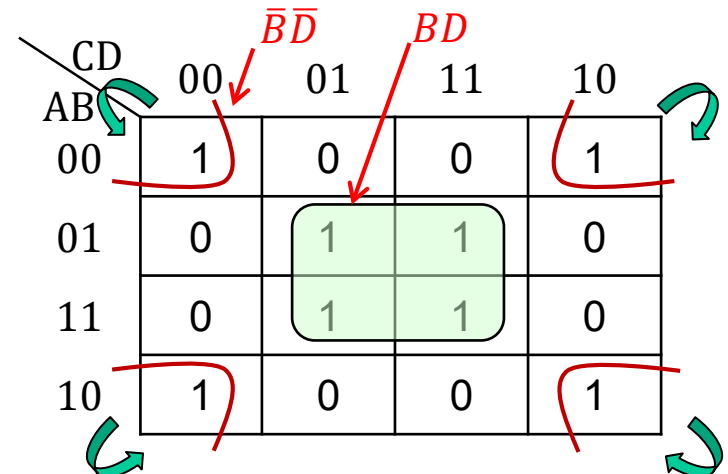

Minimization (SOP) using K-Map (cont.)

Four-variables:

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ + \bar{A}BCD + \bar{A}BC\bar{D} + AB\bar{C}\bar{D} + AB\bar{C}D \\ + ABCD + ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

↓

$$F = B + \bar{D}$$

A 4x4 Karnaugh Map for four variables A, B, C, and D. The vertical axis is labeled AB with values 00, 01, 11, 10. The horizontal axis is labeled CD with values 00, 01, 11, 10. The map contains 1s in the first column (CD=00), the last column (CD=10), and the middle two rows (AB=01 and AB=11). A red line groups the first and last columns, labeled \bar{D} . A green line groups the middle two rows, labeled B . Green curved arrows at the bottom indicate the wrap-around between the first and last columns.

CD \ AB	00	01	11	10
00	1	0	0	1
01	1	1	1	1
11	1	1	1	1
10	1	0	0	1

Grouping rules:

- Group the squares that only contains “1”
- Groups must be either horizontal or vertical (diagonal is invalid)
- Group size is always 2^n , that is, 2, 4, 8, ...
- Group should be as large as possible (contains as many as squares with “1” as possible)
- Each square with “1” must be part of a group if possible
- Simplified term retains those variables that don’t change value
- Variables that change value in the group are eliminated

Invalid groupings

CD \ AB	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	0	1	0

Squares in the group are not in power of two

Two variable change value

CD \ AB	00	01	11	10
00	0	1	0	1
01	1	0	0	1
11	0	1	1	1
10	0	1	1	1

not horizontal or vertical

Don't-care condition

- So far we assume that all combination of the input variables of a Boolean function are valid (for example, 3-variable Boolean function has 8 different input combinations that makes the function equal to 0 or 1)
- There are applications in which some variable combinations never appear.
- One of such examples is the BCD code
 - 4-bit BCD code can have 16 values
 - However, 1010 – 1111 are never used, or $A\bar{B}C\bar{D}$, $A\bar{B}CD$, $AB\bar{C}\bar{D}$, $AB\bar{C}D$, $ABC\bar{D}$, and $ABCD$ never occur
- These conditions are called **don't-care conditions**.
- Don't-care condition is marked with “X” in K-map
- For minimization, X can take either “1” or “0”.

Binary-Coded Decimal (BCD)

Decimal Symbol	BCD Digit
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Minimization with don't-care conditions

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}BCD + AB\bar{C}D + ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$$



$$F = B + \bar{D}$$

*Treat X = 1 and group the squares as usual

CD \ AB	00	01	11	10
00	1	0	0	1
01	X	1	X	1
11	X	1	X	1
10	1	0	0	1

Assume X = 1

Minimization (POS) using K-Map (cont.)

Boolean function in POS: maxterm-input correspondence: complement literals if 1

$$F = (A + B + C + \bar{D})(A + B + \bar{C} + D) \\ (A + \bar{B} + C + D)(A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D) \\ (\bar{A} + B + C + \bar{D})(\bar{A} + B + \bar{C} + D)$$



$$F = (B + C + \bar{D}) \cdot (\bar{C} + D) \cdot (\bar{B} + D)$$

CD \ AB	00	01	11	10	
00	1	0	1	0	$\bar{C} + D$
01	0	1	1	0	
11	0	1	1	0	$\bar{B} + D$
10	1	0	1	0	

$$(A + B + C + \bar{D}) \cdot (\bar{A} + B + C + \bar{D}) \\ = A\bar{A} + A \cdot (B + C + \bar{D}) + (B + C + \bar{D}) \cdot \bar{A} \\ + (B + C + \bar{D}) \cdot (B + C + \bar{D}) \\ = (B + C + \bar{D})$$

POS simplification using K-map:

- Group the squares that only contains "0"
- Form an **OR** term (sum) for each group, instead of a product
- Value "1", instead of "0", represent complement of the variable
- Follow similar grouping rules for SOP
- Either SOP or POS can be used to implement the Boolean function, depending on which gives more efficient implementation.

summarizing: proceed as SOP, but group 0's instead of 1's (square = maxterm)
+ complement the values in row-col. to find maxterm associated with square

Minimal SOP (MSOP)

Some terminology


Implicant, prime implicant and essential implicant

- **Implicant of a Boolean function**


- Each product term in SOP is called an implicant of the function

Example-1:

Implicants

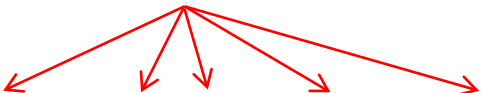
$$F(a, b, c) = ab + \bar{a}\bar{b}c + \bar{a}bc + \bar{c} + abc$$

Literals

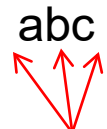

Example-2:

		BC			
		00	01	11	10
A	0	1	1	0	0
	1	1	1	1	0

How many implicants?

Minimal SOP (MSOP) – Prime implicant

- **Prime implicant**

- An implicant that cannot be combined with another term to eliminate a variable

Example-1:

$$F = AB + ABC + BC$$

Non-prime implicant (already contained in AB or BC)
←
Prime implicants

Example-2:

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$\bar{A}\bar{B}\bar{D}$ (points to cell 00,01)
 $\bar{A}\bar{B}D$ (points to cell 00,11)
 $\bar{A}B\bar{D}$ (points to cell 01,01)
 $\bar{A}BD$ (points to cell 01,11)
 $\bar{A}D$ (points to column 01)
 $\bar{A}B$ (points to row 01)

$\bar{A}\bar{B}D$, $\bar{A}B\bar{D}$ and $\bar{A}BD$

are implicants, but not prime implicants
(can be grouped into larger groups of 4)

$\bar{A}D$ and $\bar{A}B$ are essential prime implicants

graphically: prime implicant grouping
cannot be expanded further (but could
overlap with other prime implicants)

Identifying prime implicants

- A single “1” on a K-map is a prime implicant if is not adjacent to any other 1 of the function.
- Two adjacent “1”s represent a prime implicant, provided that they are not within a rectangle of 4 or more squares containing “1”s.
- Four “1”s (that are an implicant) are a prime implicant if they are not within a group of 8 squares containing “1”s

Basically, implicant is prime if it cannot be enclosed within a larger square/rectangle (as per K-map rules)

Essential prime implicant

- **Essential prime implicant**

- A prime implicant that is not included in any other prime implicant

		x_1x_2			
		00	01	11	10
x_3	0	1	1	0	0
	1	1	1	1	0

\bar{x}_1 x_2x_3

Both \bar{x}_1 and x_2x_3 are essential prime implicants

Prime implicant (not an essential prime implicant, already covered by the other two implicants)

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01	1	1	1	1
	11	1	0	0	1
	10	0	0	0	0

Essential prime implicants: $\bar{A}D$ and $B\bar{D}$

graphically: essential prime implicant is needed to cover some 1 (i.e., it does not completely overlap with other implicants)

Minimal SOP Expression (MSOP)

- What is MSOP?
 - It contains a minimal number of literals and terms
 - All essential prime implicants must be included in MSOP
- Determination of MSOP
 - Finding all of the *prime implicants* of the function
 - Select essential prime implicants (those with “1”s that have only been grouped once)
 - Finding a minimal subset of these prime implicants that covers all of the *minterms* of the function

Obtaining MSOP - examples

Example – 1:

CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

Essential
Prime implicant



Select the essential prime implicant
with minimum set of prime implicants

All implicants including
one essential prime implicant

CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	1	1	1	1
10	0	0	0	0

Obtaining MSOP - examples (cont.)

Example – 2:

CD \ AB	00	01	11	10
00	0	0	1	0
01	1	0	1	1
11	1	1	1	1
10	0	0	1	0

Essential
Prime implicant




Select the essential prime implicant
with minimum set of prime implicants

All implicants including
two essential prime implicant

CD \ AB	00	01	11	10
00	0	0	1	0
01	1	0	1	1
11	1	1	1	1
10	0	0	1	0


Obtaining MSOP - examples (cont.)

Example – 3:

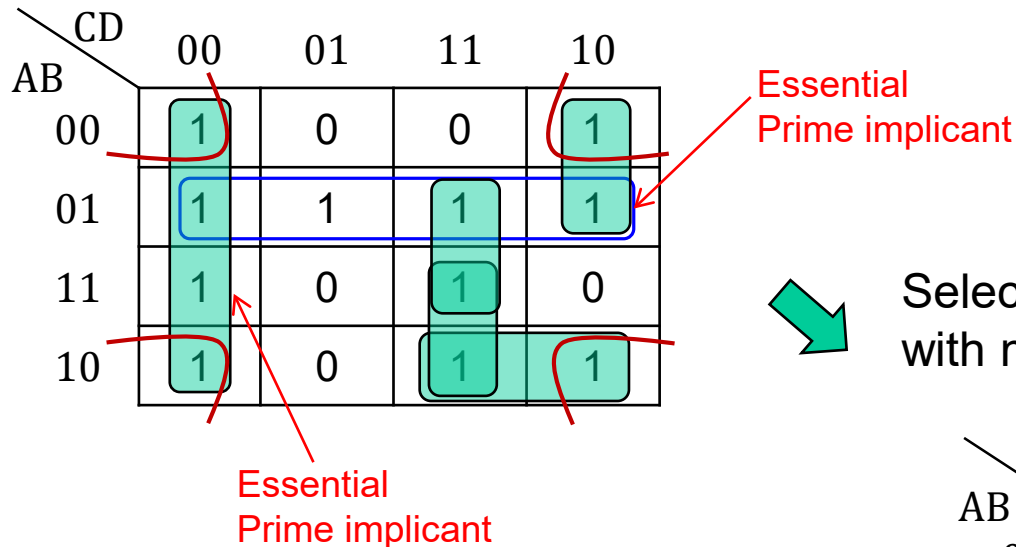

All implicants including
two essential prime implicant

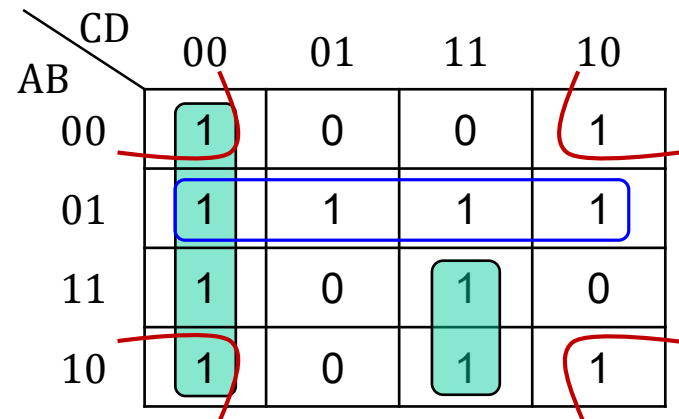Select the essential prime implicant
with minimum set of prime implicants




Gate-level implementation





- NAND only implementation
- NOR only implementation

NAND only implementation

Logic operation:


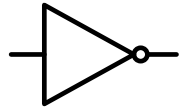


NAND implementation:

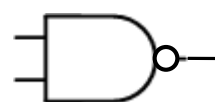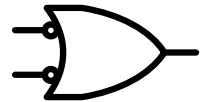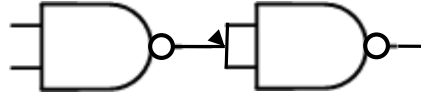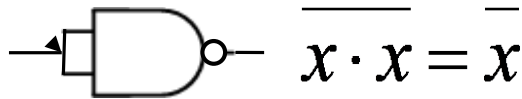


$$F = A\bar{B} + \bar{C}D$$

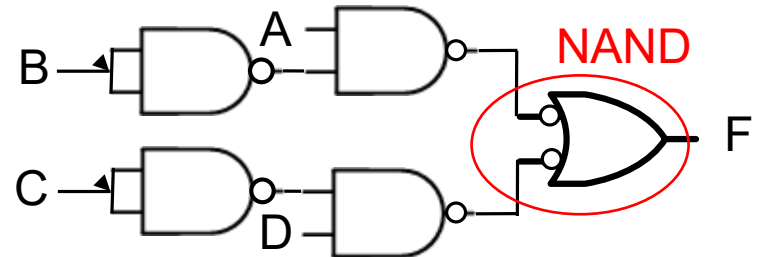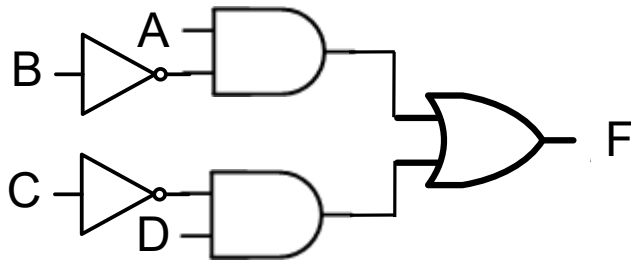- Replace the OR gate with NAND gate and balance the bubble
- Replace the inverter with NAND gate





NAND only implementation – cont.

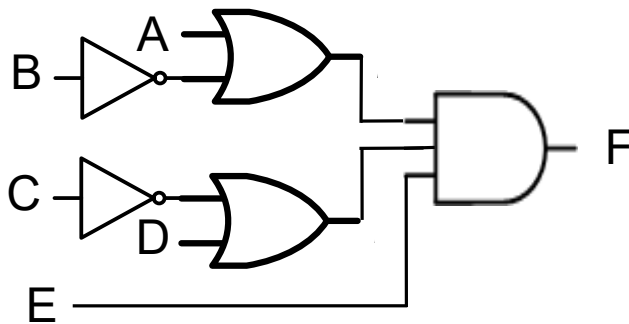
$$F = (A + \bar{B}) \cdot (\bar{C} + D) \cdot E$$



Add double bubble → Do nothing

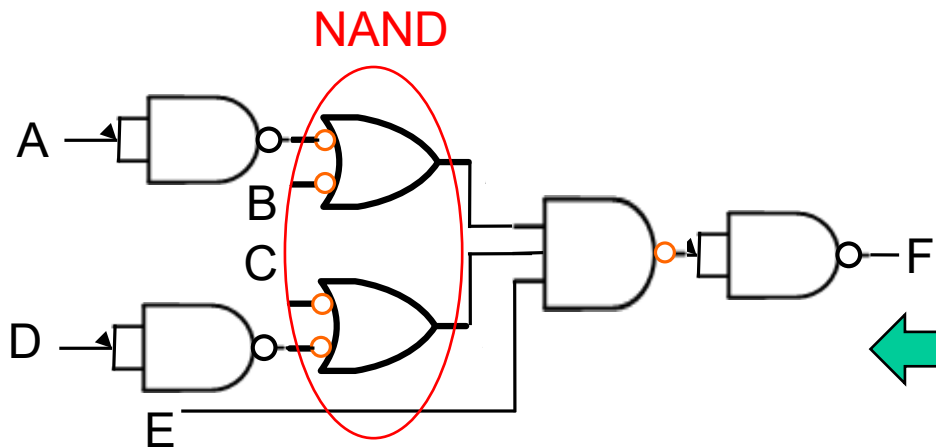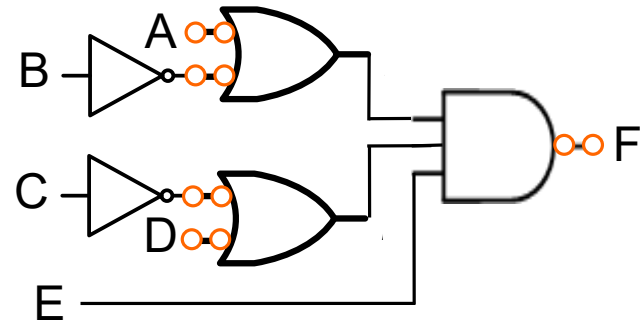


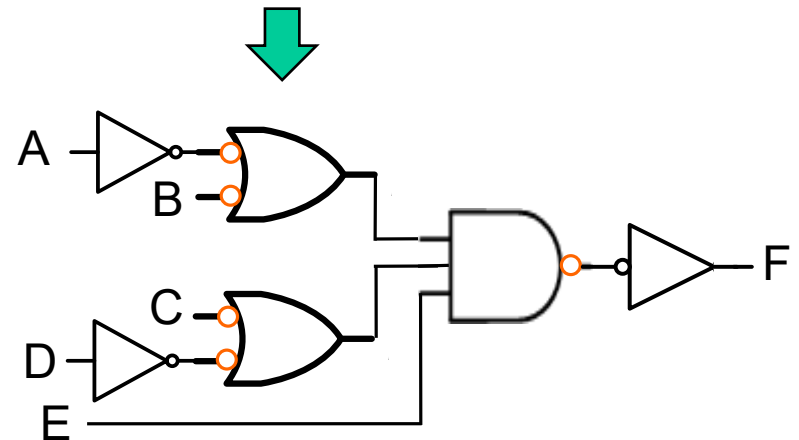Replace inverters with NAND gates,
push bubbles



NOR only implementation



Logic operation:

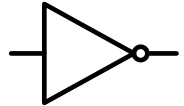

NOR implementation:






$$\overline{x + x} = \bar{x}$$

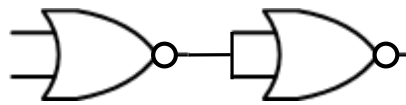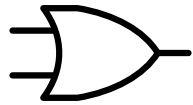

$$F = (A + \bar{B}) \cdot (\bar{C} + D) \cdot E$$


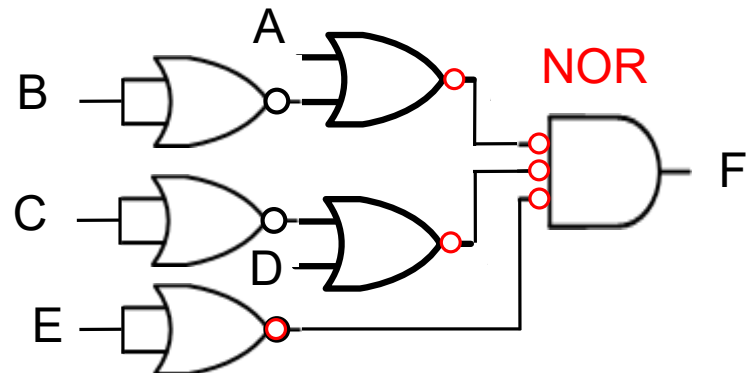
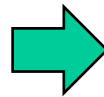
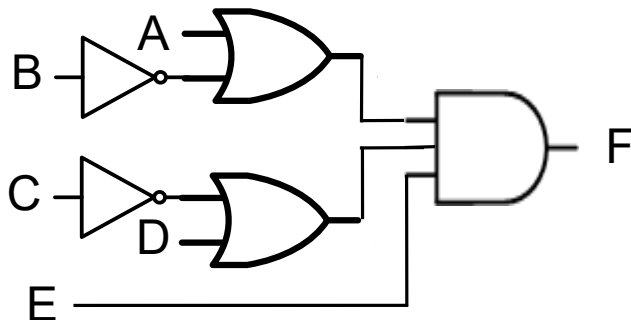
- Replace the AND gate with NOR gate and balance the bubble
- Replace the inverter with NOR gate



NOR only implementation – cont.

$$F = A\bar{B} + \bar{C}D$$



Add double bubble → Do nothing

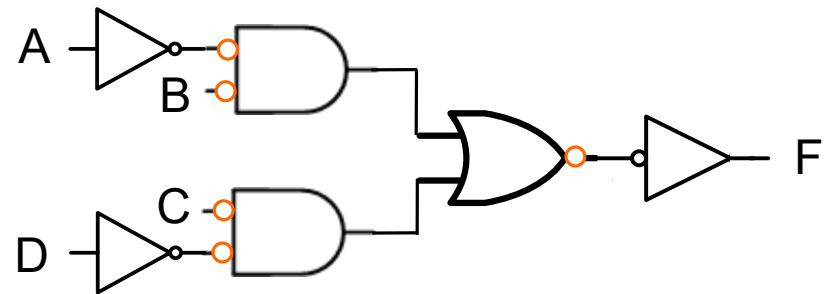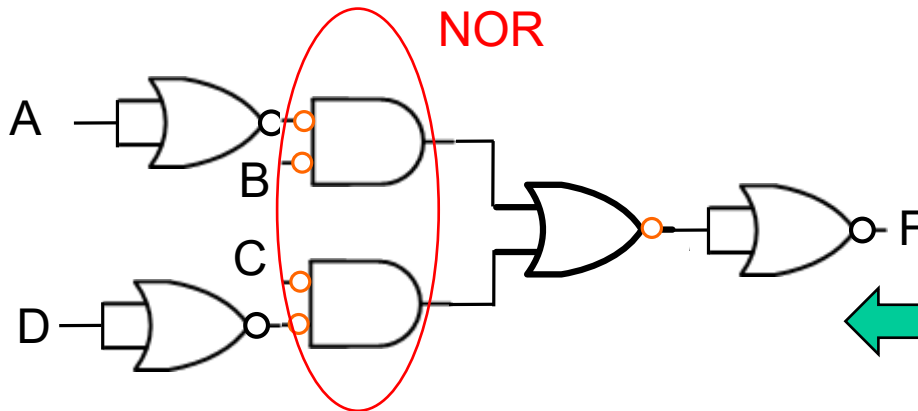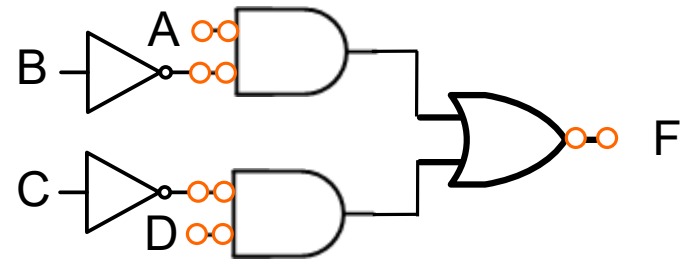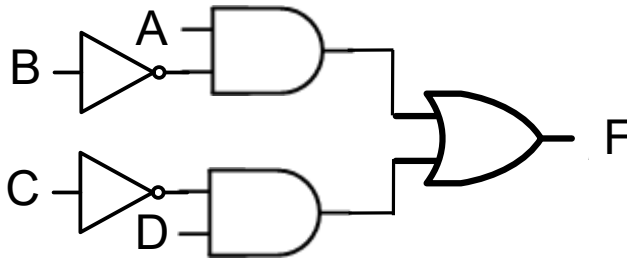



Replace inverters with NOR gates,
push bubbles

NAND only Implementation with Mixed Logic
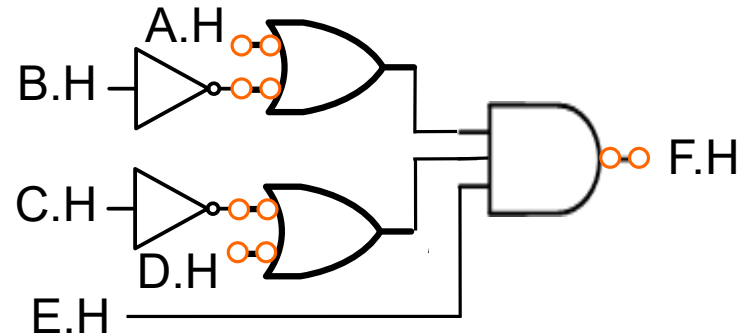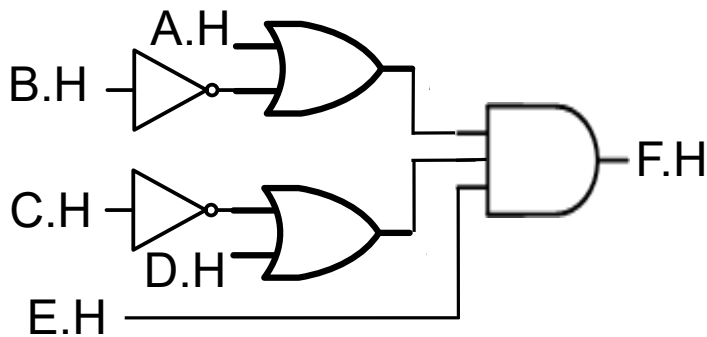
$$F = (A + \bar{B}) \cdot (\bar{C} + D) \cdot E \quad (\text{where } C, D \text{ and } F \text{ are active low})$$




active low inputs

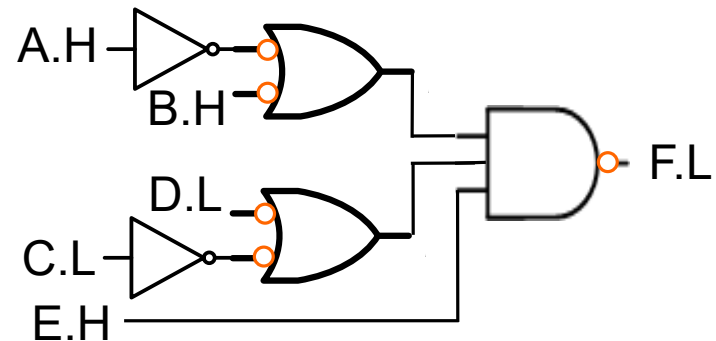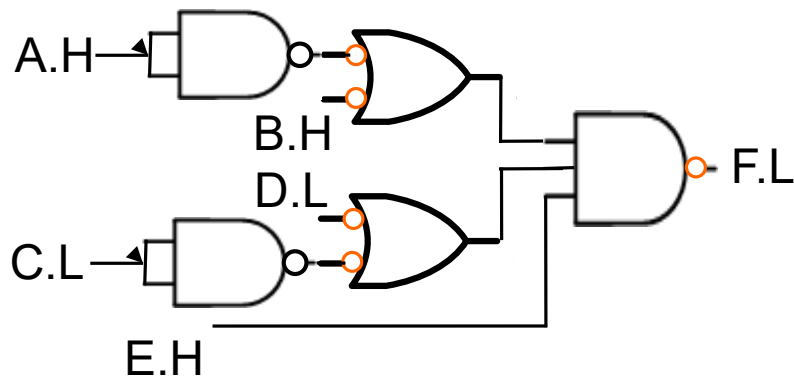

NAND only implementation with Mixed Logic – cont.

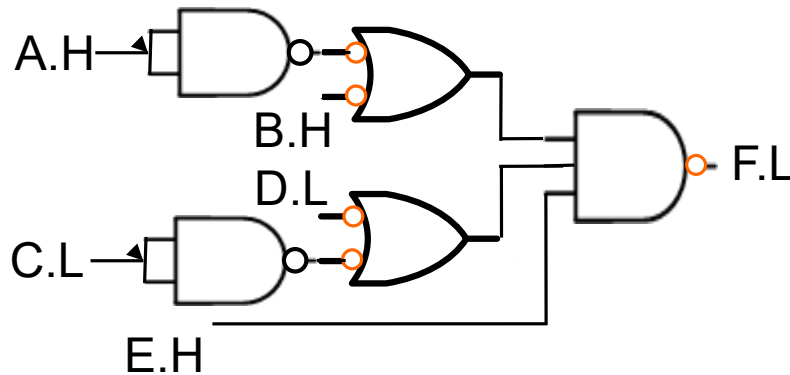Write the Boolean function implemented by the circuit below and express F in positive logic.



Summary

- Karnaugh map
- Boolean function simplification using K-map
 - SOP simplification
 - POS simplification
 - Don't-care condition
 - Minimal SOP (MSOP) and POS (MPOS)
- Gate-level implementation
 - NAND only
 - NOR only

Suggestions for Self-Improvement

- In addition to the tutorials, you may want to practice with questions in chapter 2 of the textbook (see IVLE Workbin)
 - QUESTIONS (highlighted in yellow):
harris_exercises_chapter2odd.pdf
 - ANSWERS: harris_solutions_chapter2odd.pdf

