


## ELEC1100: KCL & KVL Exercises

### Note:

- This is an additional exercises document for your own practice. Solution will be released on Mar 27 (Fri).
- **THIS IS NOT YOUR LAB HOMEWORK.**
- Lab homework starts on March 30 (Mon), go to your Canvas lab page (LA1/LA2/LA3) to download Homework Questions.
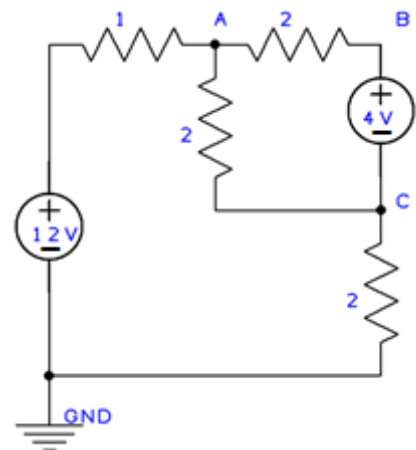
### Exercise 1

Use **KVL** to find the voltages at node A and node B in Figure 1.



### Exercise 2

Use **KCL** to find the voltages at node D and node E in Figure 2.


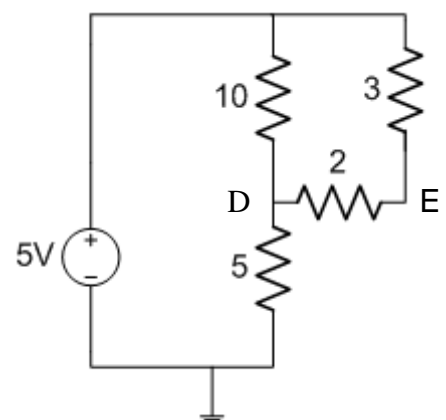


Figure 2

### Exercise 3

Figure 3 shows a Zener diode circuit where the breakdown voltage of the Zener diode is 5V. It is known that when  $V_{in} \geq 7V$ , the Zener diode can be regarded as a small resistor  $R_z = 6\ \Omega$  connected in series with a 5V voltage source as shown in the right part of Figure 3. That resistance  $R_s$  is dependent on the load  $R$  with  $R_s = 0.4R$ .

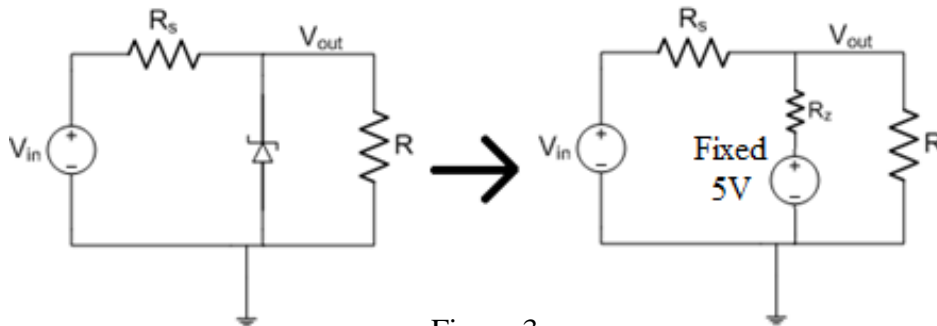

Show that when  $V_{in} \geq 7V$ ,  $V_{out}$  is given by:

$$V_{out} = \frac{15V_{in} + 5R}{R + 21}$$

(Hint: You may consider using KCL)

#### Exercise 4

- Use KCL to find the current  $I_1$  in Fig. 4.1.
- If the resistor network in Fig. 4.1 is to be replaced by a single equivalent resistor, as in Fig. 4.2, what is the resistance required?
- Use KVL to find the current  $I_2$  in Fig. 4.3.
- Based on the result in c), and by following the same procedure as that for b), find the equivalent resistance between A and B in Fig. 4.3.

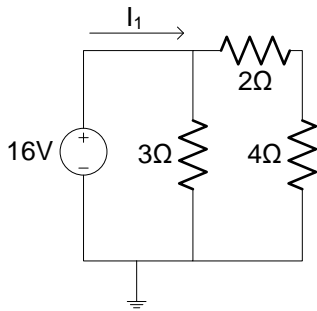


Fig. 4.1

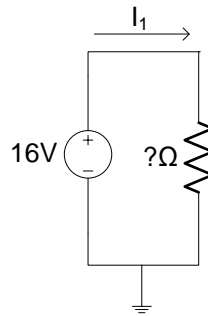


Fig. 4.2

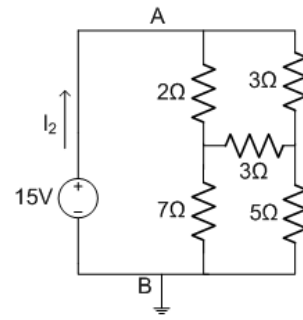


Fig. 4.3