



ELEC1100: Introduction to Electro-Robot Design

Lecture 17: Online Exam Review



ONLINE EXAM

- ❖ **Online Exam (15%):** May 02 (Sat), 10:00am-12:00noon
Similar to examples in Lecture/Tutorial notes. Mainly tests on key concepts.
- ❖ You will need to take the exam on Canvas Page: **ELEC1100 Online Exam**

- ❖ **Coverage:** Lectures 02-12
- ❖ Supporting document on your Canvas Lecture (L1/L2/L3) page:
 - Online Exam Arrangement
 - Additional Exercises





POLICIES

- ❖ This is a **closed-book** and **closed-note** exam.
- ❖ **Canvas exam page** should be the **only window/tab** on your computer screen.
- ❖ Talking or discussion with others is NOT allowed in the exam.
- ❖ **No headphones allowed.**
- ❖ **No Calculators allowed.**
- ❖ **Scratch Paper (A4 size blank sheets) is allowed.** But your scratch paper will NOT be graded.






EXAM DEVICES

- ❖ Get the following electronic devices ready before the exam starts
 - **1 mobile phone**: to join Zoom Meeting and enable exam invigilating
 - **1 computer**: to log in Canvas Exam page and answer questions

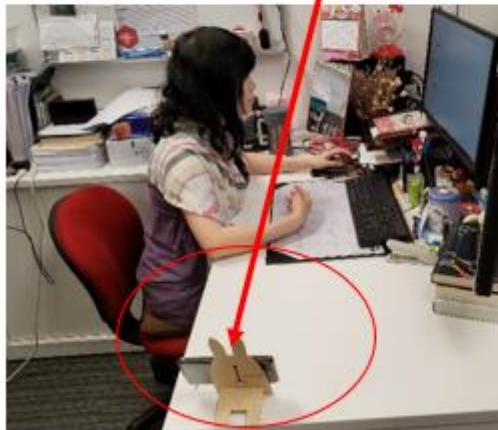Now, place your mobile phone camera to let us see your face/head and the canvas page on the screen. The exam invigilator and you will see this:



Keep your mobile speaker on for receiving instructions from your TA





EXAM SCHEDULE

- ❖ 10:00: **Zoom meeting starts**, you should join the meeting before 10:10am.
- ❖ 10:10-10:30 **Preparation: You will be sent to breakout rooms**, where your TA will do an attendance check and camera check with you. ****Being uncooperative (camera off, or camera placement not as required) will be immediately removed from the Canvas exam page.**
- ❖ 10:30-11:00 **Session 1**. Your TA will announce the **access code** (to open up Session 1 Questions) at 10:30am.
- ❖ 11:00-11:10 [Toilet Break]
- ❖ 11:10-12:00 **Session 2**. Your TA will announce the **access code** (to open up Session 2 Questions) at 11:10am.
- ❖ 12:00 [End of the Exam]





EXAM SESSIONS

❖ 10:30 - 11:00: Session 1

[10 questions, 50 points]

- Multiple Choice Single Answer
- Multiple Choice Multiple Answers

❖ 11:00 - 11:10: Toilet Break

❖ 11:10 - 12:00 Session 2

[2 questions, 50 points]

- Long Questions: show your calculation steps

❖ 12:00: End of the Exam





NOTES

- ❖ It's your responsibility to try to secure a **reliable internet connection** and get your electronic devices (**1 mobile phone + 1 computer**) ready before the exam starts.
- ❖ During the exam we will monitor you through Zoom. **Misconduct will result in a zero mark.**
- ❖ Any attempt to exam questions without attending at ZOOM meeting or during camera-off period will result in a zero mark.

formulae will be given

**Timer Equations
for NE555**

$$\text{Clock High Time} = 0.7(R_A + R_B)C_1$$

$$\text{Clock Low Time} = 0.7R_B C_1$$

$$\text{Period} = 0.7(R_A + 2R_B)C_1$$





EXAM REHEARSAL

- ❖ **Exam Rehearsal: Apr 25 (Sat), 10:00am-11:30am**
- ❖ Through Canvas Page: **ELEC1100 Online Exam**
 - The rehearsal is for you to test all the procedure, your hardware, your software and your internet connection.
 - Your answers to the rehearsal questions will not be graded.





REHEARSAL SCHEDULE

- ❖ 10:00: **Rehearsal Meeting starts**, join the meeting before 10:10am.
- ❖ 10:10-10:30 **Into breakout rooms**, where your TA will do an attendance check and camera check with you.
- ❖ 10:30-10:36 **Session 1**. Your TA will announce the **access code** at 10:30am.
(1 multiple choice single answer + 1 multiple choice multiple answers)
- ❖ 10:36-10:40 Toilet Break
- ❖ 10:40-11:30 **Session 2**. Your TA will announce the **access code** at 10:40am
(2 long questions)

Note: You may submit and leave the rehearsal early after session 2 starts at 10:40am. However, if we don't see you at 10:00-10:40am during the normal procedure, we will assume that you will not take the online exam on May 02.





PAST PAPER: DIODE AND REGULATOR

❖ Diode and Regulator:


In the voltage regulator shown below, the Zener diode has a breakdown voltage of $V_{bd} = -6.8V$.

➤ What is the mistake in the circuit?

Zener diode is not reversely connected.

➤ Supposed the mistake is fixed, determine the minimum V_{in} that the Zener diode regulates the voltage.
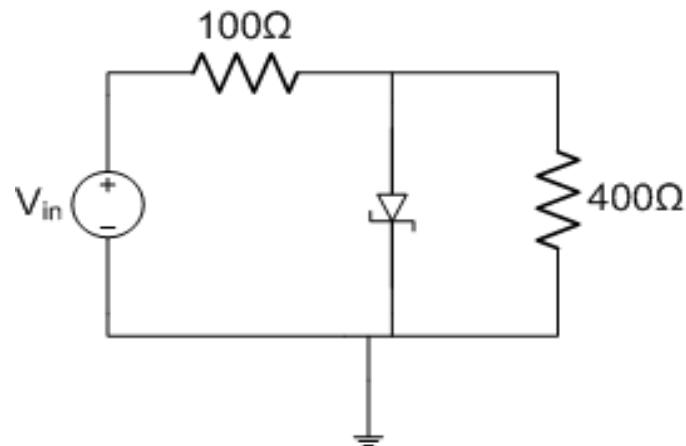
$$V_{in} \times \frac{400}{100 + 400} = 6.8$$
$$V_{in} = 8.5V$$






PAST PAPER: KCL & KVL

❖ KCL and KVL:

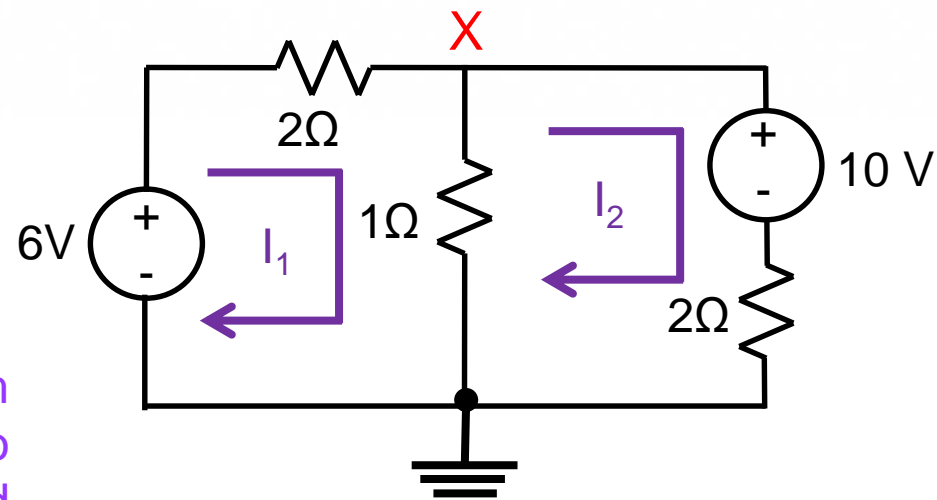- (a) Use KVL to write the voltage equation in each loop in terms of loop current I_1 and I_2 .
- (b) Based on the equations you got from part (a), solve the loop currents to determine the values of I_1 and I_2 , and find the value of voltage X



$$\text{Loop1: } 6 - 2I_1 - 1(I_1 - I_2) = 0$$

$$\text{Loop2: } 1(I_1 - I_2) - 10 - 2I_2 = 0$$



$$3I_1 - I_2 = 6$$

$$I_1 - 3I_2 = 10$$



$$I_1 = 1\text{A}$$

$$I_2 = -3\text{A}$$

$$X = 1(I_1 - I_2) = 4\text{V}$$






PAST PAPER: PWM CONTROL [1]

❖ PWM:

To design a PWM signal of frequency 10kHz and high time 81.25 μ s to drive a DC motor:

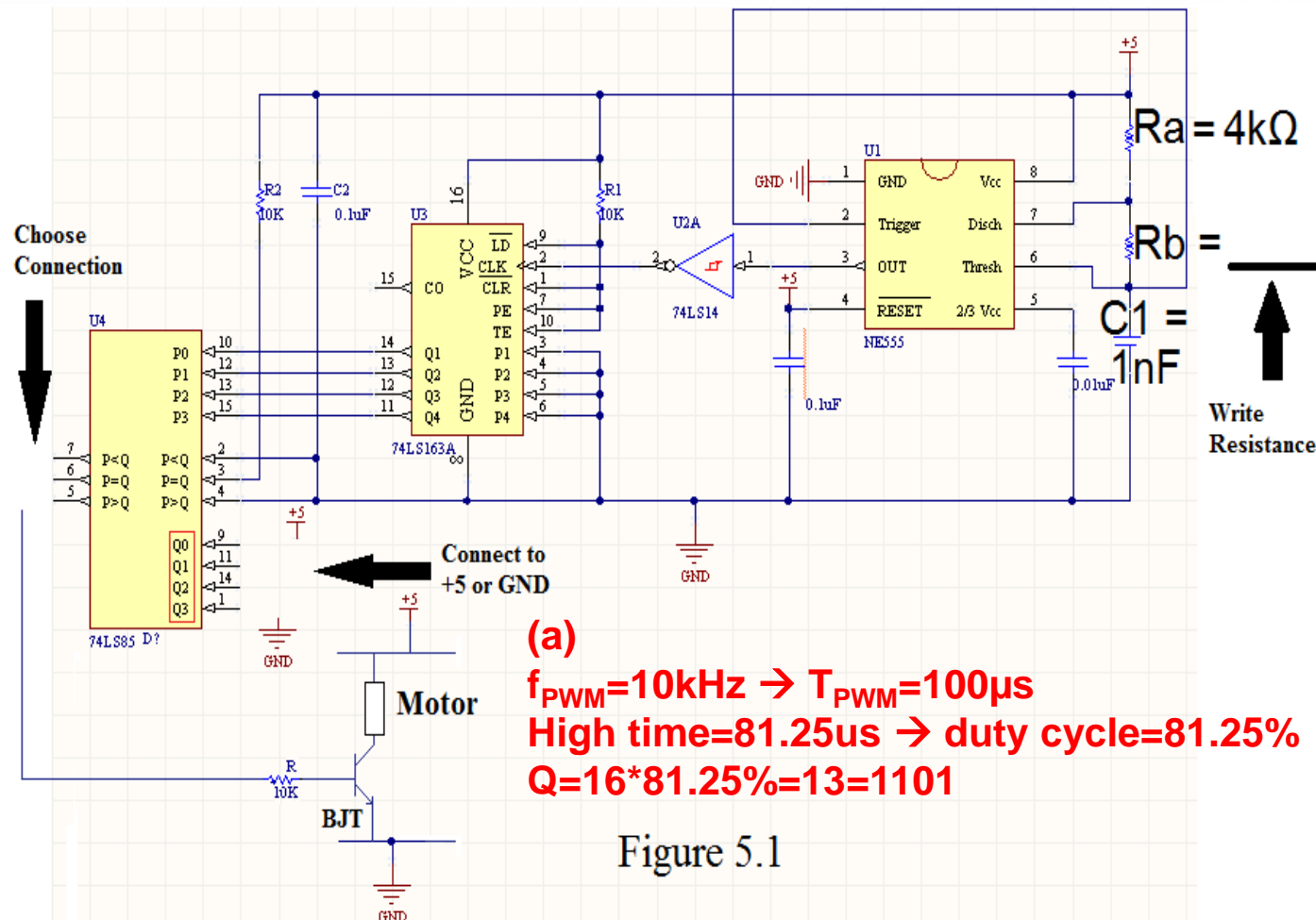- (a) Determine Q3-Q0.
- (b) Calculate R_b using timer equations.
- (c) Complete the schematic.






PAST PAPER: PWM CONTROL [2]

❖ PWM:

To design a PWM signal of frequency 10kHz and high time $81.25\mu s$ to drive a DC motor:

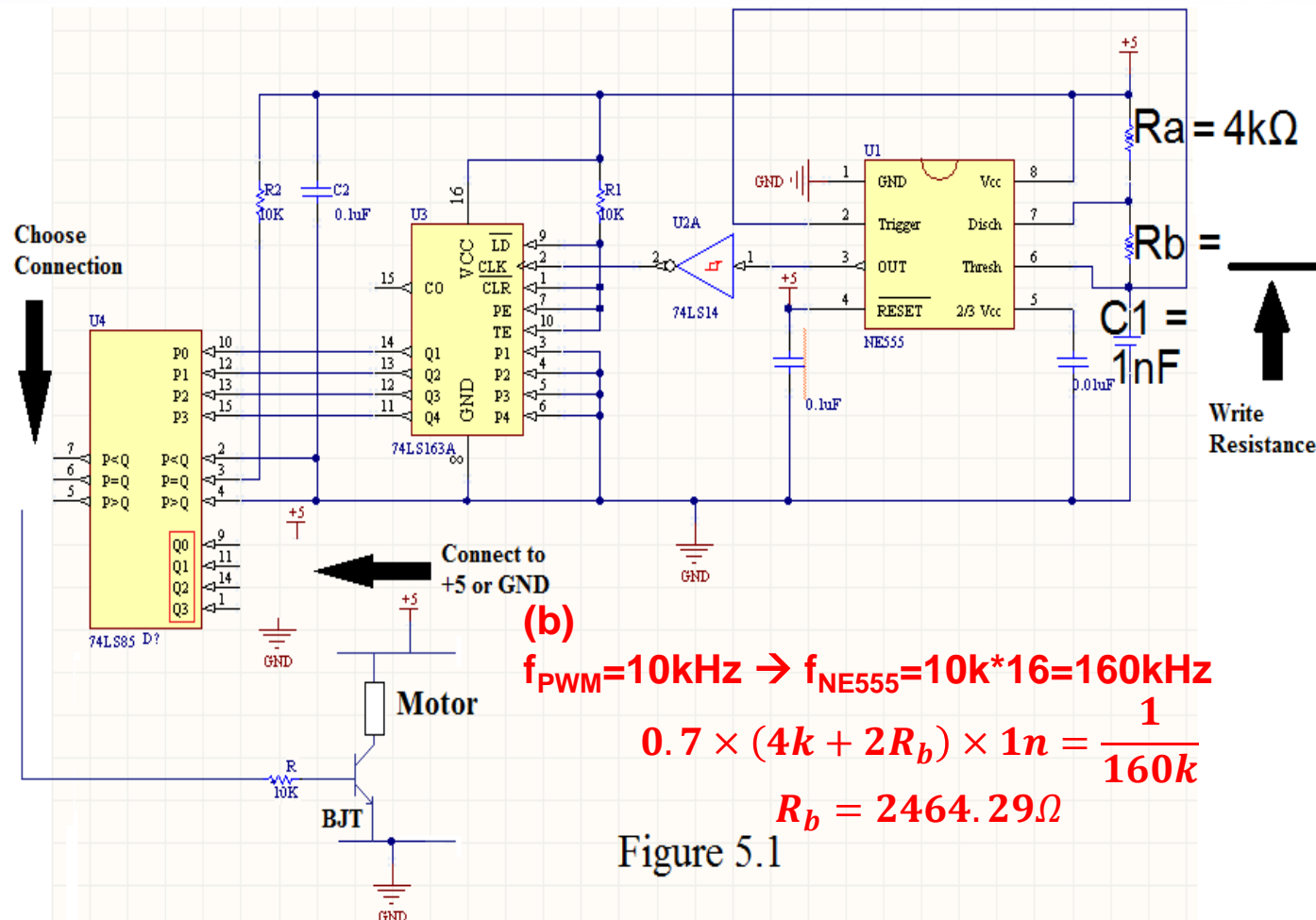- (a) Determine Q3-Q0.
- (b) Calculate R_b using timer equations.
- (c) Complete the schematic.





To design a PWM signal of frequency 10kHz and high time 81.25 μ s to drive a DC motor:

- [illegible]

Figure 5.1



PAST PAPER: LOGIC AND K-MAP [1]

❖ Logic and K-map:

We want to design a device to check whether an integer (from 0 to 9) is a multiple of 2 or 3. For example, the device returns true for integers 0, 2 and 3 but false for integers 1, 5 and 7. The decimal integer is input to the device as a 4-bit binary number (ABCD).

- Write down all the integers from 0 to 9 which are multiples of 2 or 3.

0, 2, 3, 4, 6, 8, 9

- Finish the truth table for outputs. (Remarks: “don’t care” conditions are allowed.)
- Use K-map to find out the *simplest* output expression in terms of the binary input ABCD.

A	B	C	D	Output
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	





PAST PAPER: LOGIC AND K-MAP [2]

❖ Logic and K-map:

We want to design a device to check whether an integer (from 0 to 9) is a multiple of 2 or 3. For example, the device returns true for integers 0, 2 and 3 but false for integers 1, 5 and 7. The decimal integer is input to the device as a 4-bit binary number (ABCD).

- Write down all the integers from 0 to 9 which are multiples of 2 or 3.

0, 2, 3, 4, 6, 8, 9

- Finish the truth table for outputs. (Remarks: “don’t care” conditions are allowed.)
- Use K-map to find out the *simplest* output expression in terms of the binary input ABCD.

A	B	C	D	Output
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X





PAST PAPER: LOGIC AND K-MAP [3]

❖ Logic and K-map:

We want to design a device to check whether an integer (from 0 to 9) is a multiple of 2 or 3. For example, the device returns true for integers 0, 2 and 3 but false for integers 1, 5 and 7. The decimal integer is input to the device as a 4-bit binary number (ABCD).

- Write down all the integers from 0 to 9 which are multiples of 2 or 3.

0, 2, 3, 4, 6, 8, 9

- Finish the truth table for outputs. (Remarks: “don’t care” conditions are allowed.)
- Use K-map to find out the *simplest* output expression in terms of the binary input ABCD.

$$\text{Output} = D' + A + B'C$$

		AB			
		00	01	11	10
CD	00	1	1	X	1
	01	0	0	X	1
	11	1	0	X	X
	10	1	1	X	X

A	B	C	D	Output
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X



QUESTIONS?

