

EE2026

Digital Design

COMBINATIONAL BLOCKS


Chua Dingjuan elechuad@nus.edu.sg

Combinational Building Blocks


- Combinational logic is often grouped into larger functional 'blocks'
- This layer of abstraction hides gate-level details and emphasizes the function of the building block
- Common building blocks :
 - Multiplexers / Demultiplexers
 - Decoders – Example BCD to 7-segment
 - Encoders
 - Adders – Half Adders, Full Adders, Ripple Adders
 - Tri-State Logic Elements (**Not Examinable**)
- Verilog modeling (parameter)

Multiplexer

 A multiplexer (MUX) is a combinational circuit element that selects data from one of 2^N inputs and directs it to a single output, according to an N-bit selection signal



Functional block diagram

 

Selection inputs allow one of the inputs to pass through to the output

Condensed truth table

| S_1 | S_0 | Z |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |



Actual truth table would have 2^6 rows !
(I_0 , I_1 , I_2 , I_3 , S_0 and S_1)

Example: 4:1 MUX

Multiplexers sometimes include enable input signal

$$Z = E \cdot (\overline{S_0}\overline{S_1}I_0 + S_0\overline{S_1}I_1 + \overline{S_0}S_1I_2 + S_0S_1I_3)$$


| E | S ₁ | S ₀ | I ₀ | I ₁ | I ₂ | I ₃ | Z |
|---|----------------|----------------|----------------|----------------|----------------|----------------|---|
| 0 | X | X | X | X | X | X | 0 |
| 1 | 0 | 0 | 0 | X | X | X | 0 |
| 1 | 0 | 0 | 1 | X | X | X | 1 |
| 1 | 0 | 1 | X | 0 | X | X | 0 |
| 1 | 0 | 1 | X | 1 | X | X | 1 |
| 1 | 1 | 0 | X | X | 0 | X | 0 |
| 1 | 1 | 0 | X | X | 1 | X | 1 |
| 1 | 1 | 1 | X | X | X | 0 | 0 |
| 1 | 1 | 1 | X | X | X | 1 | 1 |

```
module mux41(Z,S,I0,I1,I2,I3,E);  
  input I0, I1, I2, I3; // inputs  
  input [1:0] S; // 2-bit selection signal  
  input E; // enable  
  output Z;  
  
  assign Z = E ? ( S[1] ? (S[0] ? I3 : I2) : (S[0] ? I1 : I0) ) : 0;  
  
endmodule
```


Demultiplexer

A Demultiplexer (DEMUX) connects an input signal to any of 2^N output lines, based on an N-bit selection control

N-output switch

 

 **Functional block diagram
of 4-output demux**



Truth table

| D | S_1 | S_0 | Z_0 | Z_1 | Z_2 | Z_3 |
|---|-------|-------|-------|-------|-------|-------|
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

Example: 1:4 DEMUX

Boolean expression of output

$$Z_0 = D \cdot \overline{S_0} \cdot \overline{S_1}$$

$$Z_1 = D \cdot \overline{S_0} \cdot S_1$$

$$Z_2 = D \cdot S_0 \cdot \overline{S_1}$$

$$Z_3 = D \cdot S_0 \cdot S_1$$

| D | S ₁ | S ₀ | Z ₀ | Z ₁ | Z ₂ | Z ₃ |
|---|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

```
module demux41(Z0,Z1,Z2,Z3,S,D);
```

```
    input D; // input
```

```
    input [1:0] S; // 2-bit selection signal
```

```
    output Z0, Z1, Z2, Z3;
```

```
    assign Z0 = (S == 2'b00) ? D : 1'b0;
```

```
    assign Z1 = (S == 2'b01) ? D : 1'b0;
```

```
    assign Z2 = (S == 2'b10) ? D : 1'b0;
```

```
    assign Z3 = (S == 2'b11) ? D : 1'b0;
```


```
endmodule
```

MUX Application Example

Multiplexers can be used as *lookup tables* (LUT) to perform logic functions!

Alyssa needs to implement the function $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ for her project. However, the only part in her lab kit is an 8:1 multiplexer. How does she implement the function?

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | |
| 0 | 0 | 1 | |
| 0 | 1 | 0 | |
| 0 | 1 | 1 | |
| 1 | 0 | 0 | |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |

 


Decoder

Input: N-bit input code, Output : 2^N outputs

A decoder asserts ONE output as a function of the input (these outputs are also called one-hot!)

Functional block diagram

 

Truth Table

| A_2 | A_1 | A_0 | Z_0 | Z_1 | Z_2 | Z_3 | Z_4 | Z_5 | Z_6 | Z_7 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

Example: Decoder 2-4

A 2:4 decoder has 2^2 output lines for N inputs


- output can be single- or multi-bit

Enable signal

- if $E = 1$, normal operation
- if $E = 0$, disable outputs (all 0's)

Truth Table including Enable signal

| Inputs | | | Outputs | | | |
|--------|----------------|----------------|----------------|----------------|----------------|----------------|
| E | A ₁ | A ₀ | Z ₀ | Z ₁ | Z ₂ | Z ₃ |
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

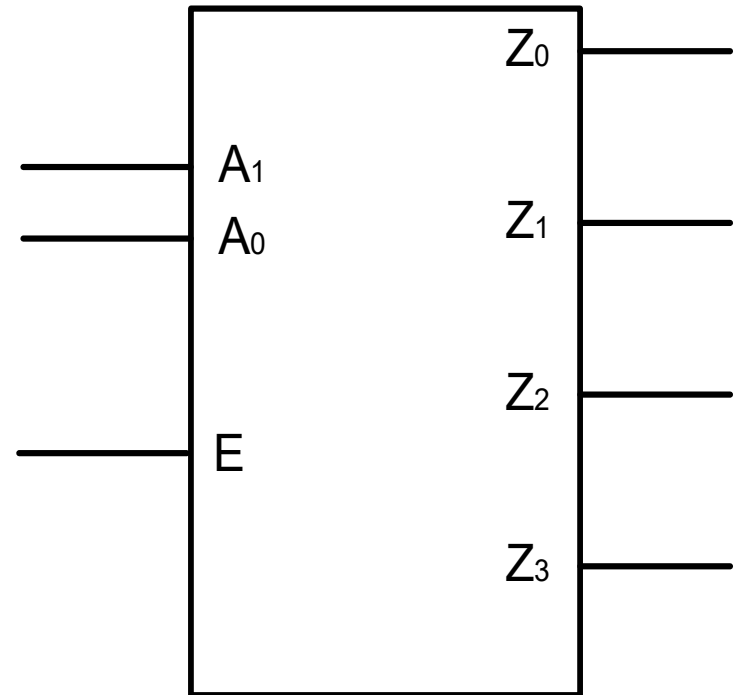

Functional block diagram

Decoder: Verilog

Dataflow Verilog description of a 2:4 decoder.

What if we would like to implement a 16:4 decoder instead?

```
module decoder24(Z,A,E);  
  input [1:0] A;  
  input E;  
  output [0:3] Z;  
  
  assign Z = ((A == 2'b00) & E) ? 4'b1000 :  
              ((A == 2'b01) & E) ? 4'b0100 :  
              ((A == 2'b10) & E) ? 4'b0010 :  
              ((A == 2'b11) & E) ? 4'b0001 :  
              4'b0000;  
  // 0000 is assigned if E=0  
  
endmodule
```

| Inputs | | | Outputs | | | |
|--------|----------------|----------------|----------------|----------------|----------------|----------------|
| E | A ₁ | A ₀ | Z ₀ | Z ₁ | Z ₂ | Z ₃ |
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

parameter

- Parameters are constants in Verilog (hence illegal to modify their value at runtime).
- They are often used to customize modules, helping to create more reusable code.

Parameterized dataflow Verilog description (arbitrary bit width)

```
module decoder(Z,A,E);  
    parameter M = 4; // parameterized design (sets # inputs)  
    parameter N = 2**M; // parameterized design (sets # outputs=2^M)  
  
    input [ M-1 : 0 ] A;  
    input E;  
    output [ 0 : N-1 ] Z;  
  
    wire [N-1:0] zerovec = {N{1'b0}}; // replication operator to create all zeroes.  
  
    assign Z = (E) ? (1 << A) : zerovec ;  
    // if enable=0, output is set to to zerovec (all zeroes)  
    // if enable=1, shift "1" A times and fill all other positions with zeros  
endmodule
```

parameter

- Modules can also be configured by passing parameters at instantiation!


```
module decoder #(parameter M = 4) (Z,A,E);  
    parameter N = 2**M ;  
    input [ M-1 : 0 ] A;  
    input E;  
    output [ 0 : N-1 ] Z;  
  
    wire [N-1:0] zerovec = {N{1'b0}};  
    assign Z = (E) ? (1 << A) : zerovec ;  
  
endmodule
```

Default value when none is provided


```
module top (input [4:0] sw, output [15:0] led);  
  
    decoder #(2) u1 (led[3:0], sw[1:0], sw[4]); //This creates a 2:4 decoder  
    //decoder #(4) u2 (led[15:0], sw[3:0], sw[4]); //This creates a 4:16 decoder  
  
endmodule
```

 Example: BCD-to-7 Segment Decoder

Converts a BCD number into signals required to display that number on a 7-segment display




 A 7-segment display. Each segment is an LED which will light when a logic 1 signal is applied to it




- 7-segment displays are of 2 types: *common anode* and *common cathode*
- Common anode display has all LED anodes connected and is active low, whereas the common cathode display is active high

Example - BCD-to-7 Segment Decoder

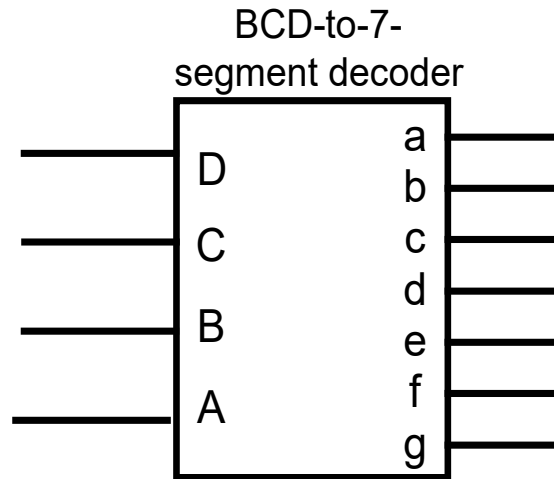

Functional block diagram

 


Truth Table

| D | C | B | A | a | b | c | d | e | f | g |
|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
| 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
| 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
| 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
| 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
| 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |

Encoder

- For different input bits (usually 2^N), encoder generates a code with fewer bits (usually N bits) uniquely identifying the input
 - performs the inverse of the decoding function

Functional block diagram

 

Truth Table (an 8-3 encoder)

| I_0 | I_1 | I_2 | I_3 | I_4 | I_5 | I_6 | I_7 | C_2 | C_1 | C_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

Example: Priority Encoder

- Generic encoders: error flagged if multiple input bits are 1
- Priority encoder allows multiple input bits to be 1
 - output set by the input bit with highest priority (i.e., most significant position), ignoring those with lower priority

| I ₀ | I ₁ | I ₂ | I ₃ | I ₄ | I ₅ | I ₆ | I ₇ | C ₂ | C ₁ | C ₀ |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| X | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | X | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| X | X | X | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| X | X | X | X | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| X | X | X | X | X | 1 | 0 | 0 | 1 | 0 | 1 |
| X | X | X | X | X | X | 1 | 0 | 1 | 1 | 0 |
| X | X | X | X | X | X | X | 1 | 1 | 1 | 1 |

Example: Priority Encoder

Dataflow Verilog description of 4-2 priority encoder

| I ₀ | I ₁ | I ₂ | I ₃ | C ₁ | C ₀ |
|----------------|----------------|----------------|----------------|----------------|----------------|
| 1 | 0 | 0 | 0 | 0 | 0 |
| X | 1 | 0 | 0 | 0 | 1 |
| X | X | 1 | 0 | 1 | 0 |
| X | X | X | 1 | 1 | 1 |

Use nested conditional operators, starting from MSB and progressively moving to the LSB


```
module priorityencoder(C,I);  
  input [3:0] I;  
  output [1:0] C;  
  assign C = (I[3]) ? (2'b11) : (I[2] ? (2'b10) : (I[1] ? (2'b01) : (2'b00)) );  
           // if I[3]=1, C=11  
           // else, if I[2]=1, C=10, etc.  
endmodule
```

- No clever parameterized dataflow Verilog description

Half Adders

It is a one bit binary adder with two inputs of A_i and B_i

 $0 + 0 = 0$
 $0 + 1 = 1$
 $1 + 0 = 1$
 $1 + 1 = 10$



| A_i | B_i | Sum_i | $Carry_{i+1}$ |
|-------|-------|---------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$S = \bar{A} \cdot B + A \cdot \bar{B} = A \oplus B$$



$$C = A \cdot B$$

Carry in from previous bit cannot be added

```
module ha(S,Cout,A,B);  
  input A, B;  
  output S, Cout; // Cout is the carry output  
  assign S = A ^ B;  
  assign Cout = A & B;  
endmodule
```

Full Adders

  Full adders can add carry bit from previous stage of addition



| A_i | B_i | C_i | S_i | C_{i+1} |
|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Full Adders (cont.)

K-map for SUM

| $B_i C_i \backslash A_i$ | 0 | 1 |
|--------------------------|---|---|
| 00 | 0 | 1 |
| 01 | 1 | 0 |
| 11 | 0 | 1 |
| 10 | 1 | 0 |

Note: C_{i+1} is not a MSOP, but less overall hardware is reqd. if we use this expression. It allows sharing of A_i XOR B_i between SUM_i and C_{i+1} .

K-map for CARRY

| $B_i C_i \backslash A_i$ | 0 | 1 |
|--------------------------|---|---|
| 00 | 0 | 0 |
| 01 | 0 | 1 |
| 11 | 1 | 1 |
| 10 | 0 | 1 |

$$\begin{aligned}
 SUM &= \bar{A}_i \bar{B}_i C_i + \bar{A}_i B_i \bar{C}_i + A_i \bar{B}_i \bar{C}_i + A_i B_i C_i \\
 &= \bar{A}_i (\bar{B}_i C_i + B_i \bar{C}_i) + A_i (\bar{B}_i \bar{C}_i + B_i C_i) \\
 &= \bar{A}_i (B_i \oplus C_i) + A_i (\overline{B_i \oplus C_i}) \\
 &= A_i \oplus B_i \oplus C_i
 \end{aligned}$$


$$\begin{aligned}
 C_{i+1} &= A_i B_i + A_i \bar{B}_i C_i + \bar{A}_i B_i C_i \\
 &= A_i B_i + C_i (A_i \bar{B}_i + \bar{A}_i B_i) \\
 &= A_i B_i + C_i (A_i \oplus B_i)
 \end{aligned}$$

Full Adder Circuit

$$SUM = (A_i \oplus B_i) \oplus C_i$$


$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

 Note: A full adder adds 3 bits
(3 input signals, each of 1 bit).



```
module fa(S,Cout,A,B,Cin);  
  input A, B, Cin; // Cin is the carry input  
  output S, Cout; // Cout is the carry output  
  assign S = A ^ B ^ Cin;  
  assign Cout = A & B | Cin & (A ^ B);  
endmodule
```

Parallel Adders

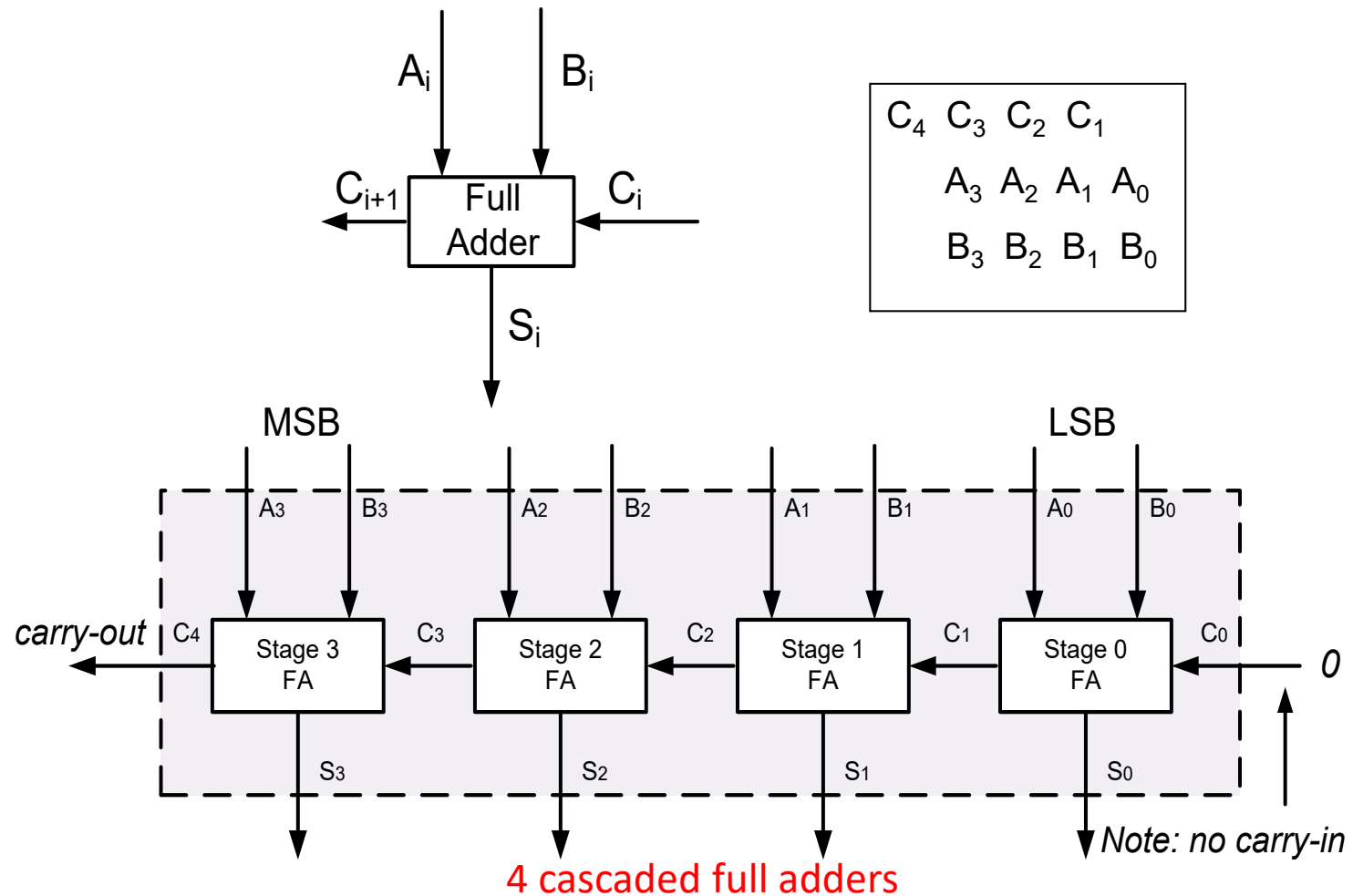


Parallel Adders (cont.)

In general, n full adders need to be used to form an n -bit adder

Carry ripple effect

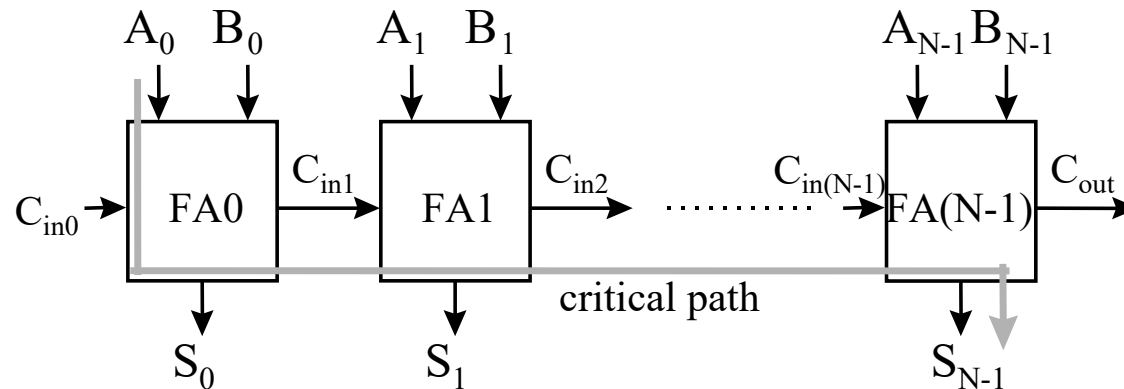- output of each full adder is not available until the carry-in from the previous stage is delivered
- carry bits have to propagate from one stage to the next
- as the carries *ripple* through the carry chain → also known as *ripple carry* adders



This slow rippling effect is substantially reduced by using *carry look ahead adders*

Parallel Adders (cont.)

Structural Verilog description (parameterized, arbitrary bit width)

```
module rca(S,Cout,A,B,Cin); // 4-bit ripple carry adder
  parameter N = 4; // parameterized bit width


  input [N-1:0] A, B;
  input Cin; // Cin is the adder carry input (at LSB)
  output [N-1:0] S;
  output Cout; // Cout is the adder carry output (at MSB)
  wire [N:0] C; // carry inputs of all full adders + carry output of last one

  assign C[0] = Cin;
  assign Cout = C[N];

  genvar i; // temp variable used only in generate loop
  generate for(i=0;i<N;i=i+1) begin
    fa FAinstance (.S(S[i]),.Cout(C[i+1]),.A(A[i]),.B(B[i]),.Cin(C[i]));
  end
endgenerate
endmodule
```


Magnitude Comparator

 Outputs are functions of relative magnitudes of input binary numbers A and B



Functional block diagram

Magnitude Comparator: Truth Table

2-bit magnitude comparator

| A_1 | A_0 | B_1 | B_0 | $(A > B)$ | $(A = B)$ | $(A < B)$ |
|-------|-------|-------|-------|-----------|-----------|-----------|
| 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 |

K-maps for $A > B$ and $A < B$

$A > B$

| $\begin{matrix} A_1 A_0 \\ B_1 B_0 \end{matrix}$ | 00 | 01 | 11 | 10 |
|--|----|----|----|----|
| 00 | 0 | 1 | 1 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 0 | 0 | 1 | 0 |

$$(A > B) = A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$$

$A < B$

| $\begin{matrix} A_1 A_0 \\ B_1 B_0 \end{matrix}$ | 00 | 01 | 11 | 10 |
|--|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 1 | 0 | 0 | 0 |
| 11 | 1 | 1 | 0 | 1 |
| 10 | 1 | 1 | 0 | 0 |

$$(A < B) = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

K-map for A=B

A=B

| $A_1A_0 \backslash B_1B_0$ | 00 | 01 | 11 | 10 |
|----------------------------|----|----|----|----|
| 00 | 1 | 0 | 0 | 0 |
| 01 | 0 | 1 | 0 | 0 |
| 11 | 0 | 0 | 1 | 0 |
| 10 | 0 | 0 | 0 | 1 |

$$(A = B) = \overline{A_1}\overline{A_0}\overline{B_1}\overline{B_0} + \overline{A_1}A_0\overline{B_1}B_0 \\ + A_1A_0B_1B_0 + A_1\overline{A_0}B_1\overline{B_0}$$

This can be generated
indirectly

using (A<B) and (A>B)



$$(A = B) = \overline{(A < B)} \cdot \overline{(A > B)}$$

Magnitude Comparator: Verilog

Dataflow Verilog description (parameterized, arbitrary bit width)


```
module magcomp(AgreaterB,AequalB,AlowerB,A,B);  
  parameter N = 4;  
  
  input [N-1:0] A, B;  
  output AgreaterB, AequalB, AlowerB;  
  
  assign AgreaterB = (A > B);  
  assign AequalB = (A == B);  
  assign AlowerB = (A < B);  
  /* to reduce complexity at the cost of slightly worse performance: assign  
    AlowerB = ~AgreaterB & ~AequalB */  
endmodule
```

Tri-State Logic Elements

Ordinarily, a digital device has 2 states

- tri-state devices also have *high impedance state (Z)*
 - floating output: the device does not force any voltage
 - voltage set by the output of some other device
 - if only one device is enabled at a time (all others in Z), multiple devices can drive the same node without conflicting
 - several tri-state logic gates
 - example: tri-state buffer with active-high enable

Functional block diagram

 

Voltage table

| E | D | Y |
|---|---|---|
| 1 | 0 | 0 |
| 1 | 1 | 1 |
| 0 | X | Z |

← Z = high impedance

Tri-State Logic Gates: Verilog

Dataflow Verilog description of various logic gates

tristate buffer with active-high enable

```
module tristatebuffer(Y,D,E);  
    input D, E;  
    output Y;  
    assign Y = E ? D : 1'bz;  
endmodule
```

tristate buffer with active-low enable

```
module tristatebuffer(Y,D,E);  
    input D, E;  
    output Y;  
    assign Y = E ? 1'bz : D;  
endmodule
```

tristate inverter with active-high enable

```
module tristateinv(Y,D,E);  
    input D, E;  
    output Y;  
    assign Y = E ? ~D : 1'bz;  
endmodule
```

tristate inverter with active-low enable


```
module tristateoinv(Y,D,E);  
    input D, E;  
    output Y;  
    assign Y = E ? 1'bz : ~D;  
endmodule
```

MUXes Based on Tri-State Elements


Tri-state gates with common output implement MUXes

When Control = 00, tri-state device for A_0 is enabled, others are disabled. Hence A_0 is connected to X_0 , etc.

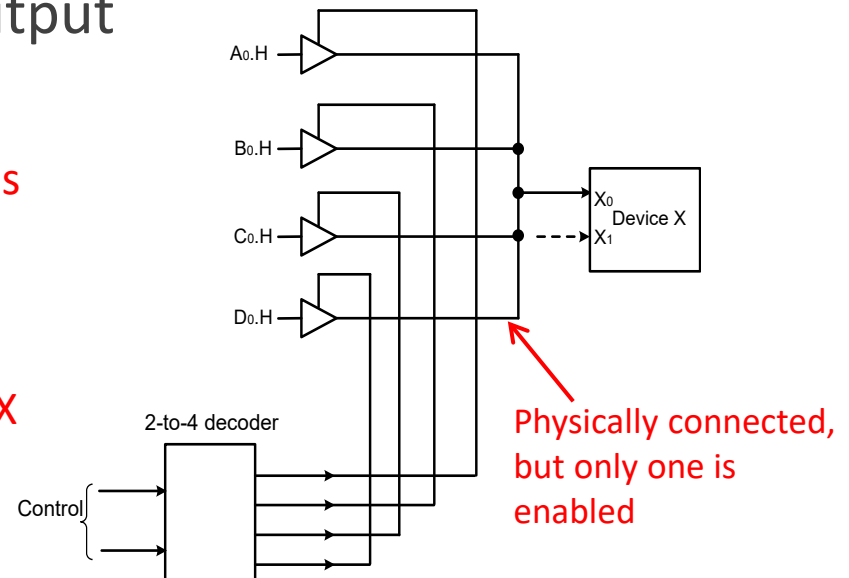Control signals select which input goes to X
⇒ effectively it behaves like a MUX



 - Useful to connect several resources to same bus
 - avoids expensive point-to-point interconnection
 - the enabled resource drives the bus (others in Z may receive)



Summary

Introduction to combinational building blocks and their Verilog description

Multiplexers / Demultiplexers

Decoders – Example BCD to 7-segment

Encoders

Adders – Half Adders, Full Adders, Ripple Adders

Tri-State Logic Elements (Not Examinable)
