




HOMEWORK 3

Issued on Nov. 7, 2021 (Sunday)


Due date: Nov. 16, 2021 (Tuesday), 11:59pm

[Please submit your homework online <https://canvas.ust.hk>]

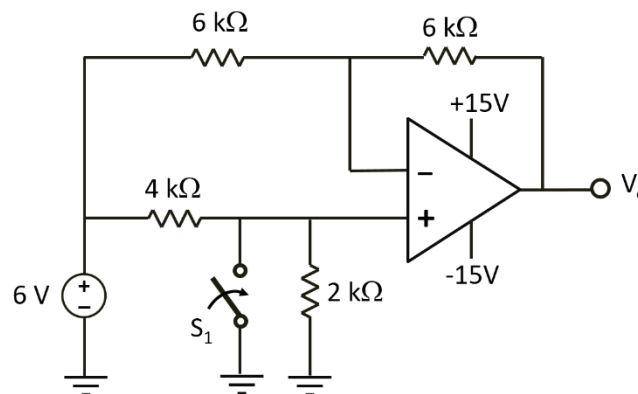
- Q1. Assuming ideal op amp, find the voltage V_o , (a) when the switch, S_1 , is open, and (b) when S_1 is closed.



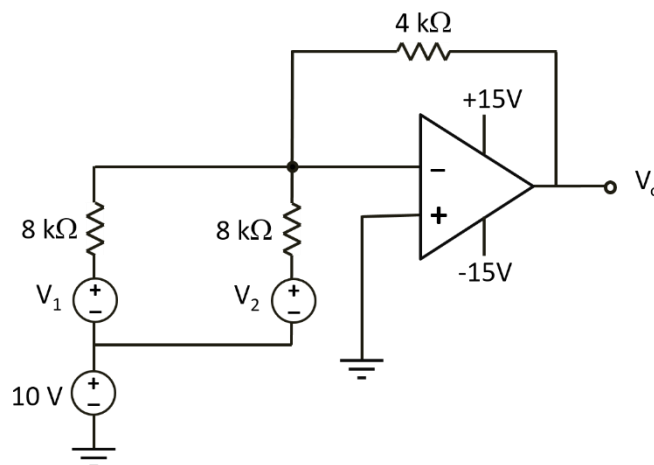- Q2. Assuming ideal op amp,
(a) Find the expression for V_o as a function of V_1 and V_2 .
(b) Find V_o when $V_1 = 4$ V, $V_2 = 4$ V.
(c) Find V_o when $V_1 = 4$ V, $V_2 = 8$ V.




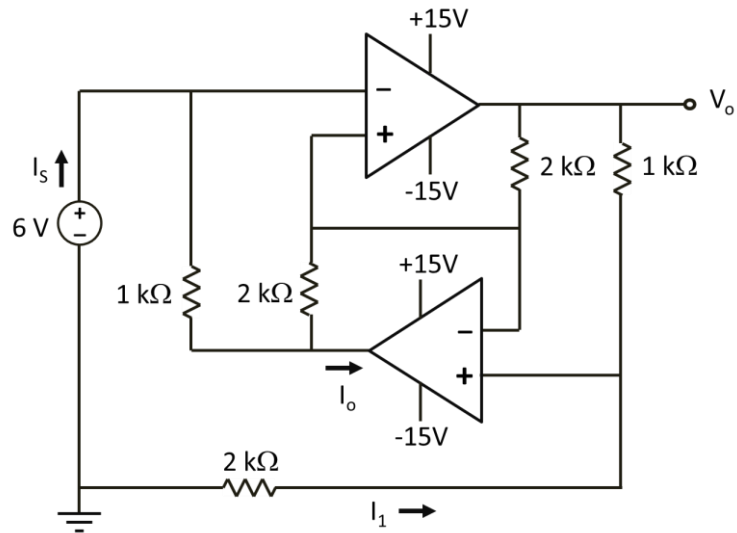Q3. Find I_1 , I_s , I_o and V_o assuming ideal op amps.






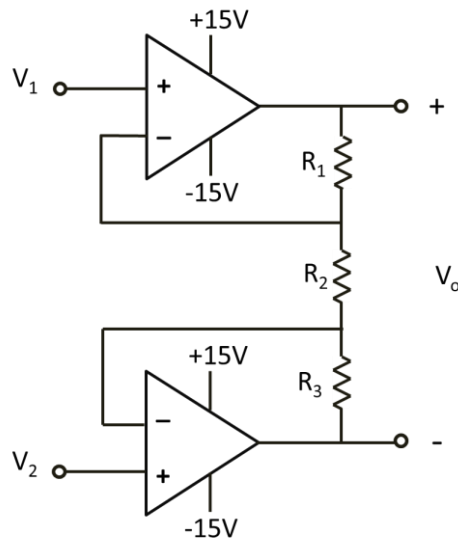Q4. Assuming ideal op amps,


- Find the expression for V_o as a function of V_1 and V_2 .
- Find V_o when $V_1 = 3\text{ V}$, $V_2 = 4\text{ V}$, $R_1 = R_2 = R_3 = 1\text{ k}\Omega$.



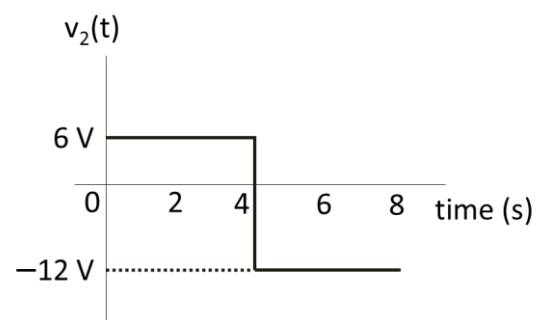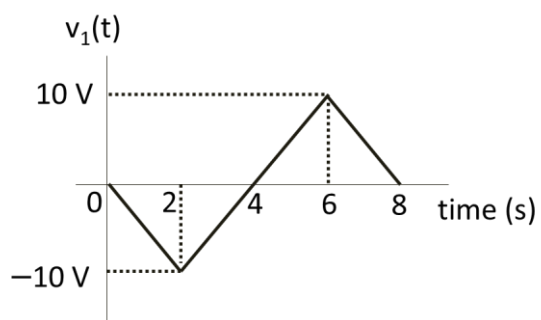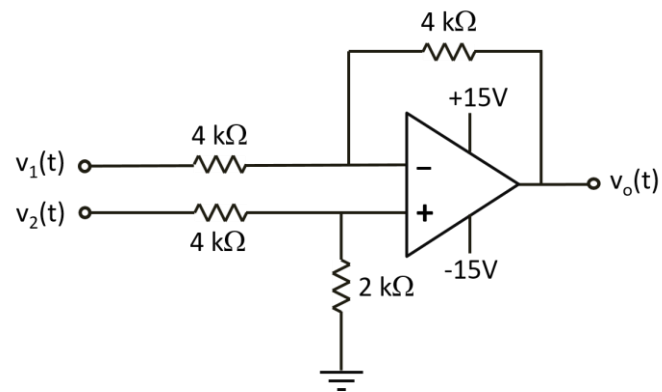Q5. Plot the waveform of $v_o(t)$ assuming ideal op amp.



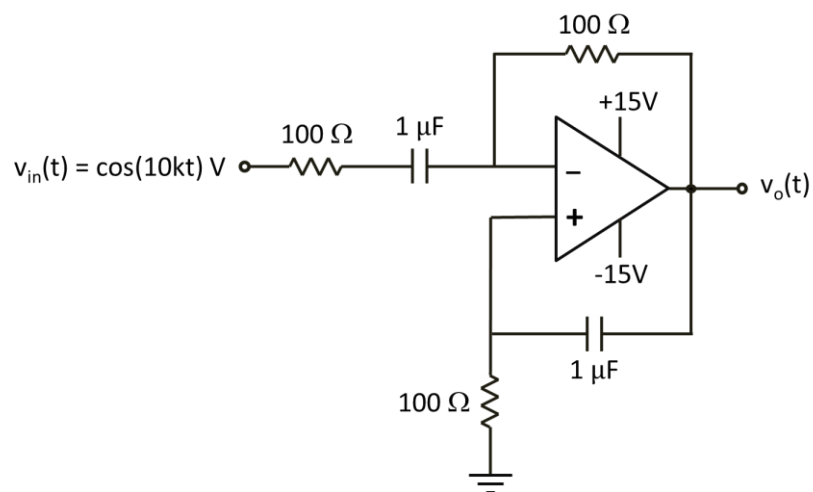Q6. Assuming ideal op amp, find $v_o(t)$.



Q7. Assuming ideal op amp, find $v_{in}(t)$.

