




## HOMework 5

Issued on Nov. 21, 2021 (Sunday)


Due date: Nov. 30, 2020 (Tuesday), 11:59pm

[Please submit your homework online <https://canvas.ust.hk>]

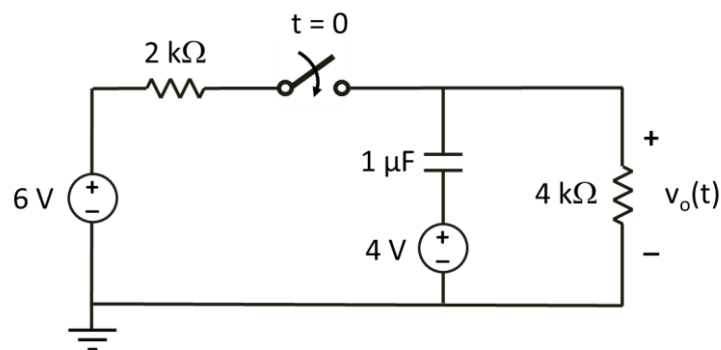
- Q1. Assume the switch has been open for a long time. The switch is closed at  $t = 0$ . Find the equation of the voltage  $v_o(t)$  for  $t > 0$ .



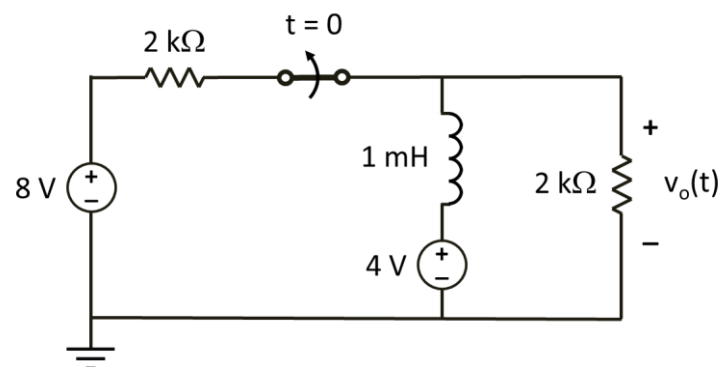
- Q2. Assume the switch has been closed for a long time. The switch is opened at  $t = 0$ . Find the equation of the voltage  $v_o(t)$  for  $t > 0$ .



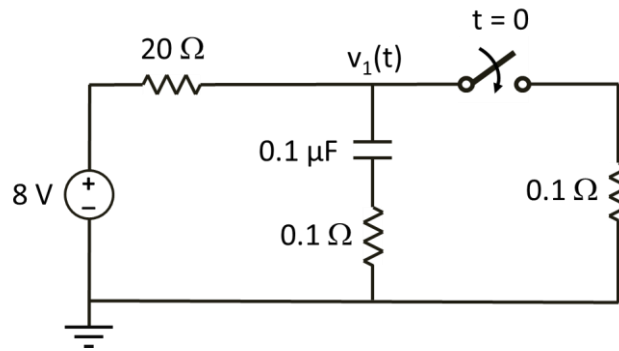
- Q3. Assume the switch has been open for a long time. The switch is closed at  $t = 0$ .
- Find the equation of the voltage  $v_1(t)$  for  $t > 0$ .
  - Plot  $v_1(t)$  as a function of time starting from  $t < 0$ .



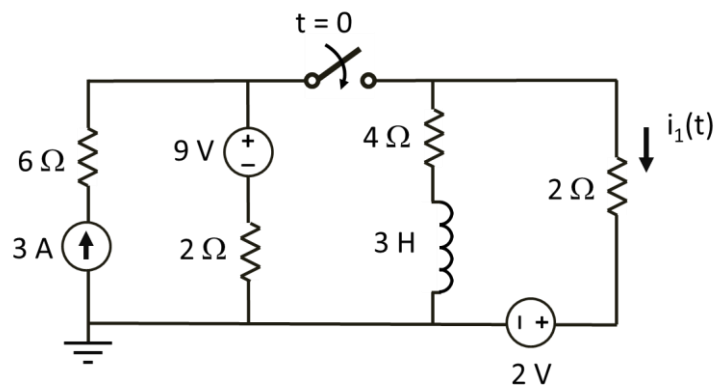
- Q4. Assume the switch has been open for a long time. The switch is closed at  $t = 0$ .
- Find the equation of the current  $i_1(t)$  for  $t > 0$ .
  - Plot  $i_1(t)$  as a function of time starting from  $t < 0$ .



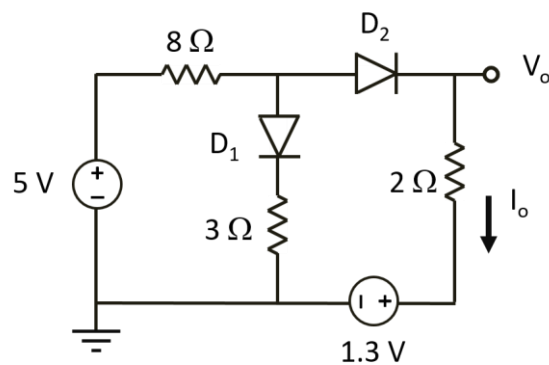
- Q5. Find  $V_o$  and  $I_o$  in the circuit below with
- ideal diode model,
  - offset diode model ( $V_F = 0.5\text{ V}$ ).



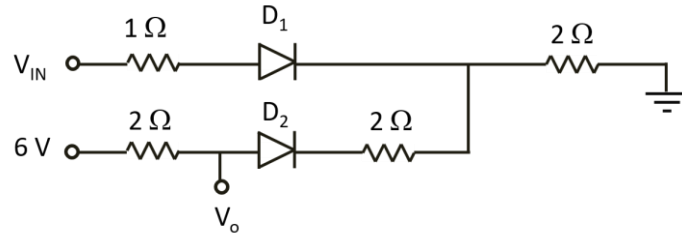- Q6. Plot  $V_o$  as a function of  $V_{IN}$  for  $V_{IN}$  from  $-5\text{ V}$  to  $25\text{ V}$  in the circuit with  
 (i) ideal diode model,  
 (ii) offset diode model ( $V_F = 0.5\text{ V}$ ).



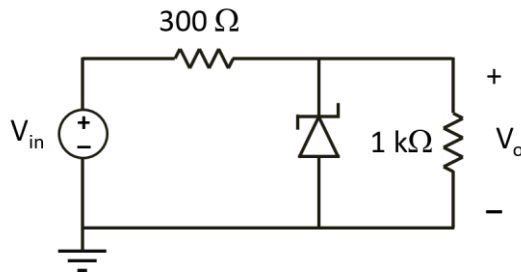- Q7. In the figure, it shows a Zener diode voltage regulator circuit ( $V_{Z0} = 5.6\text{ V}$ ,  $R_Z = 10\text{ }\Omega$ ).  
 (a) Determine the output voltage  $V_o$  if  $V_{IN} = 6.5\text{ V}$ .  
 (b) Plot  $V_o$  as the function of  $V_{IN}$  for  $6\text{ V} < V_{IN} < 8\text{ V}$ .



- Q8. Find  $V_o$  assuming ideal op amp and offset diode model ( $V_F = 0.5\text{ V}$ ) for the case:  
 (i) when  $V_{in} = 4\text{ V}$ ,  
 (ii) when  $V_{in} = -4\text{ V}$ .

