
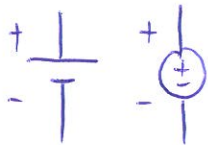
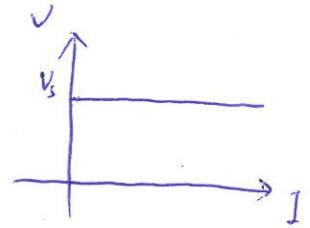


L4. DC Power & Regulation.


1. DC Source :

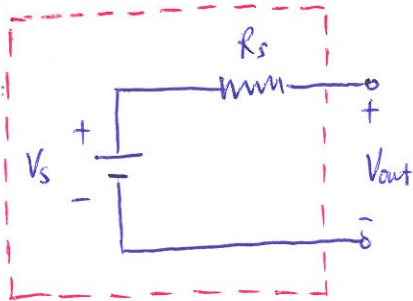1) Ideal Case:  \Rightarrow I-V characteristics



2) Real Case: 


What is the I-V characteristics?

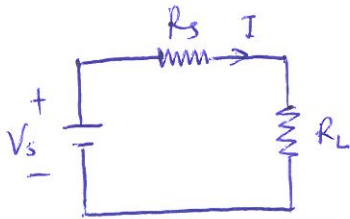



$$V_L = V_s - R_s \cdot I$$

$\left\{ \begin{array}{l} \text{If } V_L = 0, \text{ then } I = \frac{V_s}{R_s} \\ \text{If } I = 0, \text{ then } V_L = V_s \end{array} \right.$

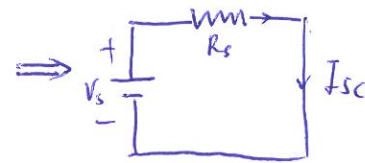
$I = \frac{V_s}{R_s}$ corresponds to the short-circuit current I_{sc}



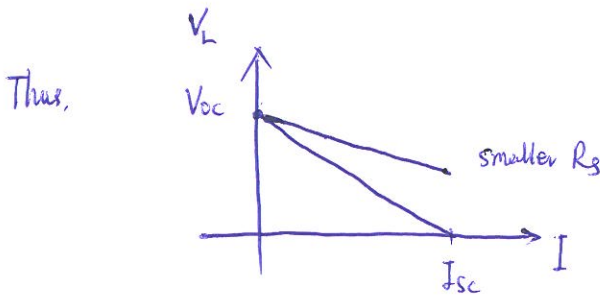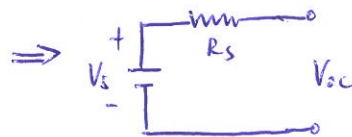$V_L = V_s$ corresponds to the open-circuit voltage V_{oc}



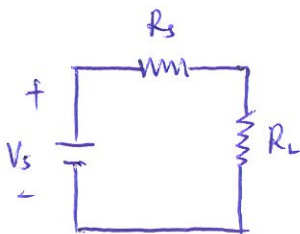2. Power efficiency & Maximum power consumption



two questions: $\left\{ \begin{array}{l} \text{What is the maximum power delivered to } R_L? \\ \text{What is the maximum power efficiency?} \end{array} \right.$

$$I = \frac{V_s}{R_s + R_L} \Rightarrow \begin{cases} P_s = I^2 R_s = \frac{V_s^2}{(R_s + R_L)^2} R_s \\ P_L = I^2 R_L = \frac{V_s^2}{(R_s + R_L)^2} R_L \end{cases}$$

Question 1: Max P_L
 R_L

$$P_L(R_L) = \frac{V_s^2}{(R_s + R_L)^2} R_L \quad \text{To maximize } P_L, \text{ we take the derivative of } P_L \text{ with respect to } R_L$$



$$\frac{dP_L(R_L)}{dR_L} = \frac{d\left(\frac{V_s^2}{(R_s + R_L)^2} R_L\right)}{dR_L} = \frac{V_s^2 (R_s + R_L)^2 - V_s^2 R_L 2(R_s + R_L)}{(R_s + R_L)^4}$$

$$\text{Let } \frac{dP_L(R_L)}{dR_L} = 0 \Rightarrow V_s^2 (R_s + R_L)^2 = V_s^2 R_L 2(R_s + R_L) \Rightarrow R_s + R_L = 2R_L \Rightarrow R_s = R_L$$

It is referred to as Load Match.

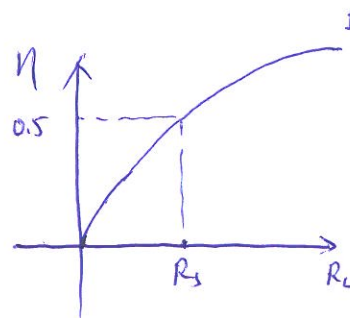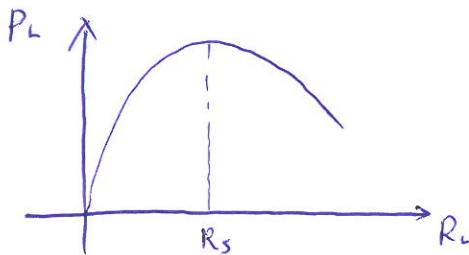Question 2: What is the maximum efficiency?

$$\eta = \frac{P_L}{P_s + P_L} = \frac{I^2 R_L}{I^2 R_s + I^2 R_L} = \frac{R_L}{R_s + R_L} = \frac{1}{\frac{R_s}{R_L} + 1} \text{ is an increasing function of } R_L.$$



3. Battery Characteristics

Battery voltage is not a constant


How can we stabilize the voltage of a battery?

4. Diode/Zener Diode/Regulator.


1) Diode: a device that only allows current to flow in one direction.

* Circuit model:


Ideal I-V characteristics:

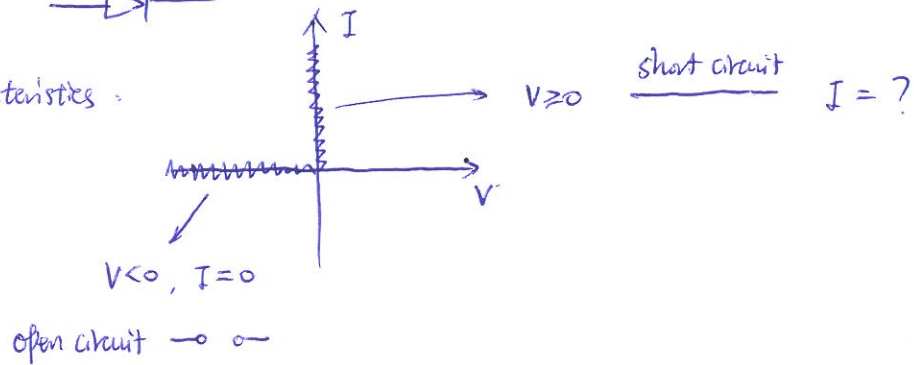

example:

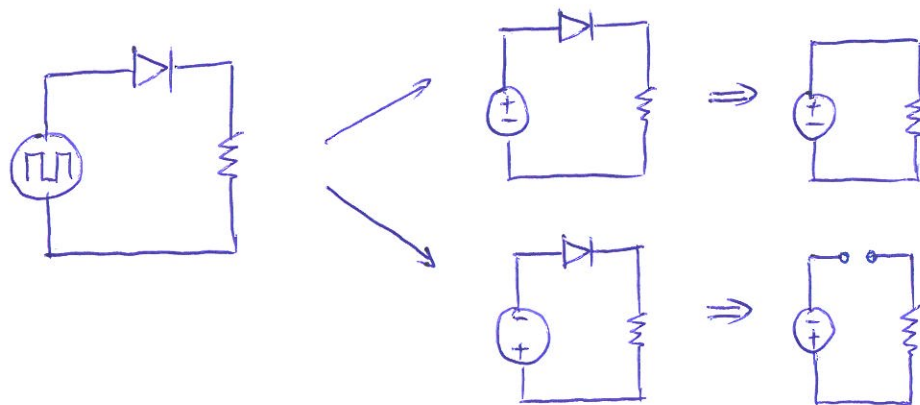

* Real diode:

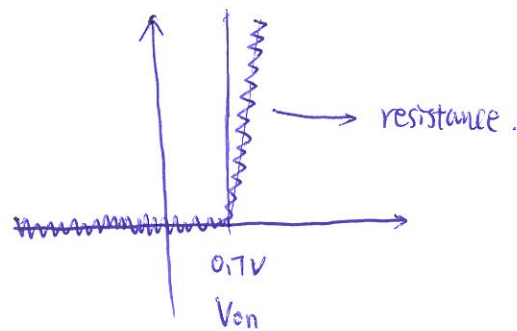


2) Zener Diode

Circuit model:


I-V characteristics

$$-V_{BD} < V < V_{on} \quad I = 0$$


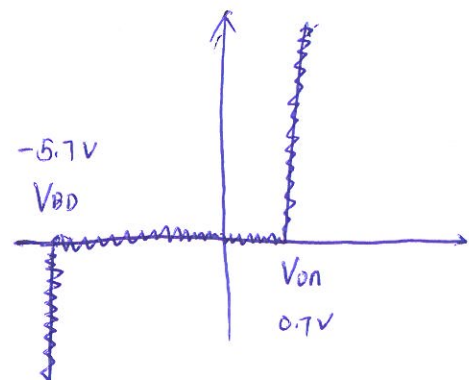
$$\begin{cases} V \geq V_{on} \\ V \leq -V_{BD} \end{cases} \quad I = \text{anything}$$



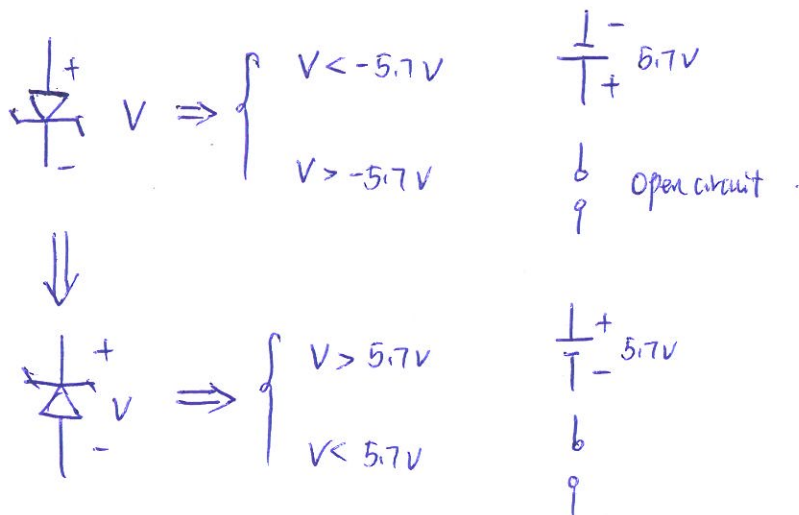
Normally, zener diode works in the breakdown region




3) Regulator

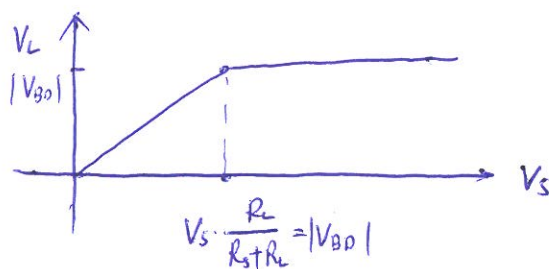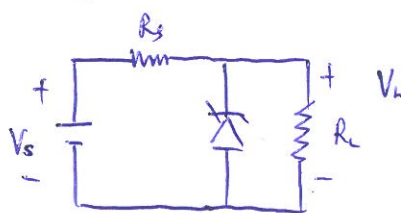

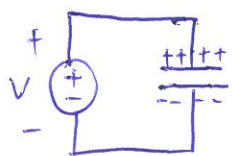
5. Capacitor : a device that stores energy in an electrical field.


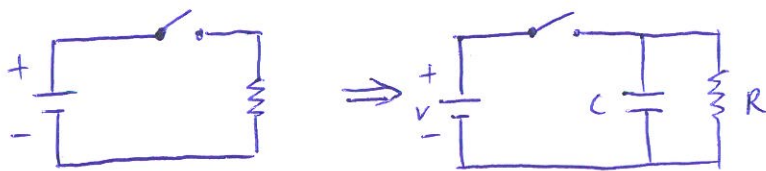
$$Q = CV \Rightarrow C = \frac{Q}{V} = \frac{\text{Coulomb}}{\text{Volt}} \quad \# \text{ of charges that can be stored if 1 Volt is applied.}$$




6. Regulator circuit

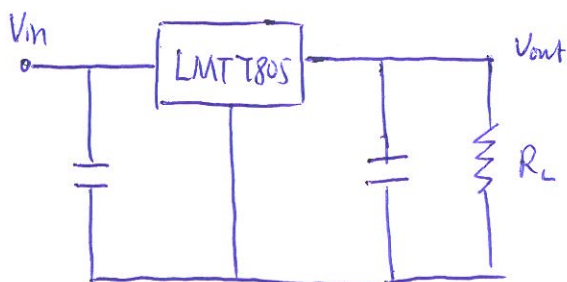

We have two parameters to measure the performance of a regulator.

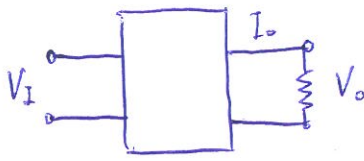
a. Line Regulation = $\frac{\Delta V_o}{\Delta V_i}$



$\frac{\Delta V_o}{\Delta V_i}$ How stable the output voltage is with respect to the input voltage?

Ideally, it is 0.

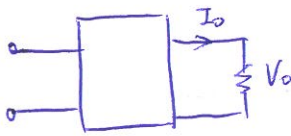b. Load Regulation: $\frac{\Delta V_o}{\Delta I_o}$



How stable the output voltage is with respect to the output current?

Ideally, it is 0

Example: $7V \leq V_{in} \leq 25V$

$$V_o = 5.0016V \text{ when } V_{in} = 7V.$$

$$V_o = 4.9976V \text{ when } V_{in} = 25V.$$

What is the line regulation?

$$\frac{\Delta V_o}{\Delta V_i} = \frac{5.0016 - 4.9976}{25 - 7} = \frac{0.004}{18} \approx 0.00022$$