


The background of the slide is a composite image. On the left, a white and black robotic arm is shown in profile, reaching out towards the center. The background features a series of DNA double helix structures that recede into the distance, and on the right, a row of server racks. A large, semi-transparent purple circle is centered over the text.

ELEC1100: Introduction to Electro-Robot Design

Lecture 13: MCU & Arduino



ELEC1100 ROADMAP

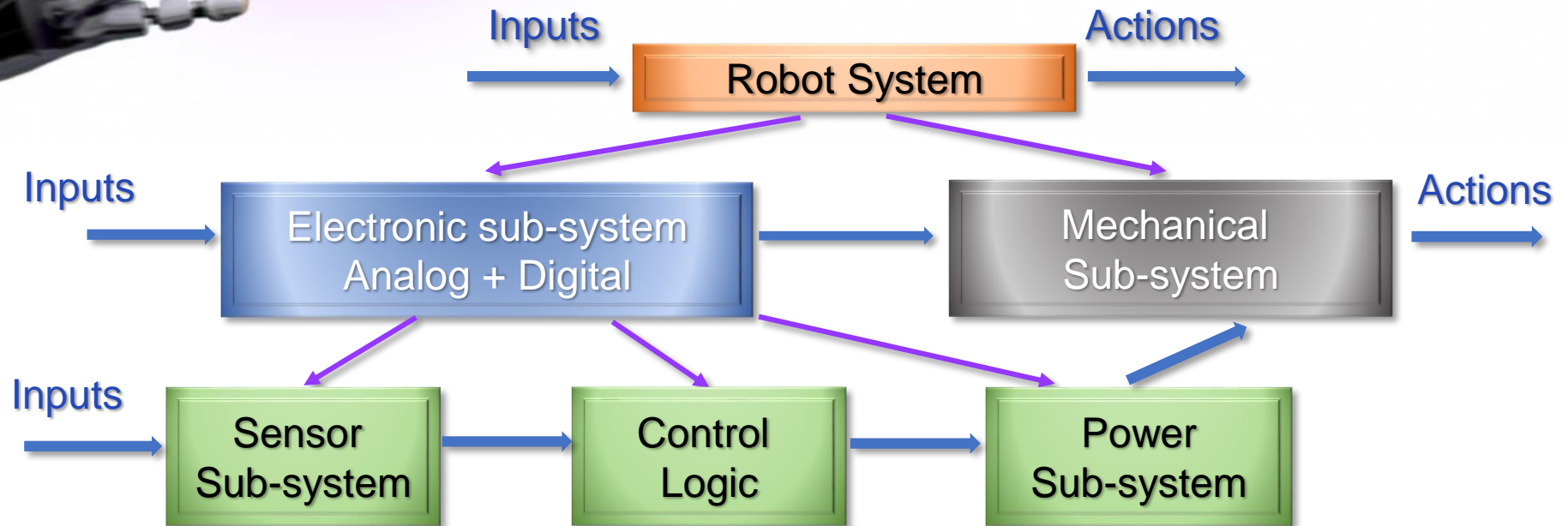

Sensor Basics:

Wk6: Sensor Basic –
Sensor/Line/ADC

Combinational/Sequential Logic:

Wk7: Robot Brain: Logic Gate and
Logic Operation

Wk8: MCU & Arduino

Basic electronics:

Wk1: Basic Electronics -
Charge/Current/Voltage/Resistor
Wk2: Energy/Power and DC Sources

Motor Power Supply:

Wk3: Pulse Signal and PWM Control
Wk4: Transistor and H-Bridge







FROM LAST LECTURE

❖ Combinational circuit

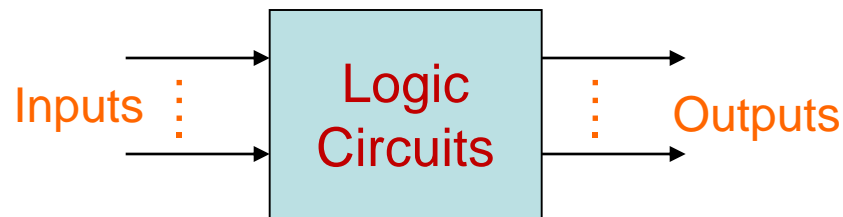- The outputs depend only on the current inputs of the circuits
- Output values are expressed by the truth table of the inputs



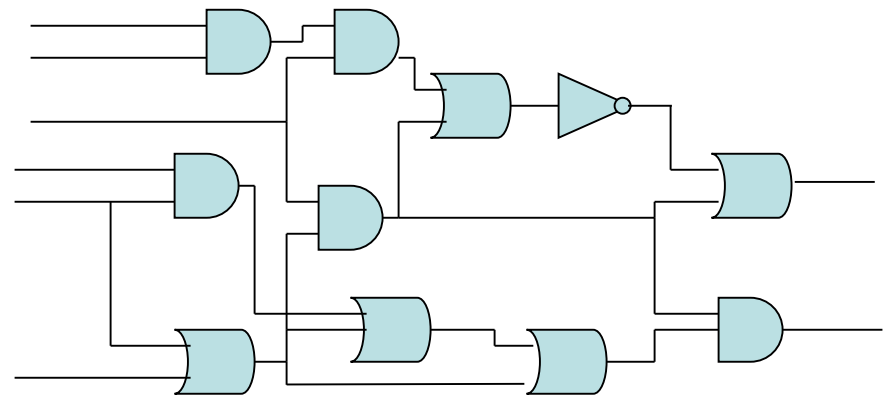- Logic level of combinational circuit:
maximum number of gates of all paths from inputs to outputs of the circuit



Logic level = 5






EXAMPLE: HALF ADDER

- ❖ The half adder is a circuit that adds two “1-bit numbers” and result of the addition is a “2-bit number”

- 2 inputs – A and B

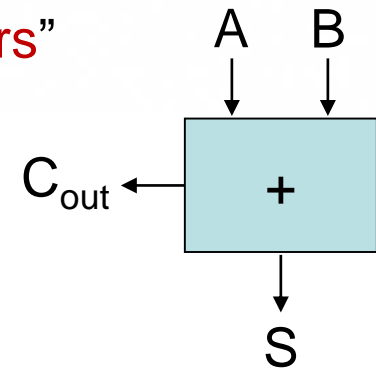
- 2 outputs – Sum (S) and Carry (C_{out})



$$A + B = 2^1 \times C_{out} + 2^0 S$$
$$= 2 \times C_{out} + S$$

- ❖ Truth table

A	B	S	C_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

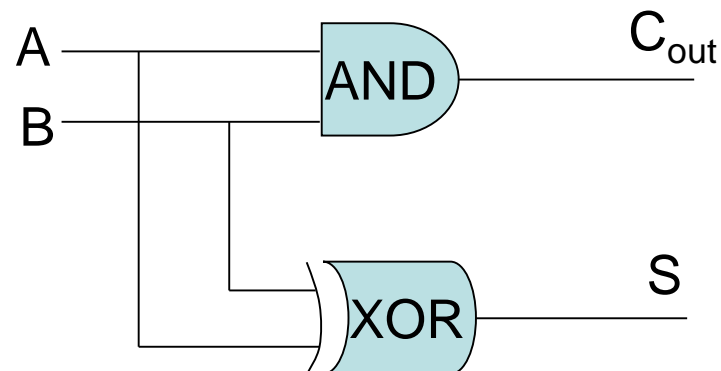



ONE-BIT FULL ADDER


❖ Full adder

- 3 inputs – A , B and C_{in}
- 2 outputs – Sum (S) and Carry (C_{out})

$$A + B + C_{in} = 2^1 \times C_{out} + 2^0 S$$
$$= 2 \times C_{out} + S$$

❖ Truth table

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

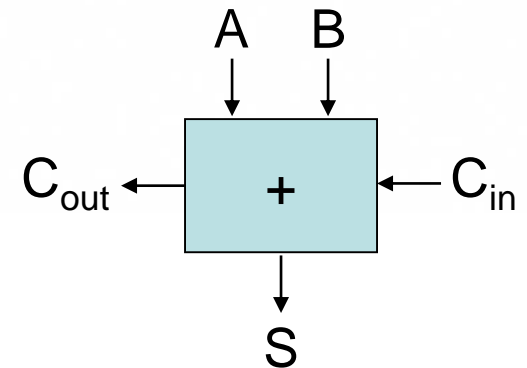

❖ K-map

S

	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
\overline{C}_{in}	0	1	0	1
C_{in}	1	0	1	0

C_{out}

	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
\overline{C}_{in}	0	0	1	0
C_{in}	0	1	1	1





ONE-BIT FULL ADDER IMPLEMENTATION


S

	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
\overline{C}_{in}	0	1	0	1
C_{in}	1	0	1	0

C_{out}

	$\overline{A}\overline{B}$	$\overline{A}B$	AB	$A\overline{B}$
\overline{C}_{in}	0	0	1	0
C_{in}	0	1	1	1

❖ Logic gate implementation

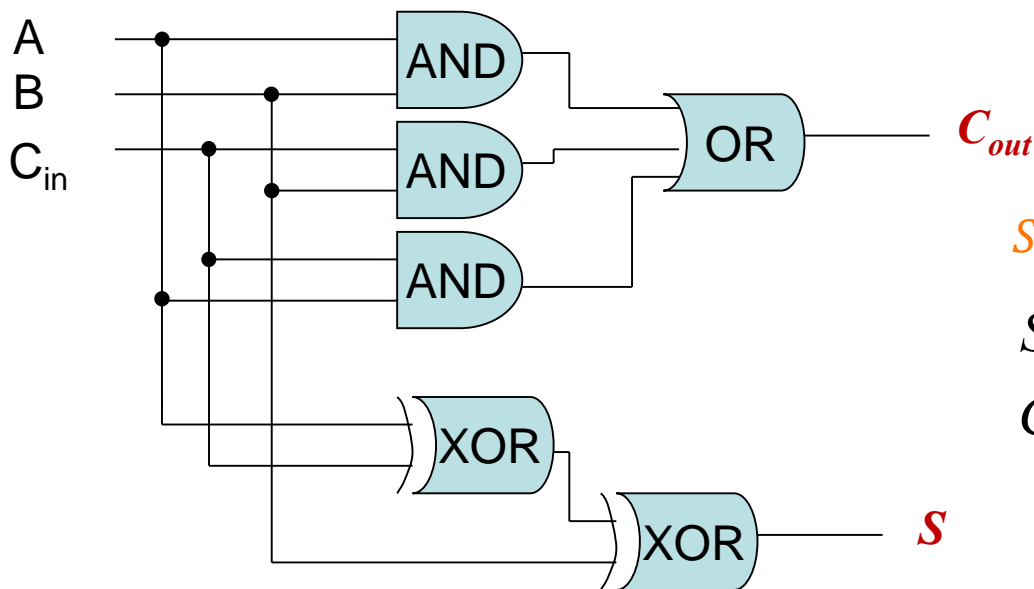

$$S = C_{in}\overline{A}\overline{B} + \overline{C}_{in}\overline{A}B + C_{in}AB + \overline{C}_{in}A\overline{B}$$

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = A \cdot B + A \cdot C_{in} + C_{in} \cdot B$$





COMBINATIONAL LOGIC

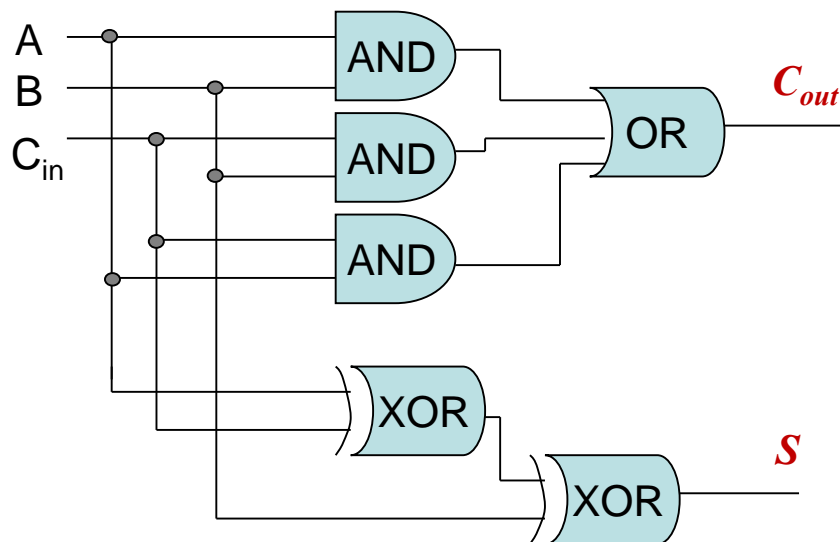- ❖ Output of the logic only depends on the current inputs but not on the history of the inputs
- ❖ As soon as the inputs change their values, the output (in general) will be affected




Take a full adder as an example

- if $A = 1$, $B = 1$, $C_{in} = 1$, then $C_{out} = 1$ and $S = 1$
- if A is changed to 0, then S is changed to 0



FROM 1-BIT ADDER TO N-BIT ADDER

❖ How to form N-bit adder ?

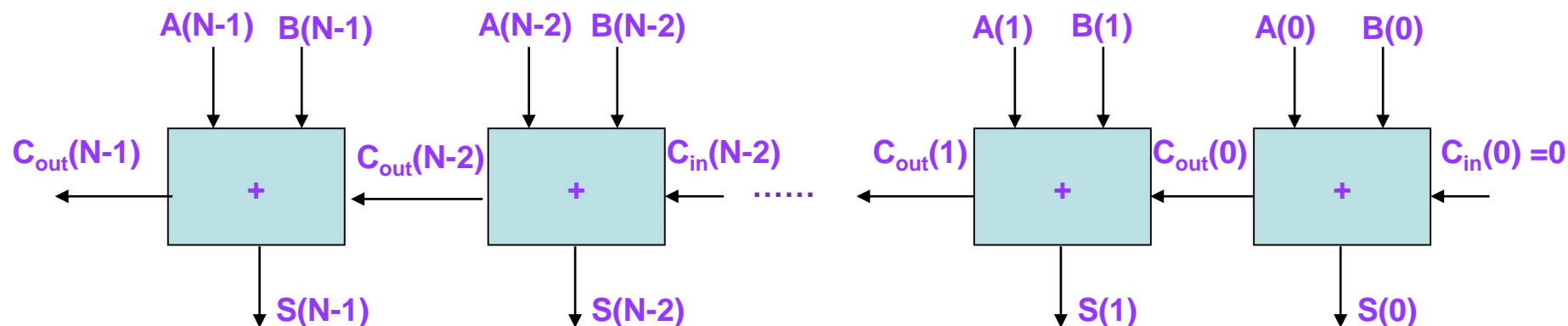

❖ Suppose we want to add m n-bit numbers (each X_i of the following equation is a N-bit number)

$$\text{Output} = X_{m-1} + X_{m-2} + \dots + X_1 + X_0$$

❖ How would you find the output?






COMBINATIONAL LOGIC APPROACH

- ❖ Example: using divide and conquer
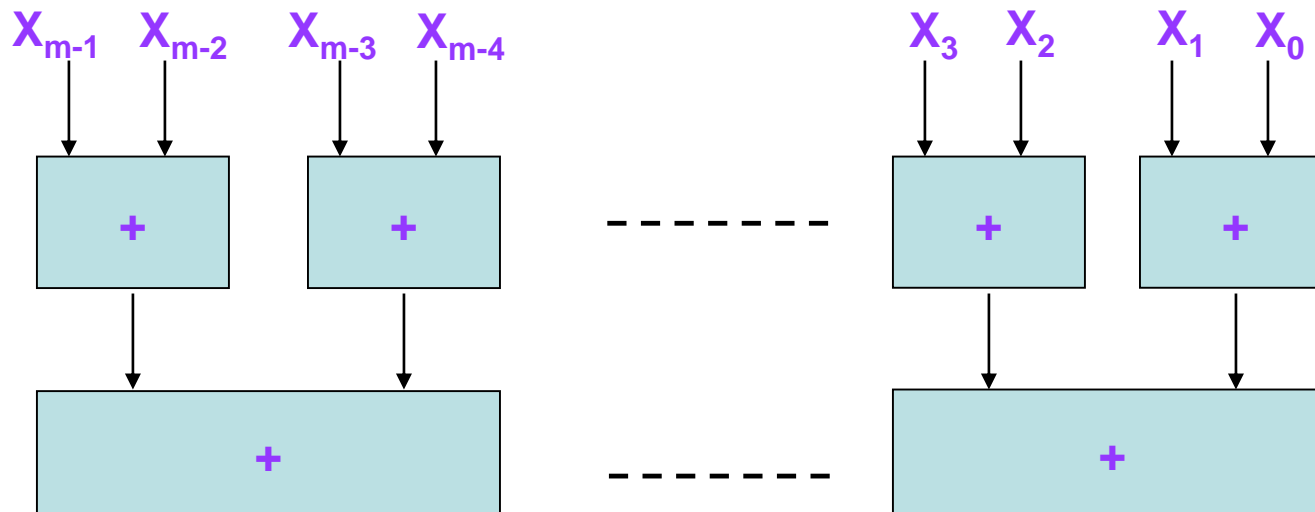
$$\text{Output} = (X_{m-1} + X_{m-2}) + \dots + (X_1 + X_0)$$




- ❖ How many adders do you need?



USING SEQUENTIAL LOGIC

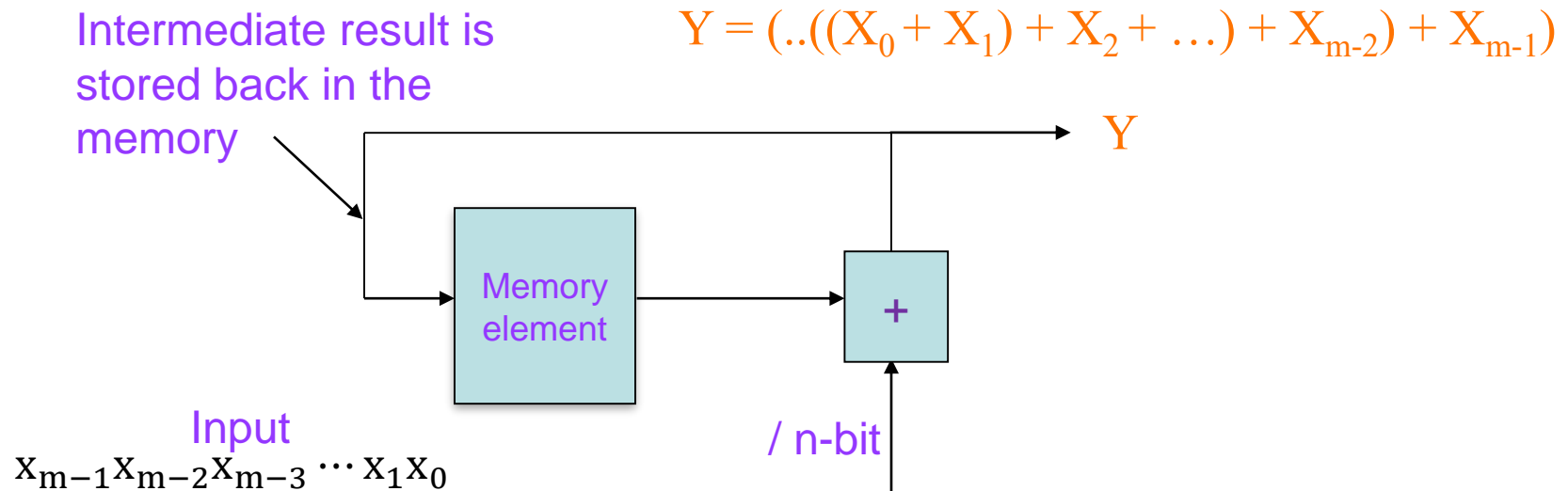- ❖ We can also use sequential logic to feedback the output of the intermediate sum to the input of the adder




- ❖ What is missing in the scheme?
- ❖ When will we know it is ready to send the data in?



SEQUENTIAL LOGIC CIRCUIT

- ❖ We need a **clock** signal to synchronize the input and the memory output

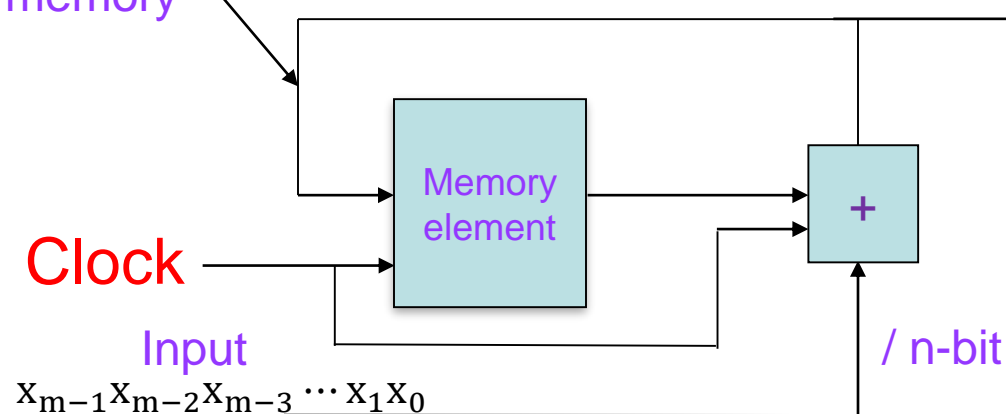Intermediate result is stored back in the memory



$$Y(t) = Y(t-1) + X(t); Y(-1) = 0$$

$$t=0: Y(0) = Y(-1) + X(0) = X(0)$$

$$t=1: Y(1) = Y(0) + X(1) = X(1) + X(0)$$

$$t=2: Y(2) = Y(1) + X(2) = X(2) + X(1) + X(0)$$

⋮

$$t=m-1: Y(m-1) = Y(m-2) + X(m)$$

$$= X(m-1) + \dots + X(1) + X(0)$$

- ❖ What is the drawback compared with combinational logic?
- ❖ A key element, **memory**, is needed






SEQUENTIAL LOGIC IN YOUR PROJECT

- ❖ How to differentiate (*detect* & *memorize*) each split?

Which way?

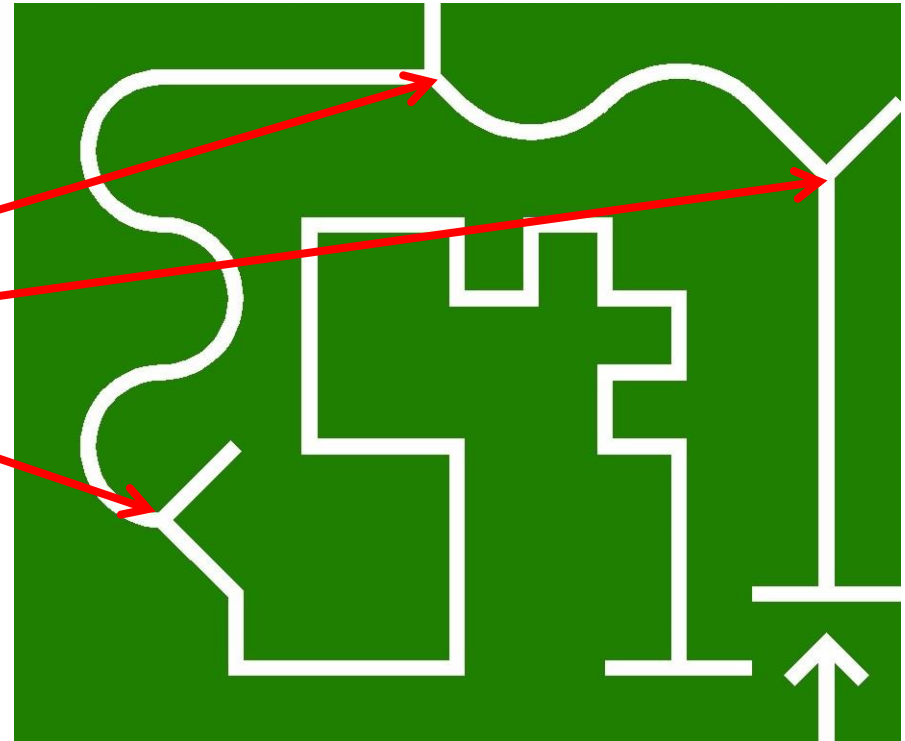

- ❖ You will need to use a *micro-controller* for involving the **clock** signal and **memory** unit into the logic control system for your vehicle.





MICRO-CONTROLLER

- ❖ A micro-controller (**MCU: micro-controller unit**) is a small computer on a single integrated circuit.
 - It is a full **computer on one chip** but with resources far from a limited desktop personal computer.
 - The single chip contain **CPU**, NON-volatile memory (**ROM**), volatile memory (**RAM**), **Timer & I/O port**.
 - There is no micro-controller works alone in circuit, it must interface with other external device like sensors, motors.....etc.



Atmel AVR Microcontroller





ARDUINO FAMILY

- ❖ **Arduino** is an open-source electronics platform that designs and manufactures **single-board micro-controllers** and micro-controller kits for building digital devices based on easy-to-use hardware and software.
- ❖ **Hardware: Arduino Boards**
You can tell your board what to do by sending a set of instructions to the micro-controller on the board.
- ❖ **Software: Arduino Integrated Development Environment (IDE)**
You can use Arduino programming language to write instructions and upload them to the Arduino board.

Arduino



Arduino Uno SMD R3

Developer	arduino.cc
Manufacturer	Many
Type	Single-board microcontroller
Operating system	None
CPU	Atmel AVR (8-bit), ARM Cortex-M0+ (32-bit), ARM Cortex-M3 (32-bit), Intel Quark (x86) (32-bit)
Memory	SRAM
Storage	Flash, EEPROM
Website	www.arduino.cc





SOME HISTORY

- ❖ The Arduino project started in 2003 as a program for students at the [Interaction Design Institute Ivrea](#) in *Ivrea, Italy*, aiming to provide a low-cost and easy way for novices and professionals to create devices that interact with their environment using sensors and actuators.
- ❖ The name **Arduino** comes from a bar in Ivrea, Italy, where some of the founders of the project used to meet. The bar was named after *Arduin of Ivrea*, who was the margrave of the March of Ivrea and King of Italy from 1002 to 1014.

Arduin of Ivrea



King of Italy






ARDUINO BOARDS

- ❖ Arduino board designs use a variety of micro-processors and controllers. The boards are equipped with sets of digital and analog input/output (I/O) pins that may be interfaced to various expansion boards or breadboards and other circuits.
- ❖ The boards feature serial communications interfaces, including Universal Serial Bus (USB) on some models, which are also used for loading programs from personal computers.


Different Types of Arduino Boards

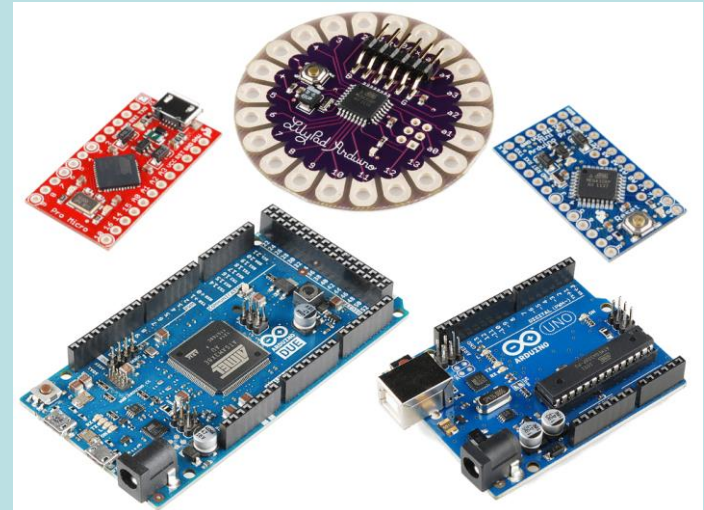



ARDUINO SOFTWARE IDE

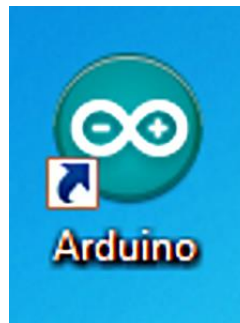- ❖ The Arduino Software IDE is a cross-platform application (for Windows, macOS, Linux) that is written in the programming language **Java**, also supports the languages **C** and **C++**.
- ❖ It includes a code editor, and provides simple *one-click* mechanisms to compile and upload programs to an Arduino board.



The Arduino software IDE on the desktop of your lab computer.






ARDUINO SKETCH

❖ A sketch is a program written with the Arduino IDE.

A minimal Arduino C/C++ program consists of only two functions:

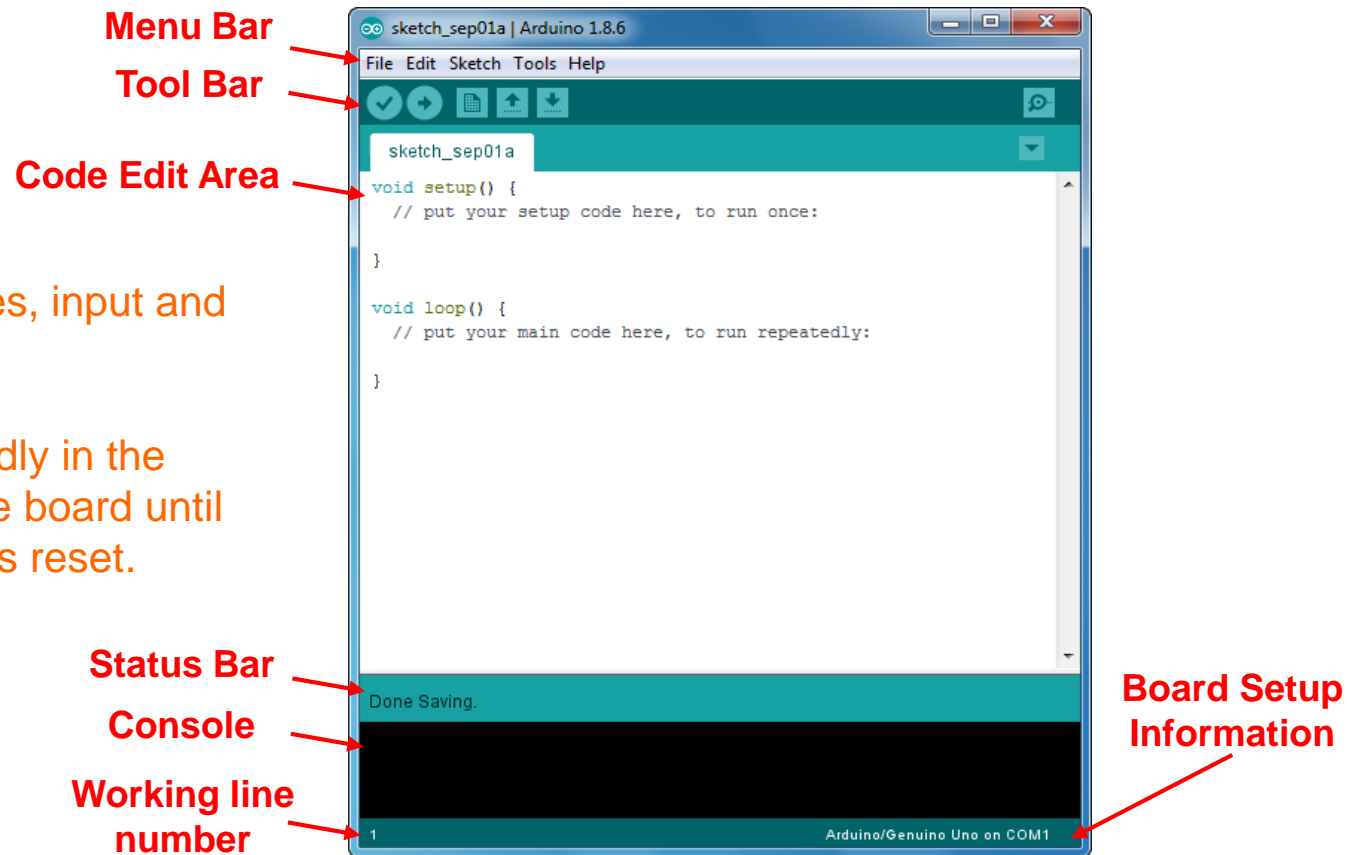- **setup()**: to initialize variables, input and output pin modes.
- **loop()**: is executed repeatedly in the main program. It controls the board until the board is powered off or is reset.






BLINK EXAMPLE

- ❖ Most Arduino Boards contain a **LED** and a current limiting resistor connected between **pin 13** and **ground**, which is a convenient feature for many tests and program functions.

```
#define LED_PIN 13           // Pin number attached to LED.


void setup() {
  pinMode(LED_PIN, OUTPUT);  // Configure pin 13 to be a digital output.
}

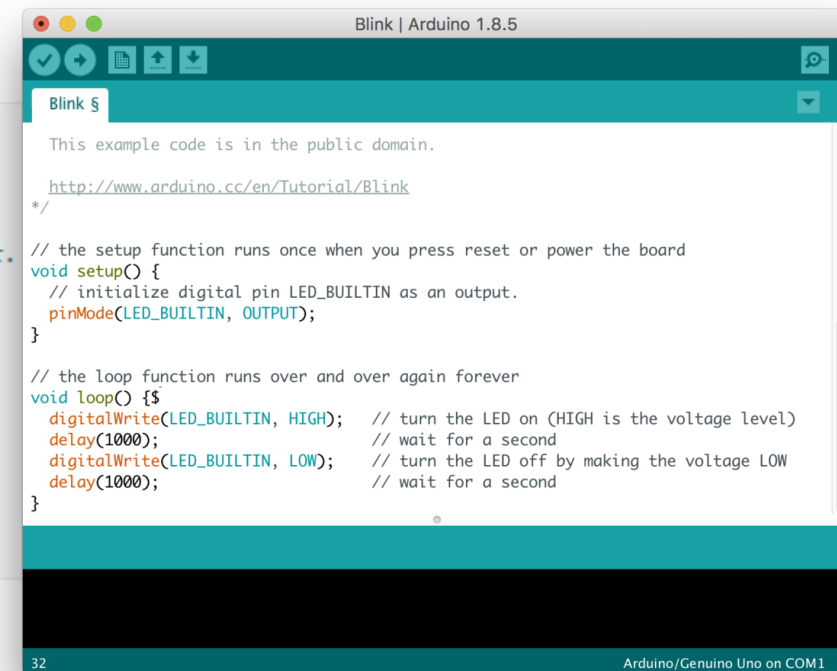void loop() {
  digitalWrite(LED_PIN, HIGH); // Turn on the LED.
  delay(1000);                 // Wait 1 second (1000 milliseconds).
  digitalWrite(LED_PIN, LOW);  // Turn off the LED.
  delay(1000);                 // Wait 1 second.
}
```



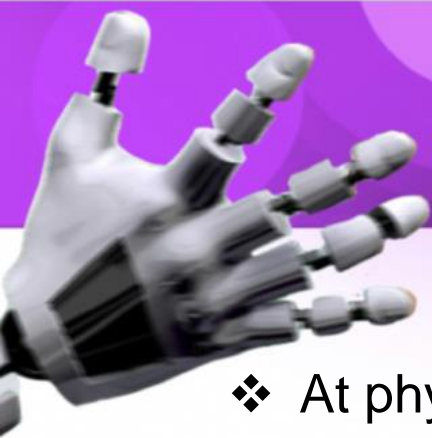Screenshot of Arduino IDE showing *Blink* program





YOUR LAB TOOLS

❖ At physical lab:




Arduino compatible
Nano-Board



IC Socket



Mini-B to Type-A USB cable

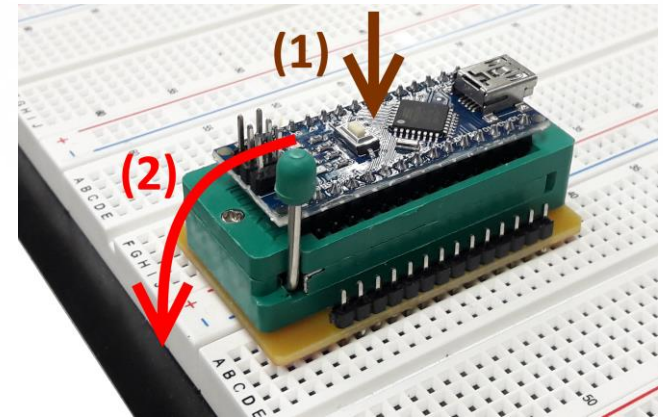

Pull down the handle to lock
your Nano-board




Connect Nano-Board
to computer's USB port



ON-LINE SIMULATION

❖ In Tinkercad:

Arduino Uno-Board


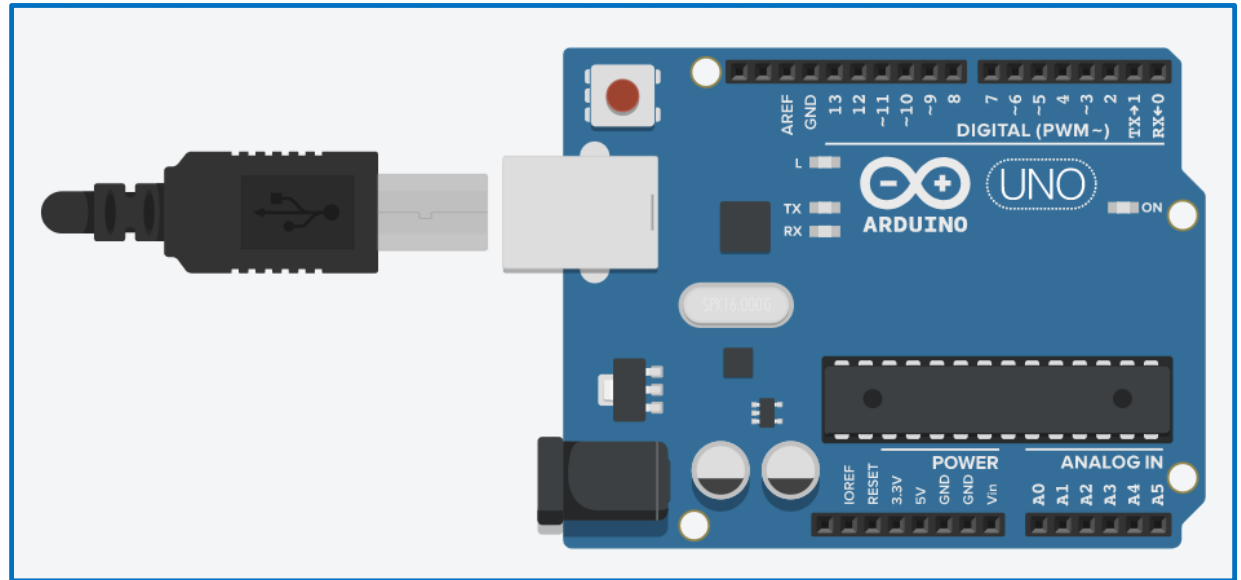


- Arduino Uno-board fairly similar to Arduino Nano-board as both are built with a microcontroller Atmega328.
- Nano-board is preferred at physical lab because of **small in size**.



INPUT/OUTPUT SIGNALS

❖ Your lab#05:

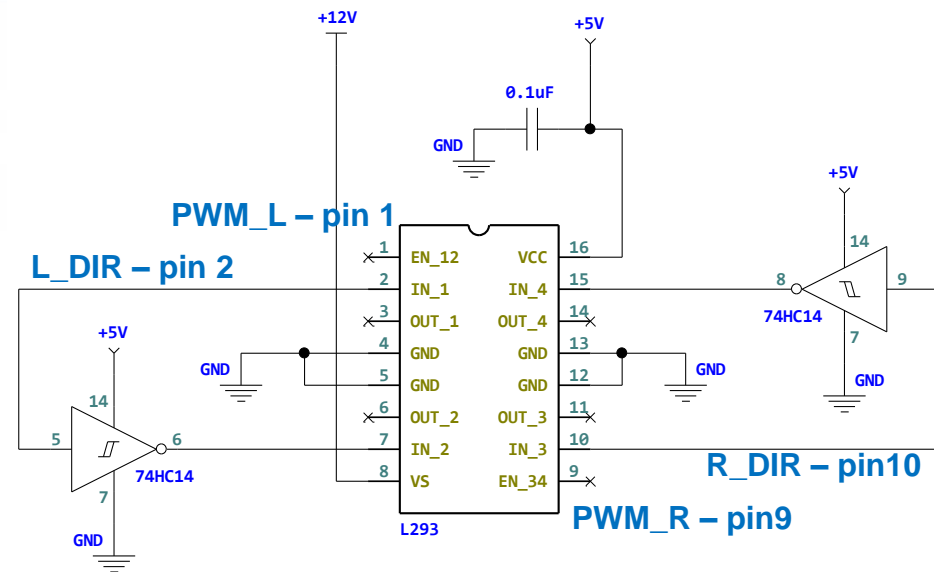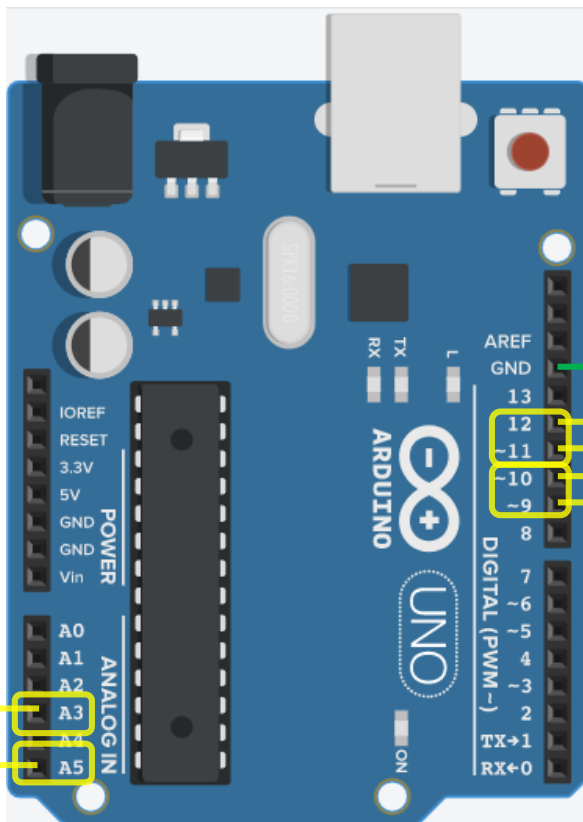



Connect your Uno-Board to the circuits from previous labs on your breadboard.






LECTURE SUMMARY

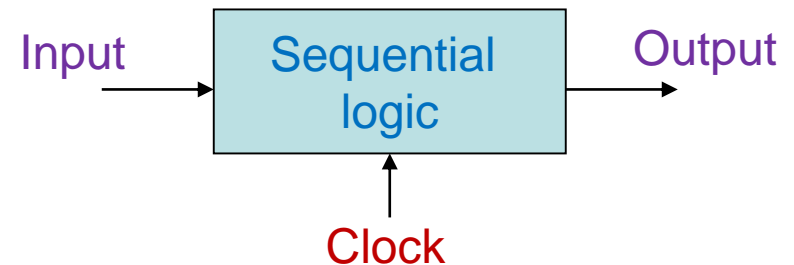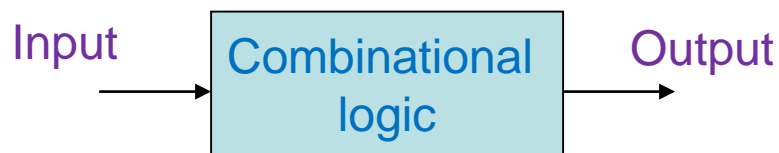- ❖ Combinational logic: Output changes as soon as inputs change
- ❖ Sequential logic: Output may change only at a specific time, depending on the clock signal.



- ❖ Arduino: Your logic & memory unit.

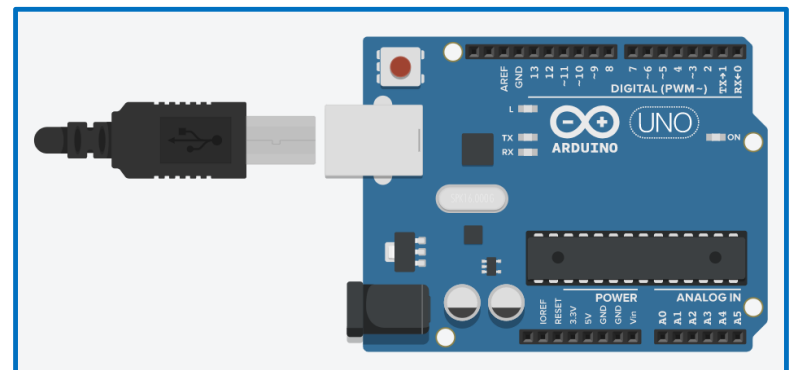



NEXT LECTURE

❖ Arduino Code:

- Introduction
- Functions
- Variables



QUESTIONS?

