



## HOMEWORK 4


Issued on Nov. 14, 2021 (Sunday)

Due date: Nov. 23, 2021 (Tuesday), 11:59pm


[Please submit your homework online <https://canvas.ust.hk>]

Assume ideal op amp in all cases.

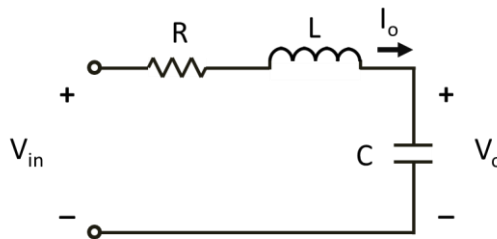Q1. Find the transfer functions  $H(s) = \frac{V_o(s)}{V_{in}(s)}$  and  $G(s) = \frac{I_o(s)}{V_{in}(s)}$ .



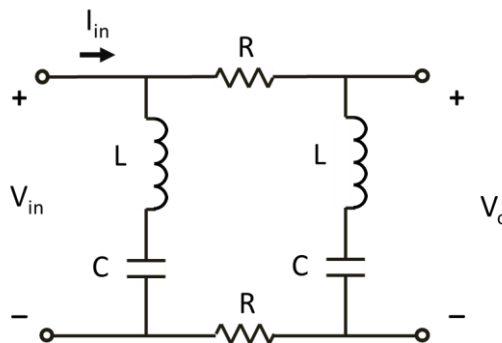Q2. Find the transfer functions  $H(s) = \frac{V_o(s)}{V_{in}(s)}$  and  $R(s) = \frac{V_o(s)}{I_{in}(s)}$ .




Q3. Sketch the Bode plots of

$$H(s) = \frac{10^6 s}{s^2 + 10010s + 10^5}$$


Q4. Sketch the Bode plots of

$$H(s) = \frac{10^4}{\frac{s^2}{10} + 200s + 10^5}$$

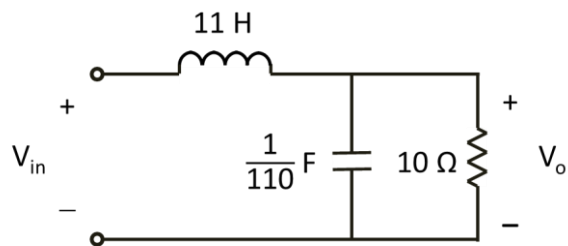Q5. Find the transfer function  $H(s) = \frac{V_o(s)}{V_{in}(s)}$  and sketch the Bode plots of  $H(s)$ .



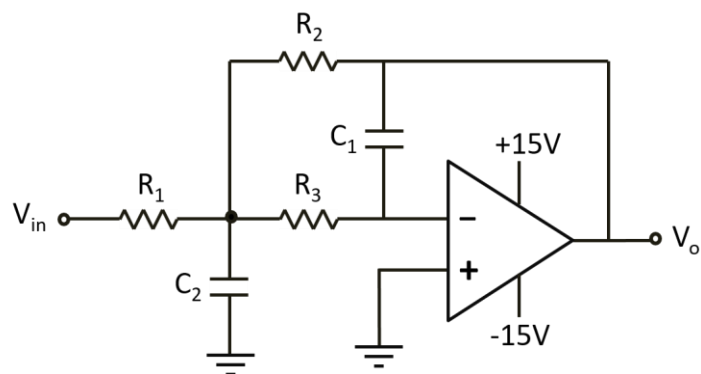Q6. Find the transfer function  $H(s) = \frac{V_o(s)}{V_{in}(s)}$ . What type of filter is this? What is the order?



- Q7. Find the transfer function  $H(s) = \frac{V_o(s)}{V_{in}(s)}$ . Sketch the Bode plots for the case  $R_1 = R_2 = 1 \text{ k}\Omega$  and  $C = 1 \text{ }\mu\text{F}$ . What type of filter is this? What is the order?

