



HOMework 1

Issued on Sept 19, 2021 (Sunday)

Due on Oct 4, 2021 (Monday, 11:59pm)

Submit your homework online <https://canvas.ust.hk>

Do not do your work on the question papers. Use separate blank papers

- Q1. Determine the power consumed by each circuit element (P_A , P_B , P_C , P_D , P_E and P_F), respectively, and specify whether each circuit component is supplying power or absorbing power (dissipated power) shown in Fig. 1 and Fig. 2.

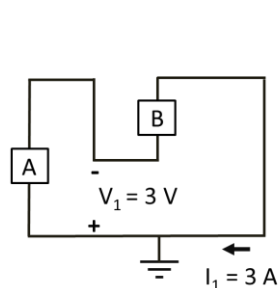


Fig. 1

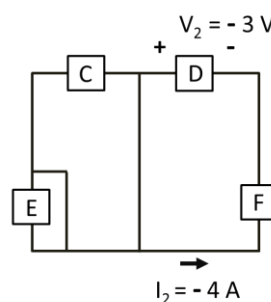


Fig. 2

- Q2. Find the resistance R_{AB} between node A and node B in the circuit shown in Fig. 3.

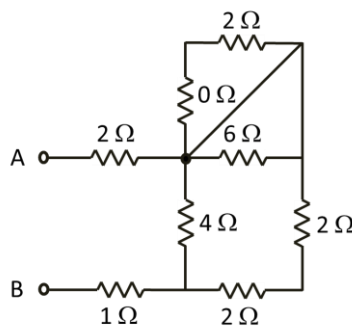


Fig. 3

- Q3. Find I_1 , V_1 and V_2 for the circuit shown in Fig. 4.

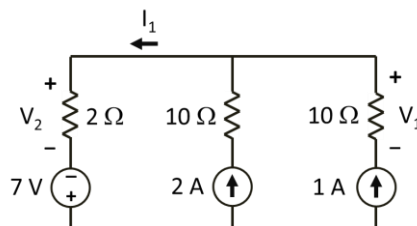


Fig. 4

Q4. Use superposition to find I_1 and V_1 in Fig. 5.

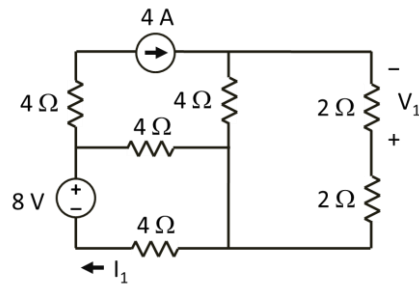


Fig. 5

Q5. Use nodal analysis to find V_1 in the circuit shown in Fig. 6.

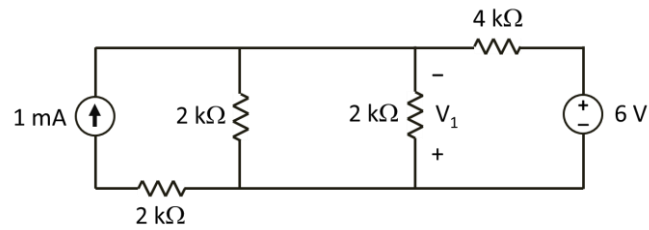


Fig. 6

Q6. Use source transformation(s) to find V_1 and I_1 in Fig. 7.

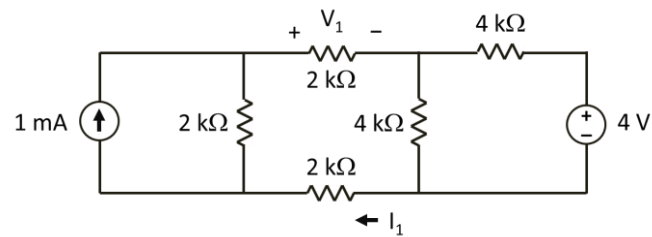


Fig. 7

Q7. Find V_1 and I_1 in Fig. 8.

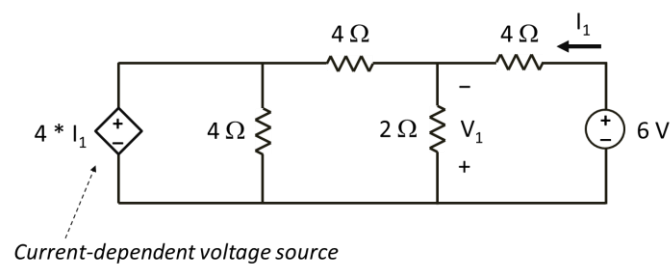


Fig. 8

- Q8. Determine the power consumed by each circuit element in Fig. 9. Specify whether each circuit component is supplying or absorbing power (dissipating power), and show the power balance.

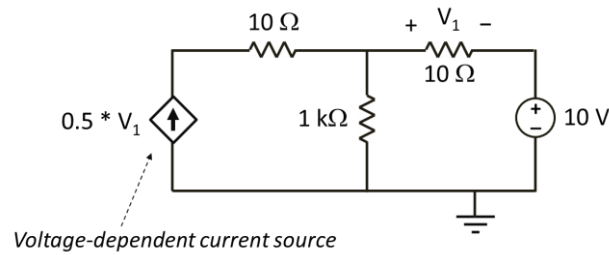


Fig. 9

- Q9. Find and draw the Norton's equivalent circuit with respect to terminals a, b in Fig. 10.

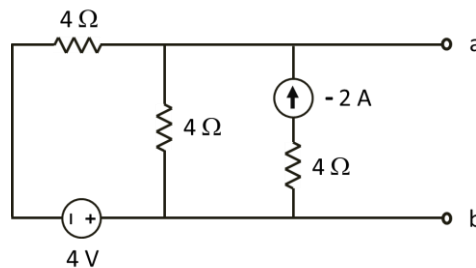


Fig. 10

- Q10. Use the Norton's equivalent circuit in Q9 to find V_1 in Fig. 11.

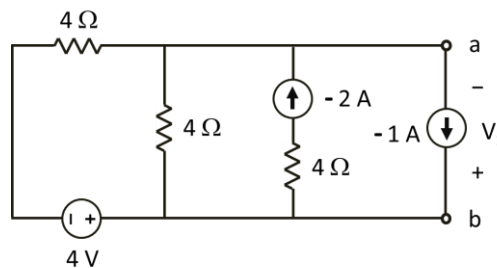


Fig. 11

- Q11. Use the Norton's equivalent circuit in Q9 to find and draw the Thevenin's equivalent circuit with respect to terminals a, b in Fig. 12.

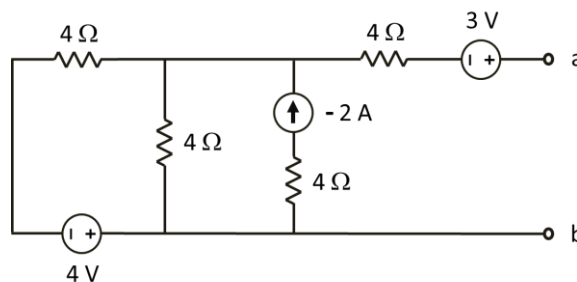


Fig. 12