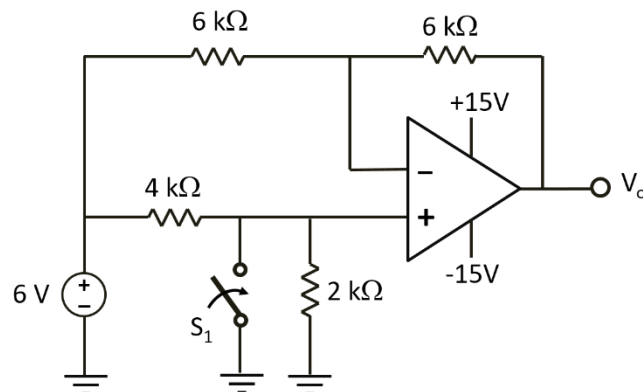




HOMEWORK 3 SOLUTION

Q1. Assuming ideal op amp, find the voltage V_o , (a) when the switch, S_1 , is open, and (b) when S_1 is closed.



(a) With S_1 open, assume op amp not saturated,

$$V_+ = 6 \left(\frac{2k}{4k + 2k} \right) = 2 \text{ V} = V_-$$

Apply KCL at V_- ,

$$\frac{V_o - V_-}{6k} = \frac{V_- - 6}{6k}$$

$$V_o = 2V_- - 6 = 4 - 6 = -2 \text{ V}$$

(b) With S_1 closed, assume op amp not saturated,

$$V_+ = 0 \text{ V} = V_-$$

This time,


$$V_o = 2V_- - 6 = 0 - 6 = -6 \text{ V}$$

Q2. Assuming ideal op amp,

(a) Find the expression for V_o as a function of V_1 and V_2 .

(b) Find V_o when $V_1 = 4 \text{ V}$, $V_2 = 4 \text{ V}$.

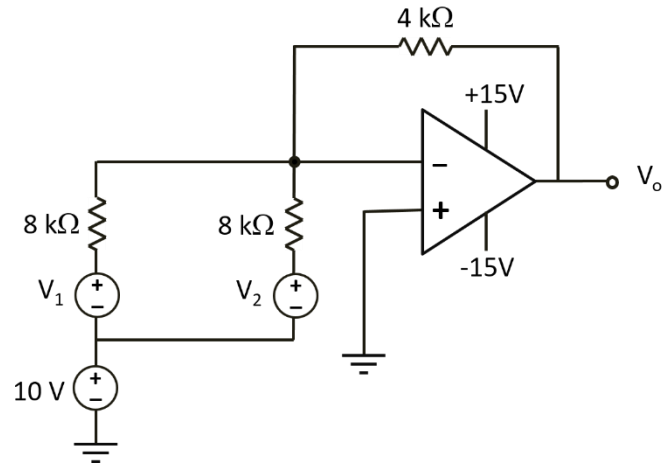(c) Find V_o when $V_1 = 4 \text{ V}$, $V_2 = 8 \text{ V}$.



(a) Assume op amp not saturated,

$$V_- = V_+ = 0 \text{ V}$$

Apply KCL at V_- ,

$$\frac{V_o - V_-}{4k} = \frac{V_- - V_1 - 10}{8k} + \frac{V_- - V_2 - 10}{8k}$$

$$2V_o = -(V_1 + V_2 + 20)$$

$$V_o = -\frac{V_1 + V_2}{2} - 10$$

(b)


$$V_o = -\frac{4 + 4}{2} - 10 = -14 \text{ V}$$

(c)

$$V_o = -\frac{4 + 8}{2} - 10 = -16 \text{ V}$$

However, this is lower than the -15-V power supply. In reality, the op amp will be saturated around -15 V .

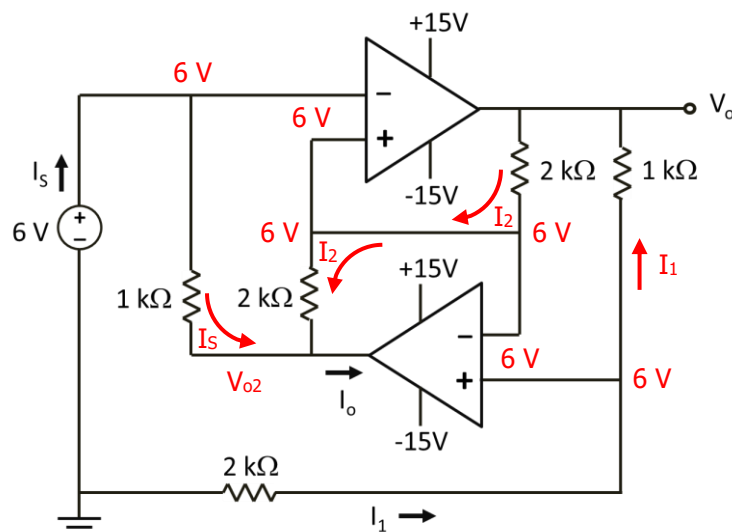Q3. Find I_1 , I_S , I_o and V_o assuming ideal op amps.



Assume op amps not saturated, their inputs are all at 6 V. Furthermore, the op amps take no input currents. We start by marking all the known voltages and main current flows in the circuit diagram above.

Notice that I_1 can be computed by the voltage across the bottom 2-k Ω resistor as follows

$$I_1 = -\frac{6}{2k} = -3 \text{ mA}$$

Next,

$$V_o = -I_1(2k + 1k) = 9 \text{ V}$$

From which

$$I_2 = \frac{V_o - 6}{2k} = 1.5 \text{ mA}$$

Hence,

$$V_{o2} = 6 - I_2 \times 2k = 3 \text{ V}$$

Therefore,


$$I_s = \frac{6 - V_{o2}}{1k} = 3 \text{ mA}$$

Finally,

$$I_o = I_s + I_2 = 4.5 \text{ mA}$$

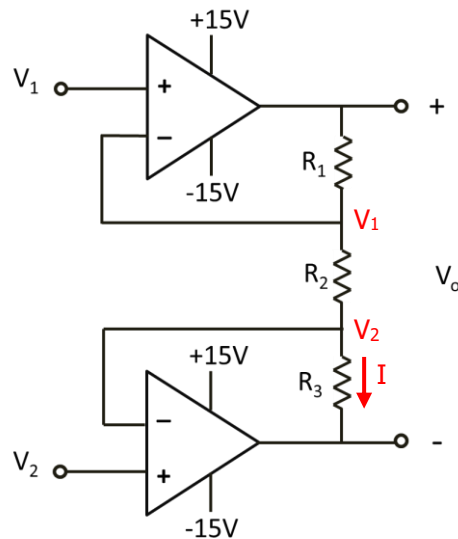Q4. Assuming ideal op amps,

- Find the expression for V_o as a function of V_1 and V_2 .
- Find V_o when $V_1 = 3 \text{ V}$, $V_2 = 4 \text{ V}$, $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$.



- We start by marking all the known voltages and the main current flow in the circuit diagram above. Assume op amps not saturated.

Note that

$$I = \frac{V_1 - V_2}{R_2}$$



Therefore,

$$V_o = I(R_1 + R_2 + R_3) = \left(\frac{R_1 + R_2 + R_3}{R_2} \right) (V_1 - V_2)$$

(b) When $V_1 = 3 \text{ V}$, $V_2 = 4 \text{ V}$, $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$,

$$V_o = \left(\frac{1\text{k} + 1\text{k} + 1\text{k}}{1\text{k}} \right) (3 - 4) = -3 \text{ V}$$

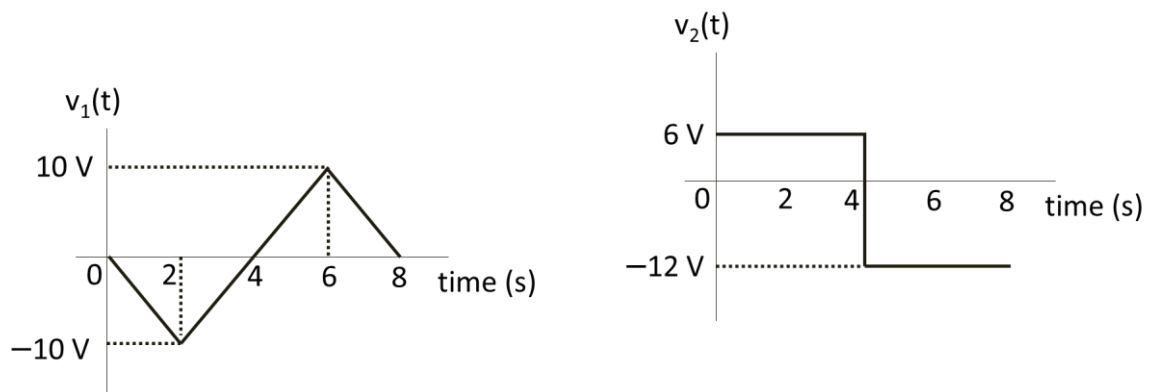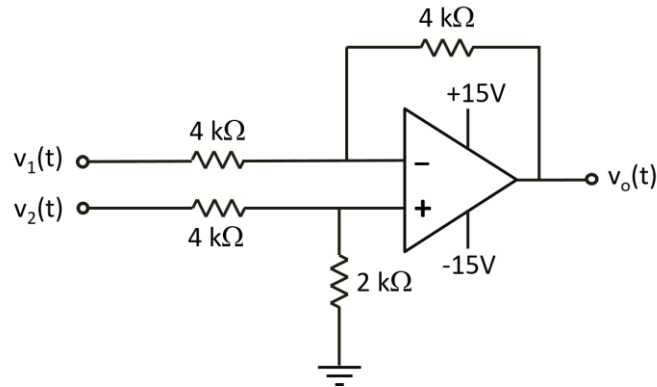Q5. Plot the waveform of $v_o(t)$ assuming ideal op amp.



Assume op amp not saturated,


$$v_+ = \left(\frac{2\text{k}}{4\text{k} + 2\text{k}} \right) v_2 = \frac{v_2}{3} = v_-$$

Apply KCL to node v_- ,


$$\frac{v_o - v_-}{4\text{k}} = \frac{v_- - v_1}{4\text{k}}$$

$$v_o = 2v_- - v_1 = \frac{2v_2}{3} - v_1$$

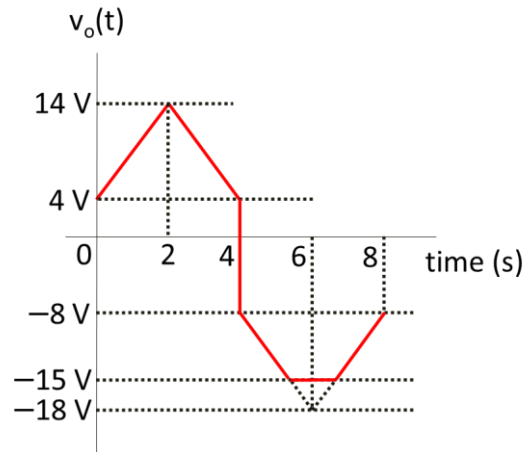The $v_o(t)$ waveform is plotted below. Notice that the op amp reaches saturation and $v_o(t)$ is railed at around -15 V during part of the second phase.



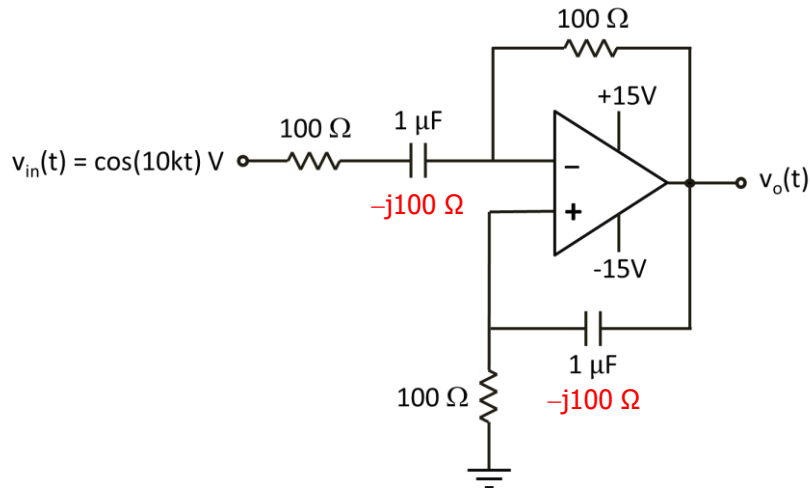Q6. Assuming ideal op amp, find $v_o(t)$.



At $\omega = 10\text{k rad/s}$, the impedance of the capacitors $= \frac{1}{j10\text{k} \times 1\mu} = -j100 \Omega$.

The bottom resistor and capacitor form a voltage divider. Assume op amp not saturated,

$$V_+ = \left(\frac{100}{100 - j100} \right) V_o = \left(\frac{1}{1 - j} \right) V_o = \left(\frac{1 + j}{2} \right) V_o = V_- \quad (1)$$

Apply KCL to node V_- ,

$$\frac{V_{in} - V_-}{100 - j100} = \frac{V_- - V_o}{100}$$

$$V_{in} = (1 - j)(V_- - V_o) + V_- = (2 - j)V_- - (1 - j)V_o$$

Substituting (1),

$$\begin{aligned} V_{in} &= \frac{(2 - j)(1 + j)}{2} V_o - (1 - j)V_o = \left(\frac{2 + 1 - j + j2 - 2 + j2}{2} \right) V_o = \left(\frac{1 + j3}{2} \right) V_o \\ &= (0.5 + j1.5)V_o = 1.581 \angle 71.57^\circ \times V_o \end{aligned}$$


Hence,

$$V_o = \frac{V_{in}}{1.581 \angle 71.57^\circ} = 0.632 \angle (-71.6^\circ) \times 1 \angle 0^\circ = 0.632 \angle (-71.6^\circ)$$

Finally,

$$v_o(t) = 0.632 \cos(10kt - 71.6^\circ) \text{ V}$$

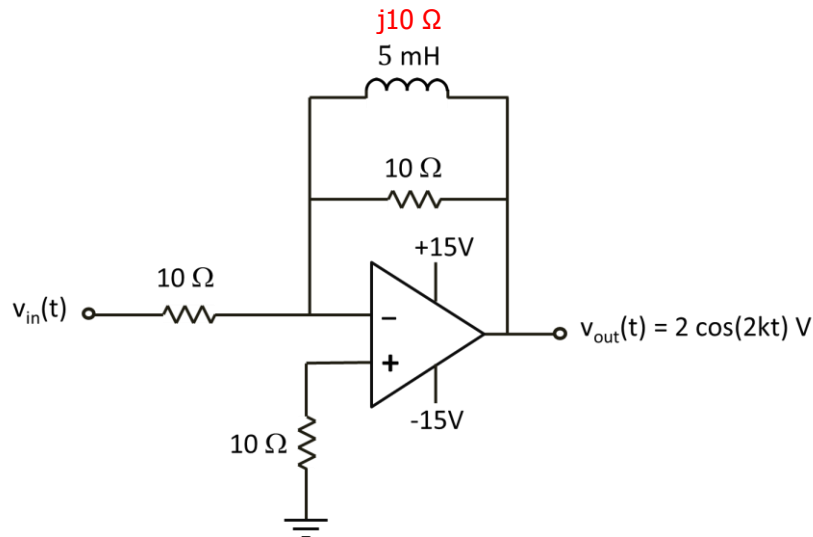Q7. Assuming ideal op amp, find $v_{in}(t)$.



At $\omega = 2k \text{ rad/s}$, the impedance of the inductor $= j2k \times 5m = j10 \Omega$.

V_+ is at 0 V ground. The presence of the 10- Ω resistor doesn't matter because there is no current going through it for an ideal op amp. (For a non-ideal op amp, the resistor could be used to balance out the tiny input bias currents.) Assume op amp not saturated,

$$V_- = V_+ = 0 \text{ V}$$

Apply KCL to node V_- ,

$$\frac{V_{in} - V_-}{10} = \frac{V_- - V_{out}}{10 \parallel j10}$$

$$\frac{V_{in} - 0}{10} = \frac{0 - V_{out}}{\frac{j100}{10 + j10}} = -\left(\frac{1 + j}{j10}\right) V_{out}$$

$$V_{in} = j(1 + j)V_{out} = \angle 90^\circ(\sqrt{2} \angle 45^\circ)V_{out} = 1.414 \angle 135^\circ \times 2 \angle 0^\circ$$

Hence,

$$v_{in}(t) = 2.82 \cos(2kt + 135^\circ) \text{ V}$$