




ELEC1100 - Tutorial 2

Diodes & DC Regulation


Introduction to Lab#02

Review

Power Sources in Physical Lab

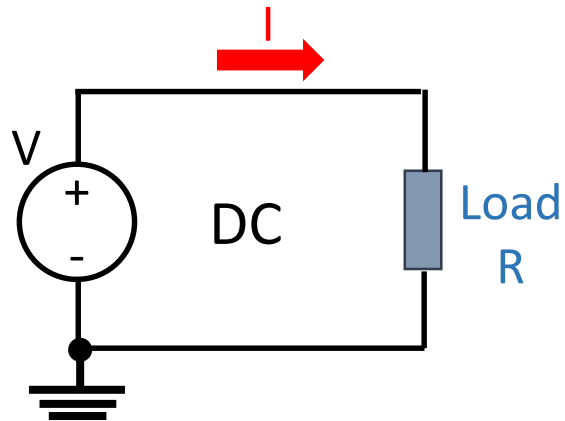


DC power supply

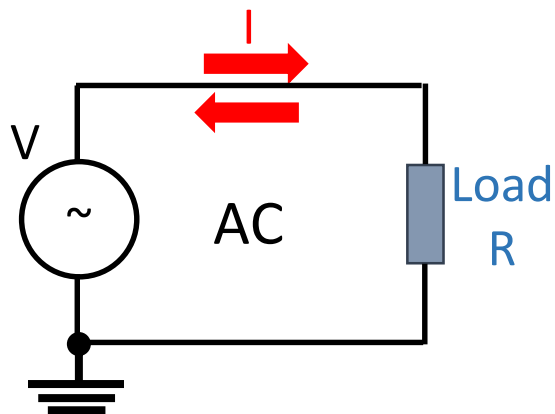

Signal generator


Draw waveforms

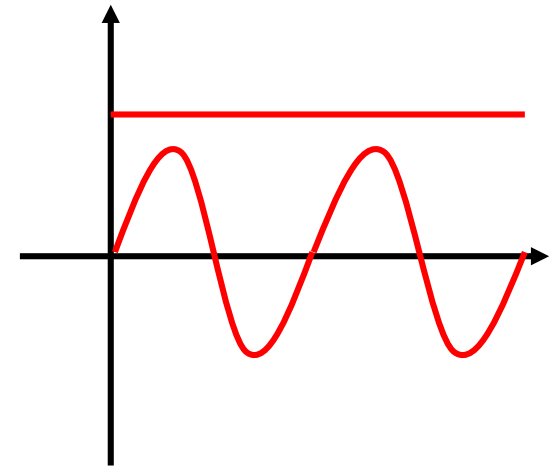

Review


❖ Generate a Sine wave in Tinkercad

[Lab#02_S1]


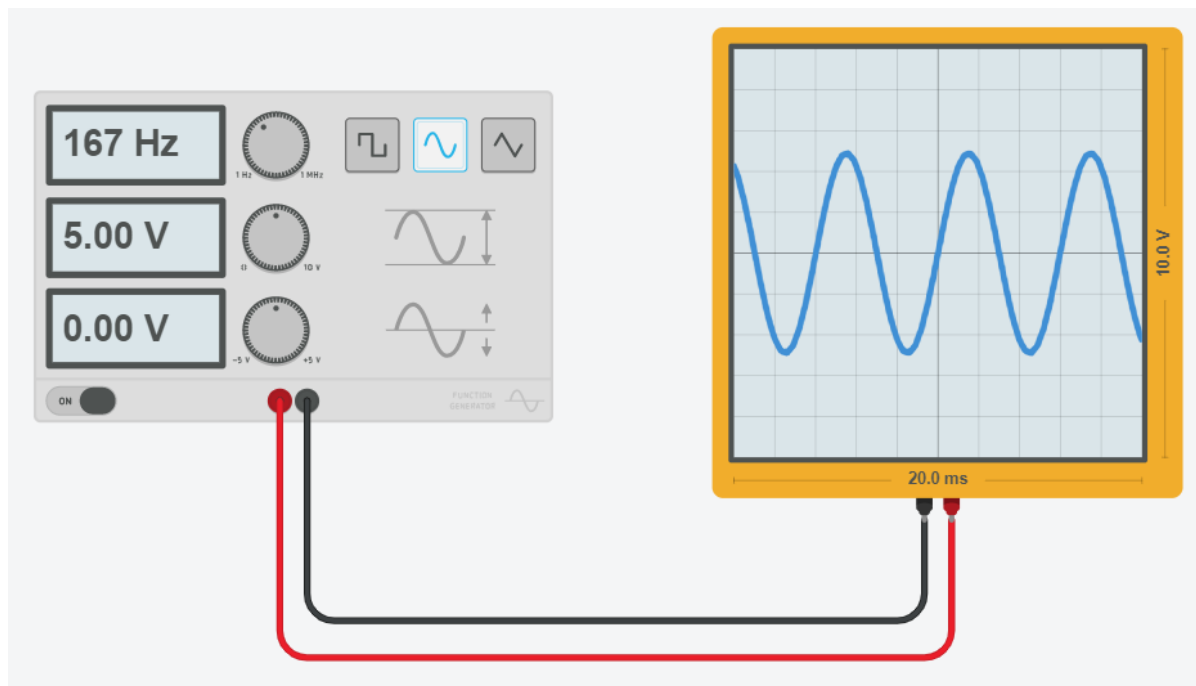


Diode Circuit


❖ Regular diode

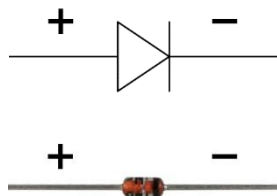

Black Strip is Negative

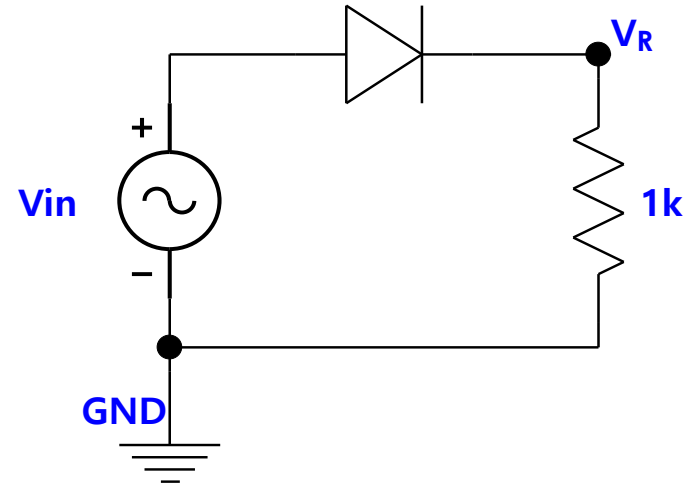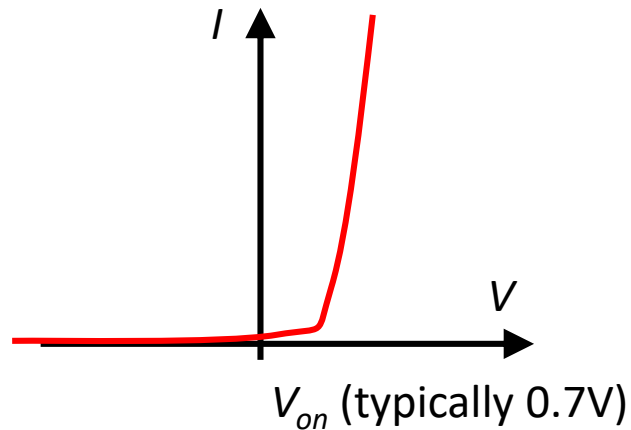


10Vpp, 1kHz

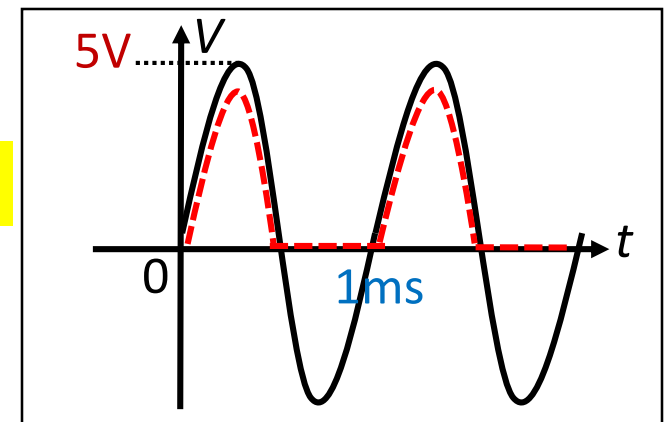

Diode Circuit in Tinkercad

[Lab#02_S2]

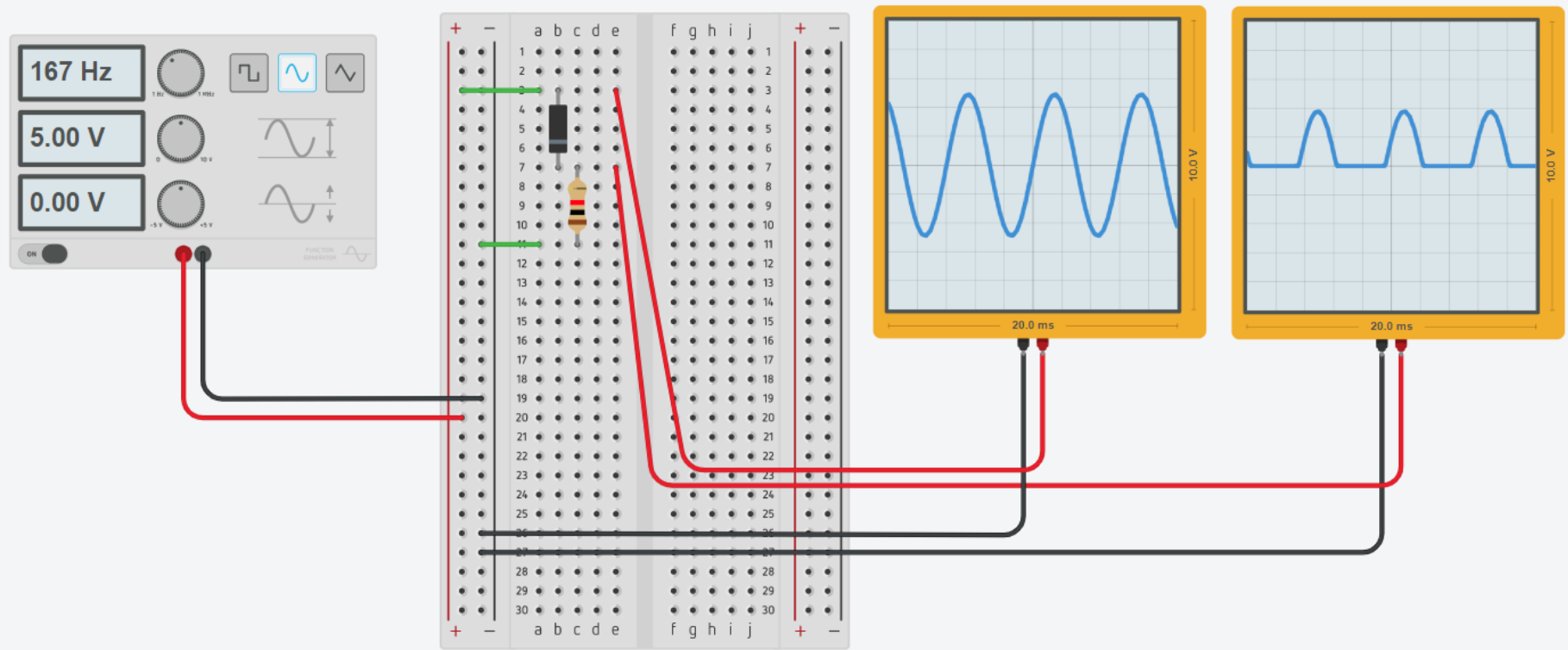


DC to DC Conversion


❖ When do you need DC to DC?

Eg. Your phone needs 9V to operate, but the motion sensor only needs 5V; you don't want to insert two batteries!

Version I: Zener Diode

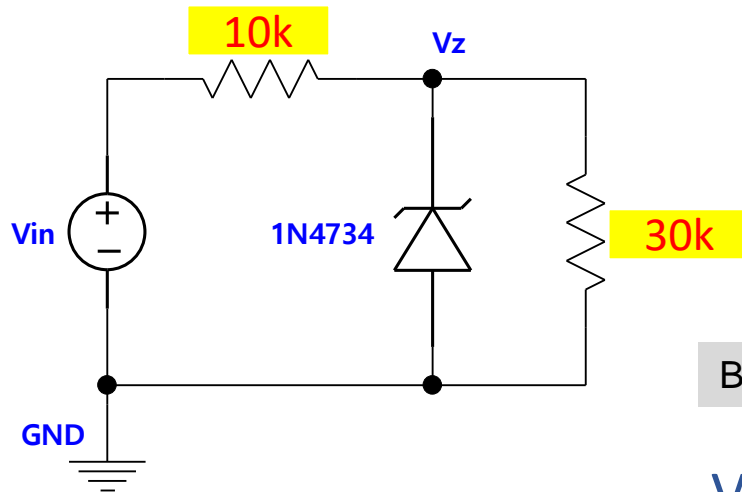


Zener diode

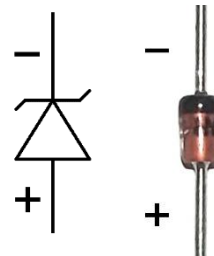


Black Strip is Negative

$$V_z = V_{bd} \approx -5.7V$$

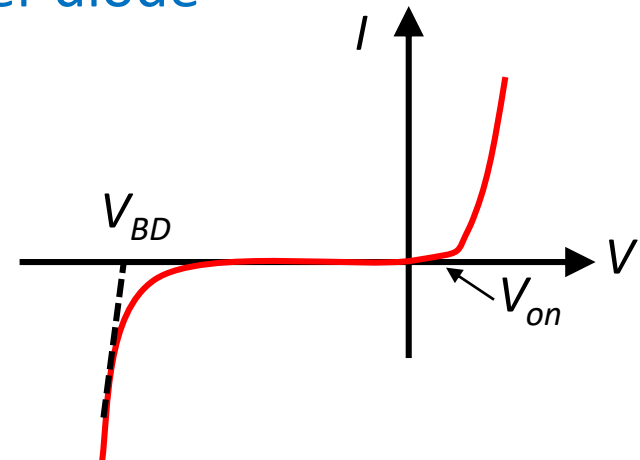

Zener Diode Circuit in Tinkercad



[Lab#02_S3]

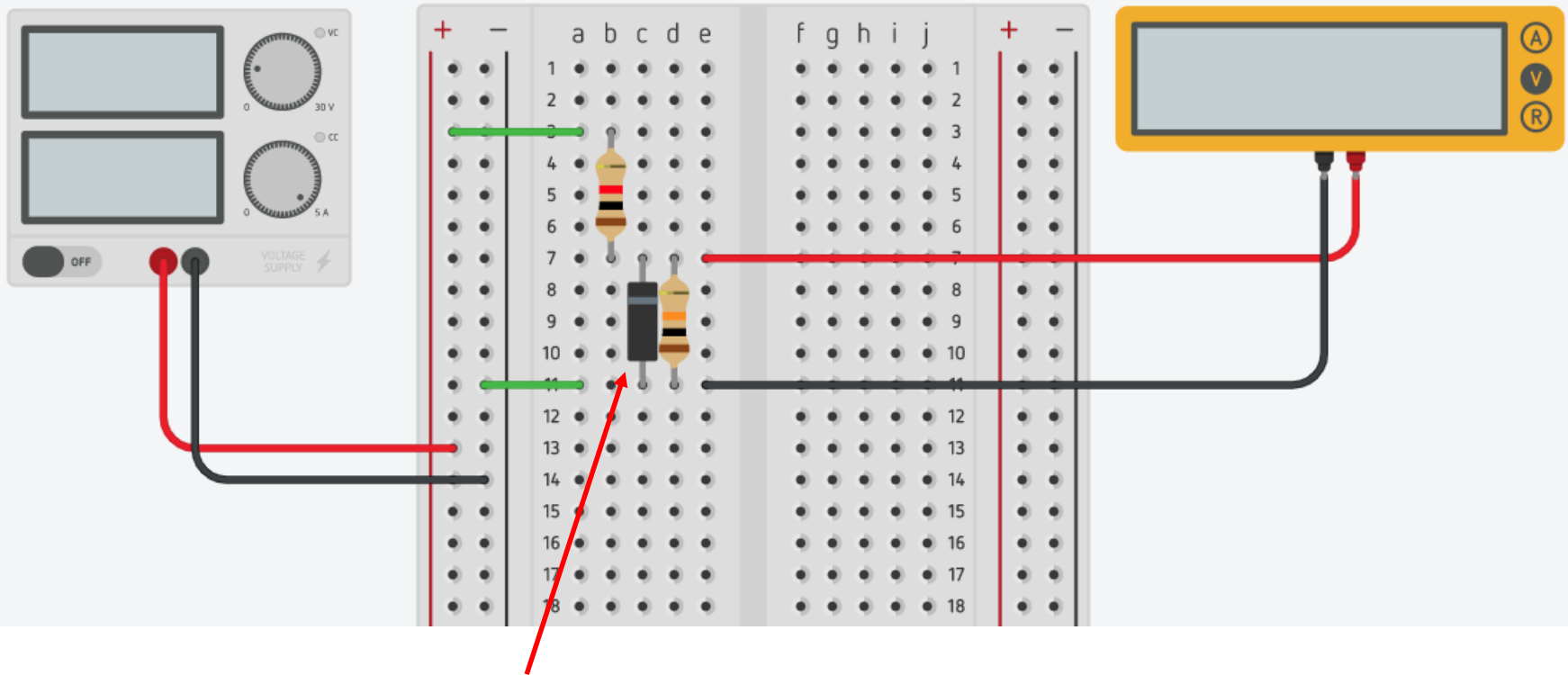


Notice the polarity of Zener diode

DC to DC Conversion

Version II: Voltage Regulator LM7805

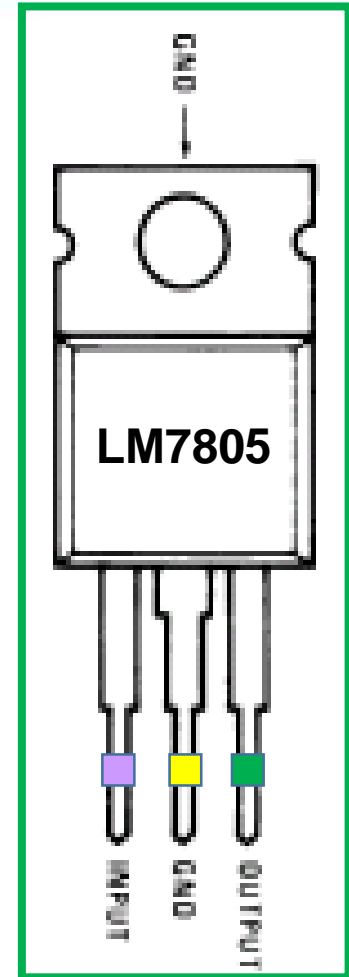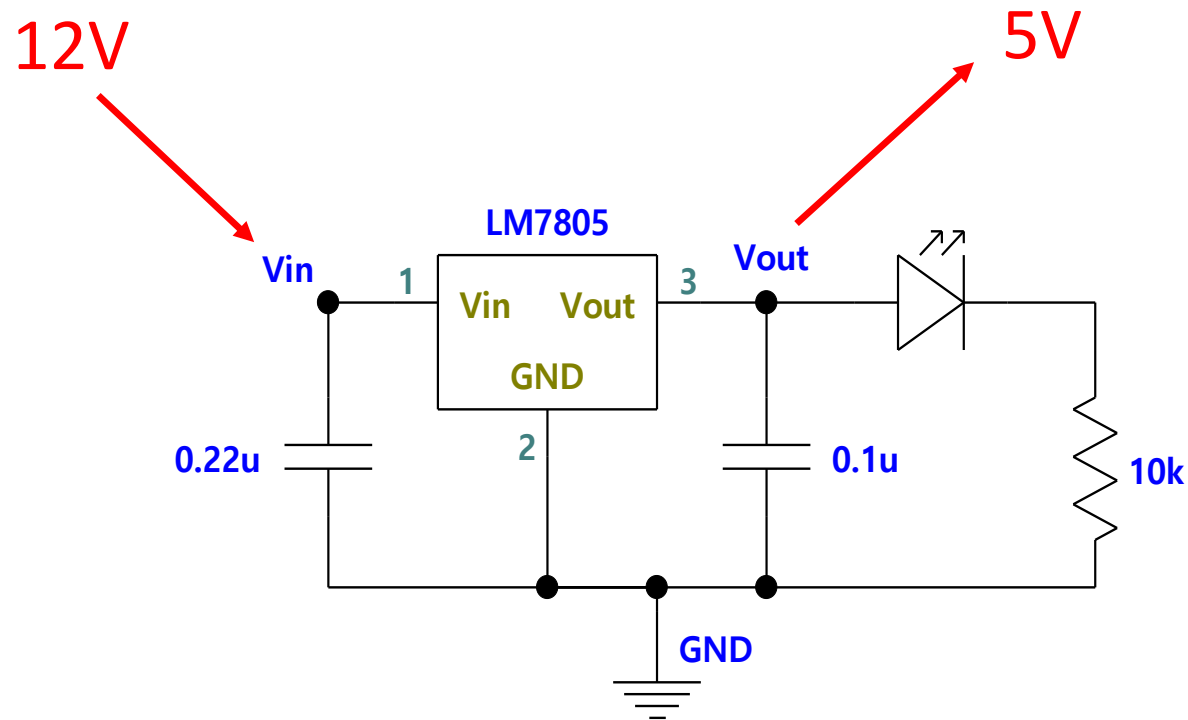

Regulator Circuit in Tinkercad

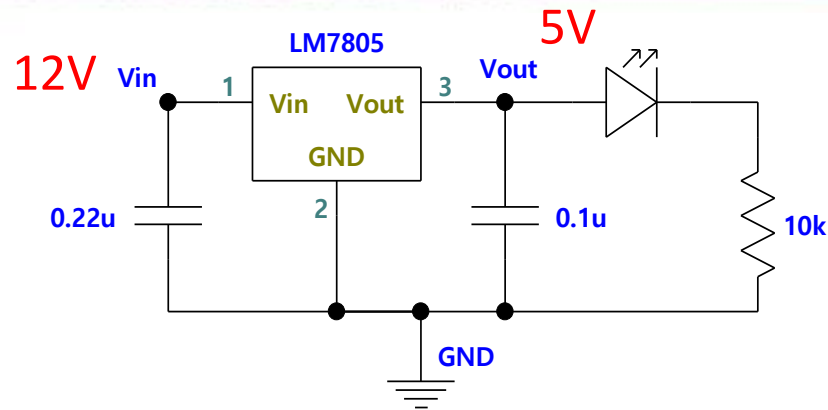

[Lab#02_S4]

