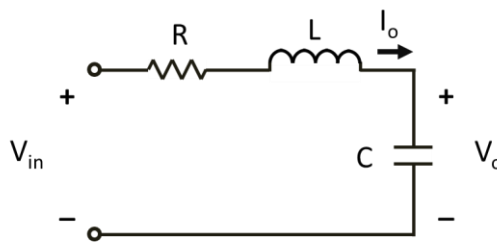




HOMEWORK 4 SOLUTION

Assume ideal op amp in all cases.

Q1. Find the transfer functions $H(s) = \frac{V_o(s)}{V_{in}(s)}$ and $G(s) = \frac{I_o(s)}{V_{in}(s)}$.



$$I_o = \frac{V_{in}}{R + sL + \frac{1}{sC}} = \frac{sC}{s^2LC + sCR + 1} V_{in}$$

Hence


$$G(s) = \frac{I_o(s)}{V_{in}(s)} = \frac{sC}{s^2LC + sCR + 1}$$

$$V_o = \frac{I_o}{sC} = \left(\frac{sC}{s^2LC + sCR + 1} V_{in} \right) \frac{1}{sC} = \frac{1}{s^2LC + sCR + 1} V_{in}$$

Hence

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s^2LC + sCR + 1}$$

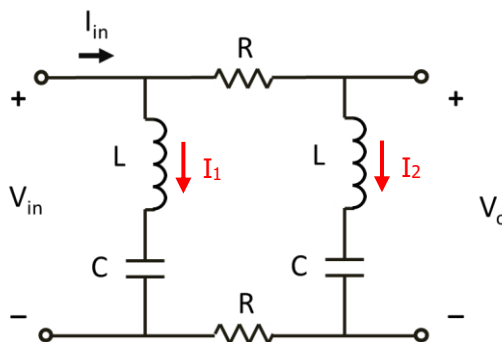Q2. Find the transfer functions $H(s) = \frac{V_o(s)}{V_{in}(s)}$ and $R(s) = \frac{V_o(s)}{I_{in}(s)}$.



The R, L, C and R are connected in series on the right. They form a voltage divider in which

$$V_o = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC} + R} V_{in} = \frac{s^2LC + 1}{s^2LC + 2sCR + 1} V_{in} \quad (1)$$

Hence,

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{s^2LC + 1}{s^2LC + 2sCR + 1}$$

Since

$$I_1 = \frac{V_{in}}{sL + \frac{1}{sC}} = \frac{sC}{s^2LC + 1} V_{in}$$

and

$$I_2 = \frac{V_{in}}{R + sL + \frac{1}{sC} + R} = \frac{sC}{s^2LC + 2sCR + 1} V_{in}$$

Therefore,

$$\begin{aligned} I_{in} &= I_1 + I_2 = \frac{sC}{s^2LC + 1} V_{in} + \frac{sC}{s^2LC + 2sCR + 1} V_{in} \\ I_{in} &= \frac{2sC(s^2LC + sCR + 1)}{(s^2LC + 1)(s^2LC + 2sCR + 1)} V_{in} \end{aligned} \quad (2)$$

(1) ÷ (2),

$$\begin{aligned} R(s) &= \frac{V_o(s)}{I_{in}(s)} = \left(\frac{s^2LC + 1}{s^2LC + 2sCR + 1} \right) \frac{(s^2LC + 1)(s^2LC + 2sCR + 1)}{2sC(s^2LC + sCR + 1)} \\ &= \frac{(s^2LC + 1)^2}{2sC(s^2LC + sCR + 1)} \quad (4^{\text{th}} \text{ order system}) \end{aligned}$$

Q3. Sketch the Bode plots of

$$H(s) = \frac{10^6 s}{s^2 + 10010s + 10^5} = \frac{10^6 s}{(s + 10)(s + 10000)} = \frac{10s}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{10000}\right)}$$


There is a zero at $s = 0$ corresponding to $\omega = 0$ rad/s.

There are two poles at $s = -10, -10000$ corresponding to $\omega = 10, 10000$ rad/s.

At sufficiently low frequencies, $H(j\omega) \approx j10\omega$ with a 90° phase.

When $\omega = 0.1$ rad/s, $H(j\omega) = H(j0.1) \approx j$ with a magnitude $\approx 1 = 0$ dB. This is the point the magnitude plot should pass through.

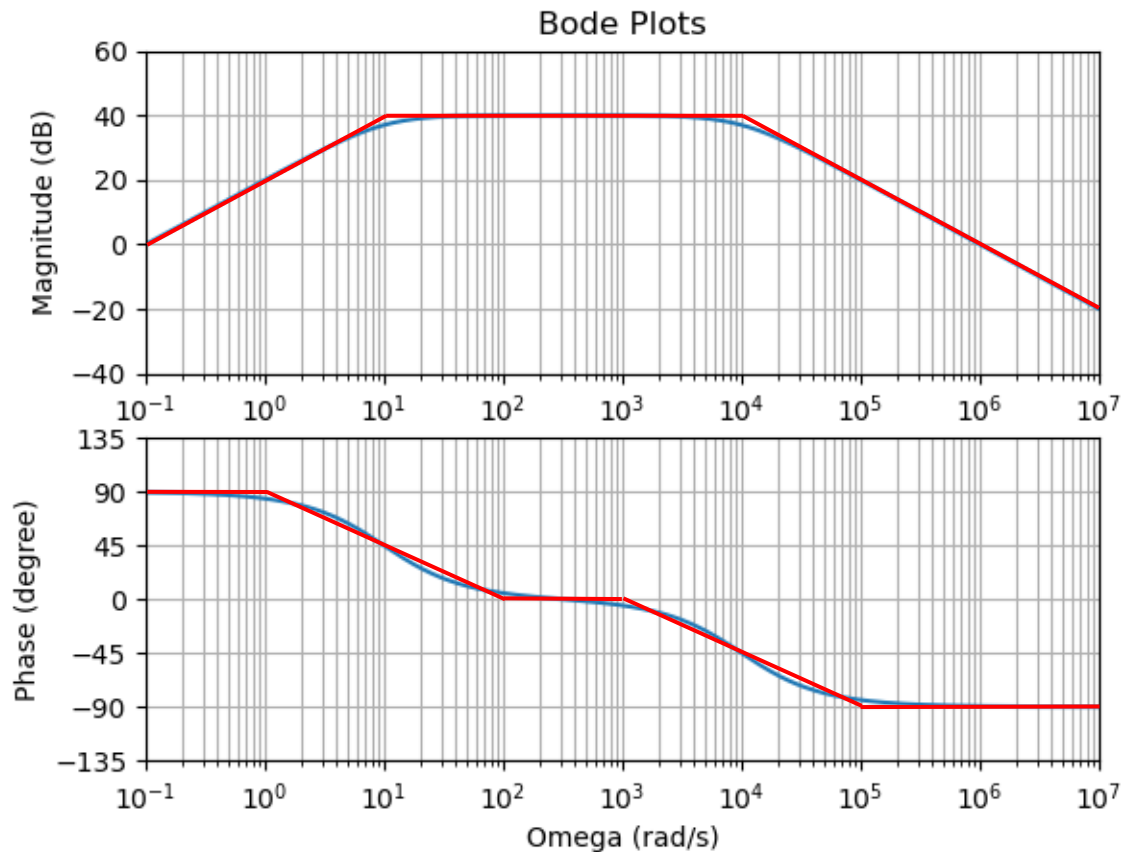The Bode plots are as shown below. Only the red sketches are required. The blue computer-generated plots are for your reference.




Q4. Sketch the Bode plots of

$$\begin{aligned}
 H(s) &= \frac{10^4}{\frac{s^2}{10} + 200s + 10^5} = \frac{10^5}{s^2 + 2000s + 10^6} \\
 &= \frac{10^5}{(s + 1000)(s + 1000)} = \frac{0.1}{\left(1 + \frac{s}{1000}\right)\left(1 + \frac{s}{1000}\right)}
 \end{aligned}$$


DC magnitude = $20 \log_{10} 0.1 = -20$ dB.

There are two identical poles at $s = -1000$ corresponding to $\omega = 1000$ rad/s. Their combined effects are two times that for a single pole at the same location. Hence, the magnitude roll-off is -40 dB/dec beyond 1000 rad/s and the phase shift is -90° /dec centered at 1000 rad/s.

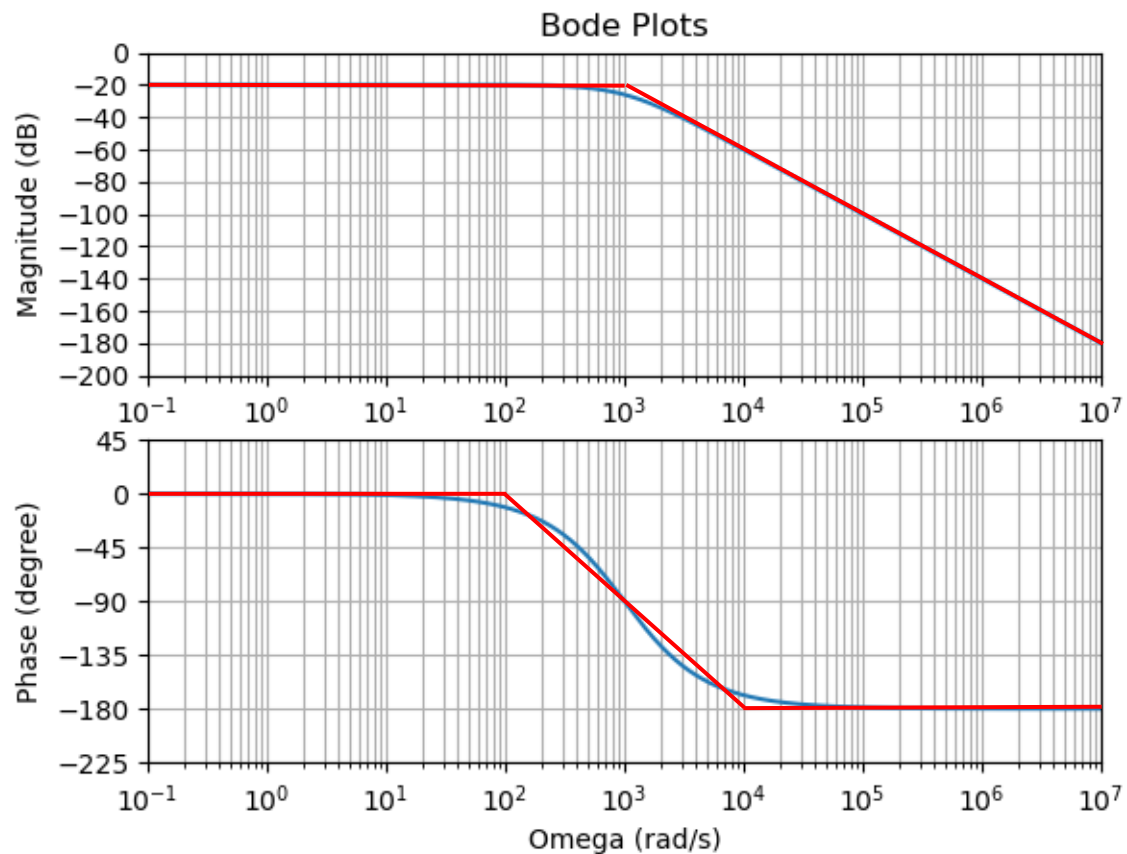The Bode plots are as shown below. Only the red sketches are required. The blue computer-generated plots are for your reference.



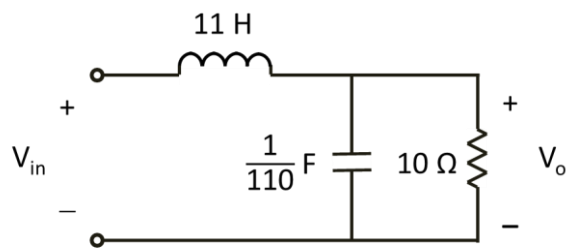Q5. Find the transfer function $H(s) = \frac{V_o(s)}{V_{in}(s)}$ and sketch the Bode plots of $H(s)$.



First,

$$R \parallel \left(\frac{1}{sC} \right) = \frac{\frac{R}{sC}}{R + \frac{1}{sC}} = \frac{R}{sCR + 1}$$

Now,


$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{R \parallel \left(\frac{1}{sC} \right)}{sL + R \parallel \left(\frac{1}{sC} \right)} = \frac{\frac{R}{sCR + 1}}{sL + \frac{R}{sCR + 1}} = \frac{R}{s^2 LCR + sL + R}$$

$$= \frac{10}{s^2 11 \left(\frac{1}{110} \right) 10 + s 11 + 10} = \frac{10}{s^2 + s 11 + 10} = \frac{10}{(s + 1)(s + 10)} = \frac{1}{\left(1 + \frac{s}{1}\right)\left(1 + \frac{s}{10}\right)}$$


DC magnitude = 1 = 0 dB.

There are two poles at $s = -1, -10$ corresponding to $\omega = 1, 10$ rad/s.

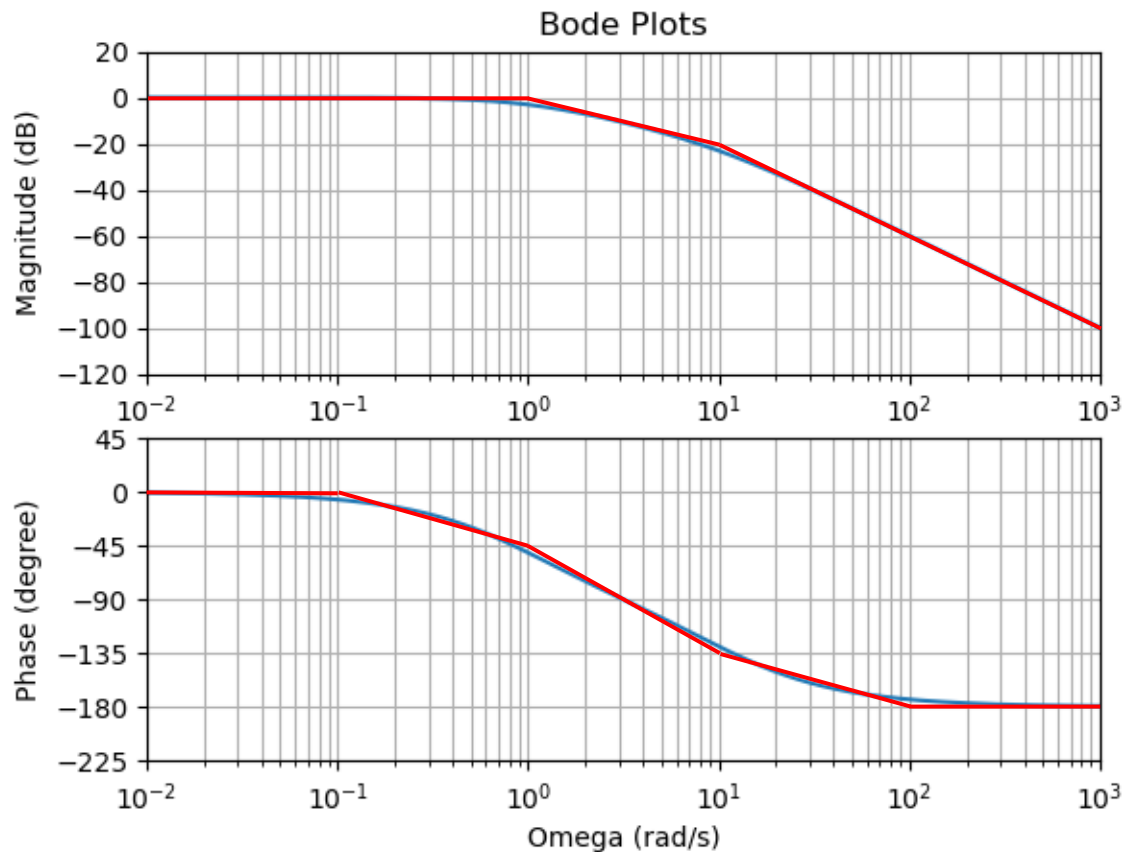The Bode plots are as shown below. Only the red sketches are required. The blue computer-generated plots are for your reference.



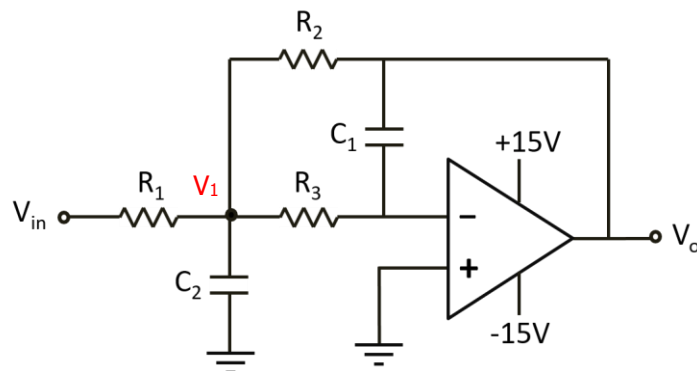Q6. Find the transfer function $H(s) = \frac{V_o(s)}{V_{in}(s)}$. What type of filter is this? What is the order?



Assume op amp not saturated,

$$V_+ = 0 = V_-$$

Apply KCL at node V_- ,

$$\frac{V_1 - V_-}{R_3} = \frac{V_- - V_o}{\frac{1}{sC_1}}$$

$$\frac{V_1 - 0}{R_3} = sC_1(0 - V_o)$$

$$V_1 = -sC_1R_3V_o \quad (1)$$

Apply KCL at node V_1 ,

$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_o}{R_2} + \frac{V_1}{\frac{1}{sC_2}} + \frac{V_1}{R_3}$$

$$\frac{V_{in}}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_1 + sC_2V_1 - \frac{V_o}{R_2}$$

$$R_2R_3V_{in} = (R_1R_2 + R_2R_3 + R_3R_1 + sC_2R_1R_2R_3)V_1 - R_1R_3V_o$$

Substituting (1),


$$R_2R_3V_{in} = -(R_1R_2 + R_2R_3 + R_3R_1 + sC_2R_1R_2R_3)sC_1R_3V_o - R_1R_3V_o$$

Hence,

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = -\frac{R_2R_3}{s^2C_1C_2R_1R_2R_3^2 + sC_1R_3(R_1R_2 + R_2R_3 + R_3R_1) + R_1R_3}$$

There are two poles and no zeros. This is a **second-order low-pass filter**.

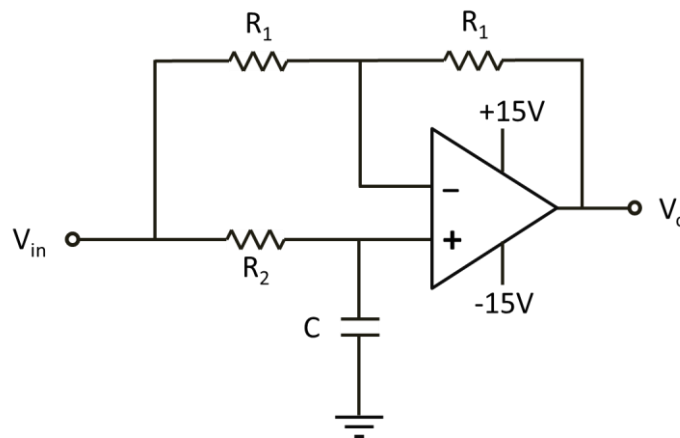- Q7. Find the transfer function $H(s) = \frac{V_o(s)}{V_{in}(s)}$. Sketch the Bode plots for the case $R_1 = R_2 = 1 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$. What type of filter is this? What is the order?



It can be easily seen that

$$V_- = \frac{V_{in} + V_o}{2} \quad (1)$$

R_2 and C form a voltage divider in which

$$V_+ = \frac{\frac{1}{sC}}{R_2 + \frac{1}{sC}} V_{in} = \frac{1}{sCR_2 + 1} V_{in} \quad (2)$$

Equate (1) and (2),

$$\begin{aligned} \frac{V_{in} + V_o}{2} &= \frac{1}{sCR_2 + 1} V_{in} \\ V_o &= \frac{2}{sCR_2 + 1} V_{in} - V_{in} = \frac{1 - sCR_2}{1 + sCR_2} V_{in} \end{aligned}$$

Therefore,

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1 - sCR_2}{1 + sCR_2}$$

There is a zero at $s = \frac{1}{CR_2}$ and a pole at $s = -\frac{1}{CR_2}$, both corresponding to the **same corner frequency** $\omega = \frac{1}{CR_2}$, which is the frequency at which $|\pm sCR_2| = 1$, where $s = j\omega$.

Since the corner frequencies coincide, the effects of the zero and pole on the magnitude exactly cancel each other:

$$|H(j\omega)| = \frac{|1 - j\omega CR_2|}{|1 + j\omega CR_2|} = \frac{\sqrt{1 + (-\omega CR_2)^2}}{\sqrt{1 + (\omega CR_2)^2}} = 1 = \text{constant}$$

However, their effects on the phase are combined:

$$\begin{aligned} \angle[H(j\omega)] &= \angle \left[\frac{1 - j\omega CR_2}{1 + j\omega CR_2} \right] = \angle(1 - j\omega CR_2) - \angle(1 + j\omega CR_2) \\ &= \tan^{-1}(-\omega CR_2) - \tan^{-1}(\omega CR_2) = -2\tan^{-1}(\omega CR_2) \end{aligned}$$

Moreover, it can be easily seen that $H(j0) = 1 = 1\angle 0^\circ$ and $H(j\infty) = -1 = 1\angle(\pm 180^\circ)$, but only $1\angle(-180^\circ)$ is correct because the phase decreases with frequency.

This is therefore a **first-order all-pass filter**.

The Bode plots for the case $R_1 = R_2 = 1 \text{ k}\Omega$ and $C = 1 \text{ }\mu\text{F}$ are shown below. An ideal all-pass filter passes all frequencies with a constant gain. The only effect is the frequency-dependent phase shift it introduces.

