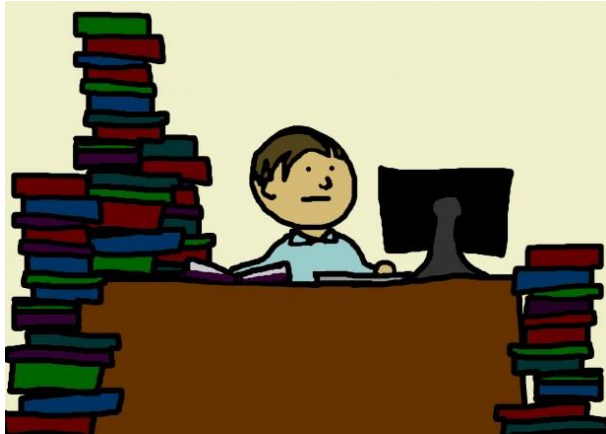


# **FSM 2 : Finite State Machines**

---

# Let's Try This Out...

---



Bob is stressed out as he has too many deadlines and isn't sleeping enough! He has decided to develop a FSM to regulate his time between sleeping and studying.

- When he is idle, there are two actions he can do next : SLEEP or STUDY.
- To prevent exhaustion, he buys a body exhaustion sensor and checks it every hour. When he is exhausted, the sensor output EX will be TRUE.
- When he is exhausted, he should sleep (SLEEP is TRUE). When he is not exhausted, he should study (STUDY is TRUE).
- Implement his FSM using D Flip Flops and gates.


# Step 1 : Block Diagram, STD

---

1) Block Diagram




2) State Transition Diagram

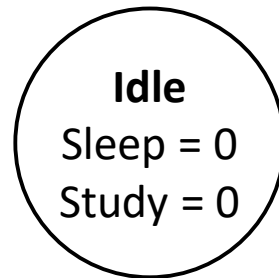

# Step 2 : Next State Table

State Transition Diagram

 

Current State Input Next State

S		S+

$S_1S_0$	EX	$S_1+S_0+$

State	$S_1S_0$
	00
	01
	10

# Step 2 : Next State Table

$S_1S_0$	EX	$S_1+S_0+$
0 0	0	1 0
0 0	1	0 1
0 1	0	1 0
0 1	1	0 1
1 0	0	1 0
1 0	1	0 1

$D_1 =$

$D_0 =$

$D_1$  :

$S_1S_0$	00	01	11	10
EX				
0				
1				

$S_1+ =$

$D_0$  :

$S_1S_0$	00	01	11	10
EX				
0				
1				


$S_0+ =$

\*Minimum area vs minimum risk implementations
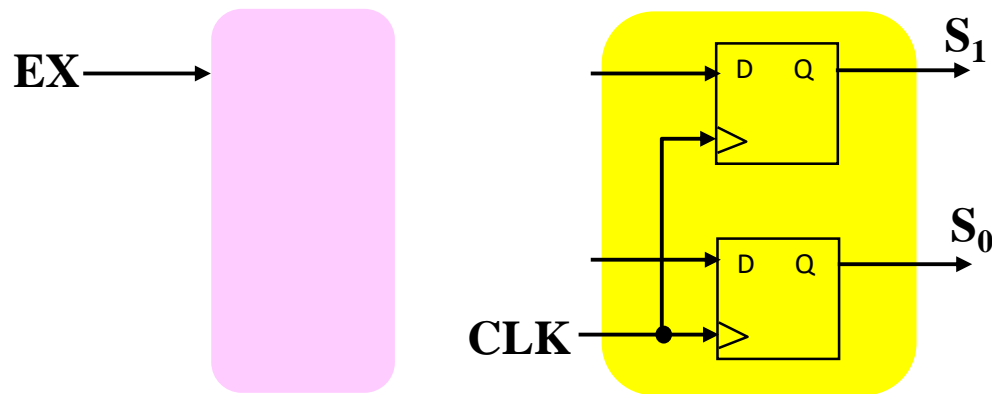
# Step 2 : Next State Table


---

If the state assignments were to change, would the next state logic change?



# Step 3 : Output Logic


State	$S_1S_0$
IDLE	00
SLEEP	01
STUDY	10

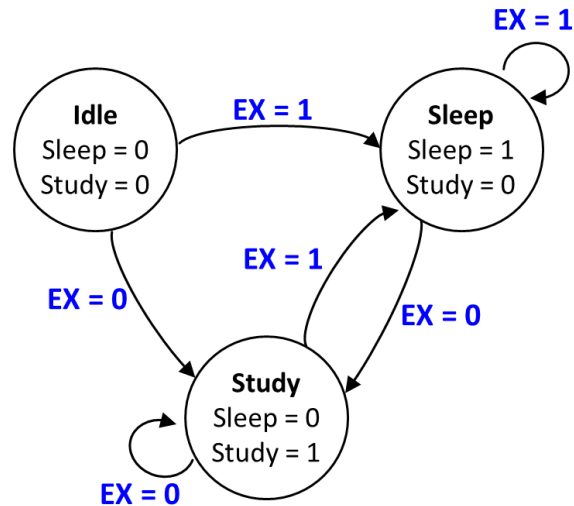

$S_1S_0$	Sleep	Study
0 0		
0 1		
1 0		

Sleep =

Study =

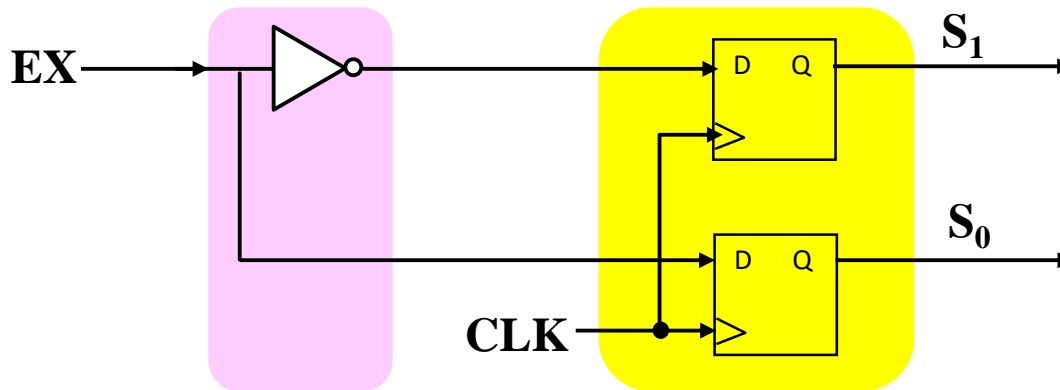

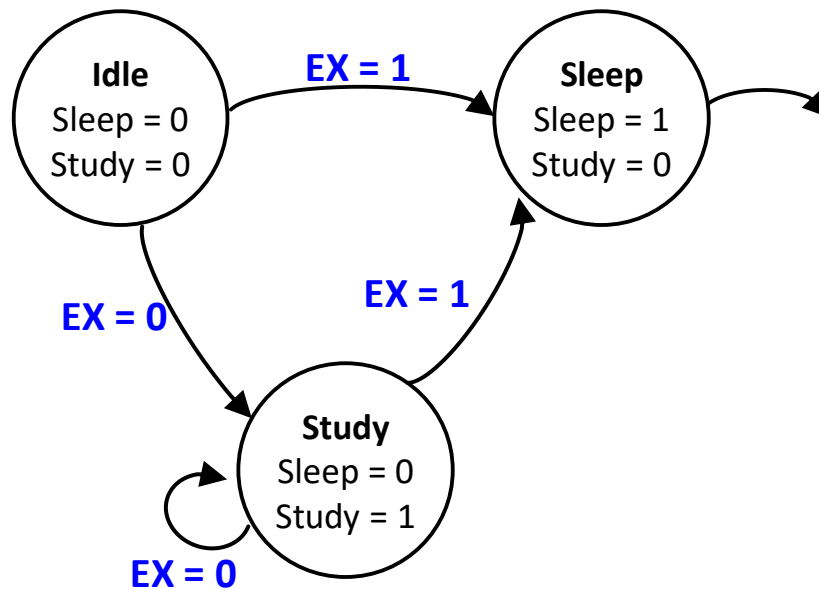
# Changing Sleep Time...



Bob has decided that he is sleep state for too long and has decided to fix his sleep time to 5 hours.


How can we modify his state transition diagram?





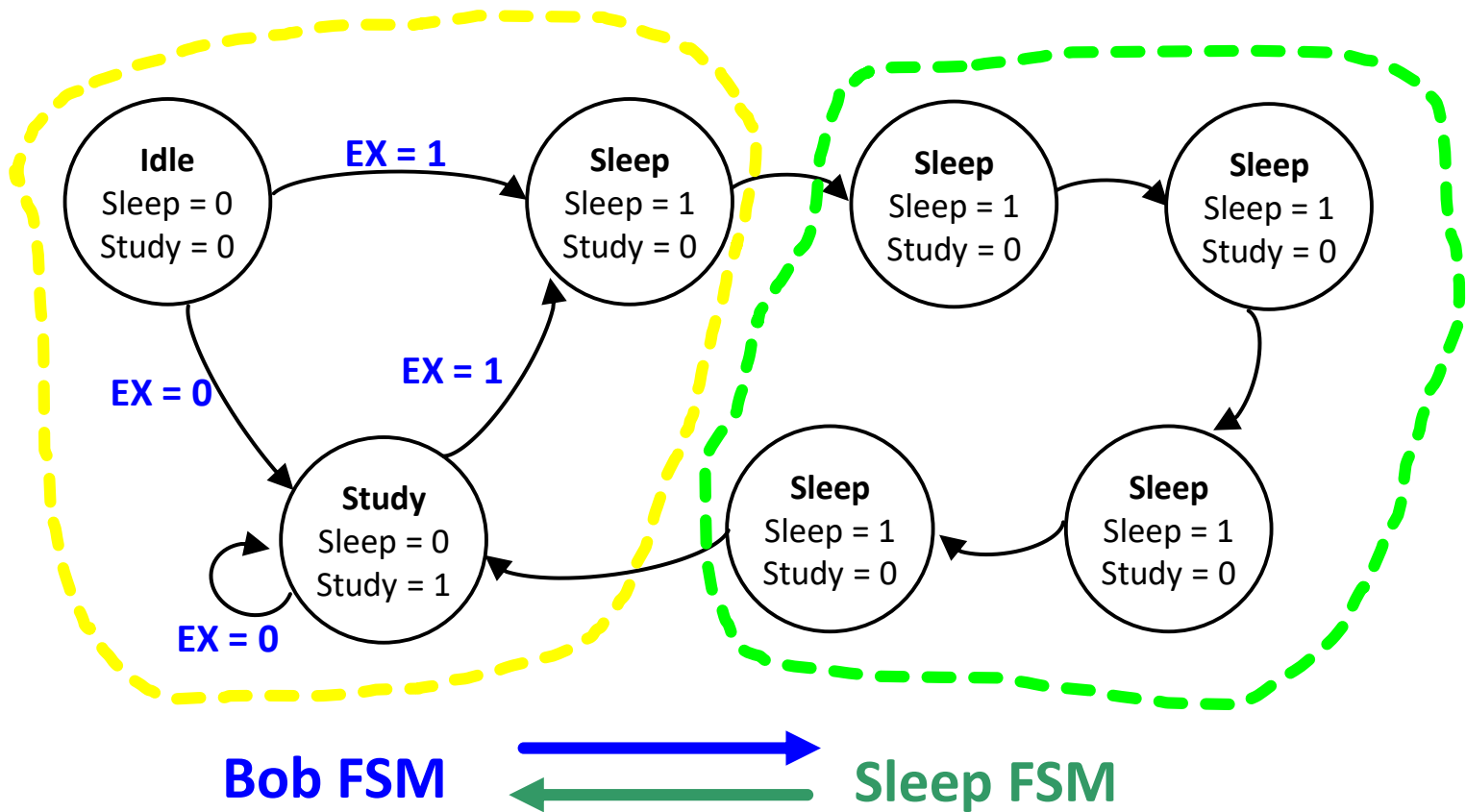
# Modular Design of FSMs

Designing complex FSMs is often easier if they can be broken down into simpler FSMs that interact.




# Modular Design of State Machines

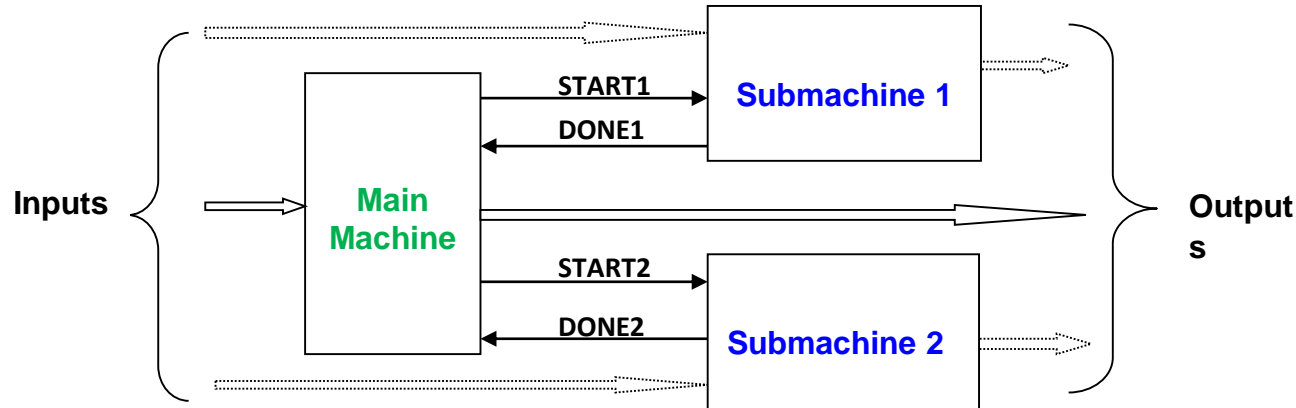


- **Main machine** : executes main algorithm, controls the **submachines** & get the job done. Commands & gets feedback signals from **submachines**.
- **Submachines** respond to external inputs & commands from **main machine**. Can give outputs as well as feedback to the **main machine**.
- Common examples of **submachines** are **counters**, **shift registers**, etc.
- Sometimes the **main machine** is called the **controller** and the **submachines** are called **controlled circuit elements** or **architectural elements**.
- **Trick here** is to **modularize** appropriately, and pick suitable components for the submachines that simplify the design problem.
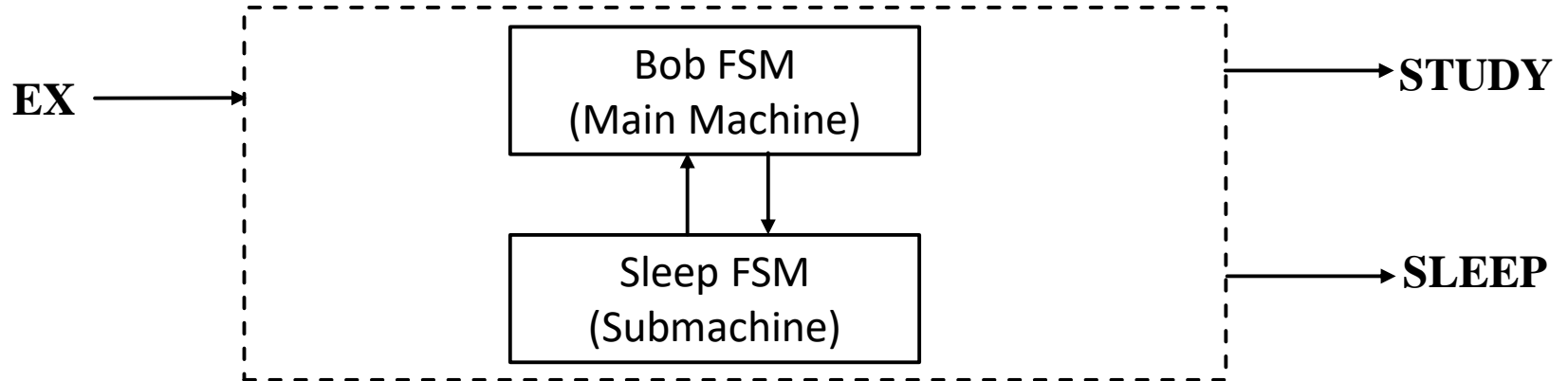
# Modularizing...


What is a natural submachine that we can use?



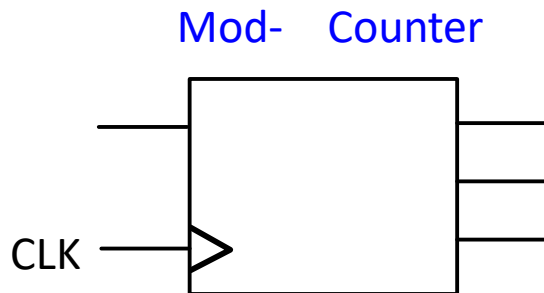
What inputs would you provide? What outputs would you want?



# Modified FSM

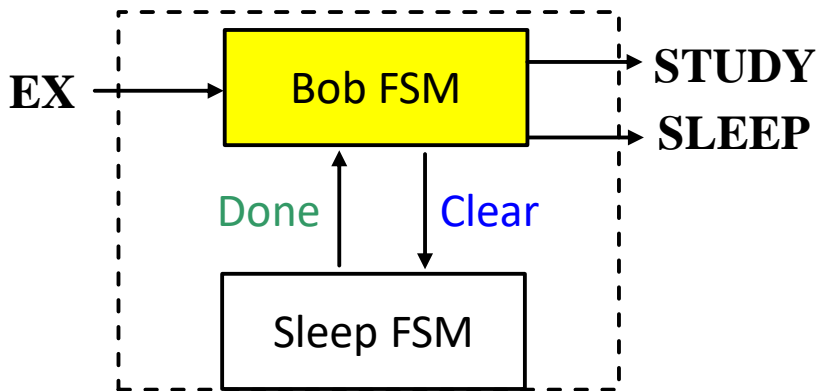


## Sleep FSM



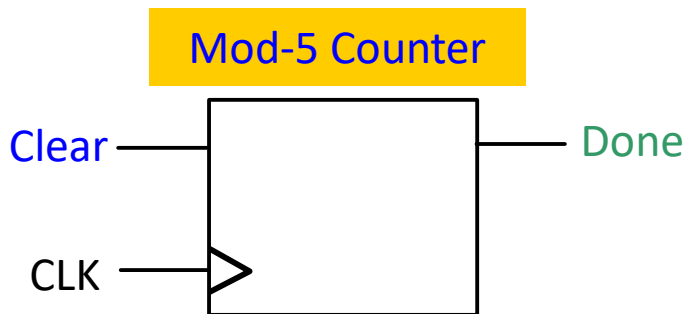




**Done = 1** when count = 4 (100)

## Bob FSM

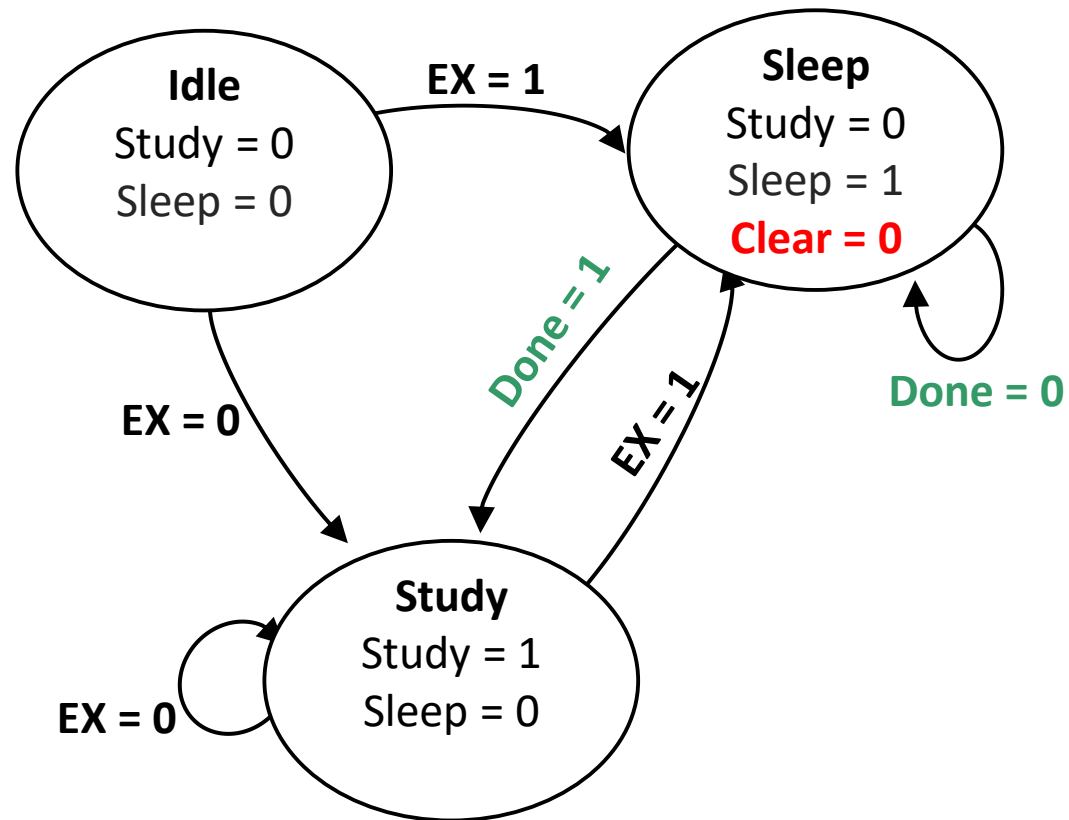

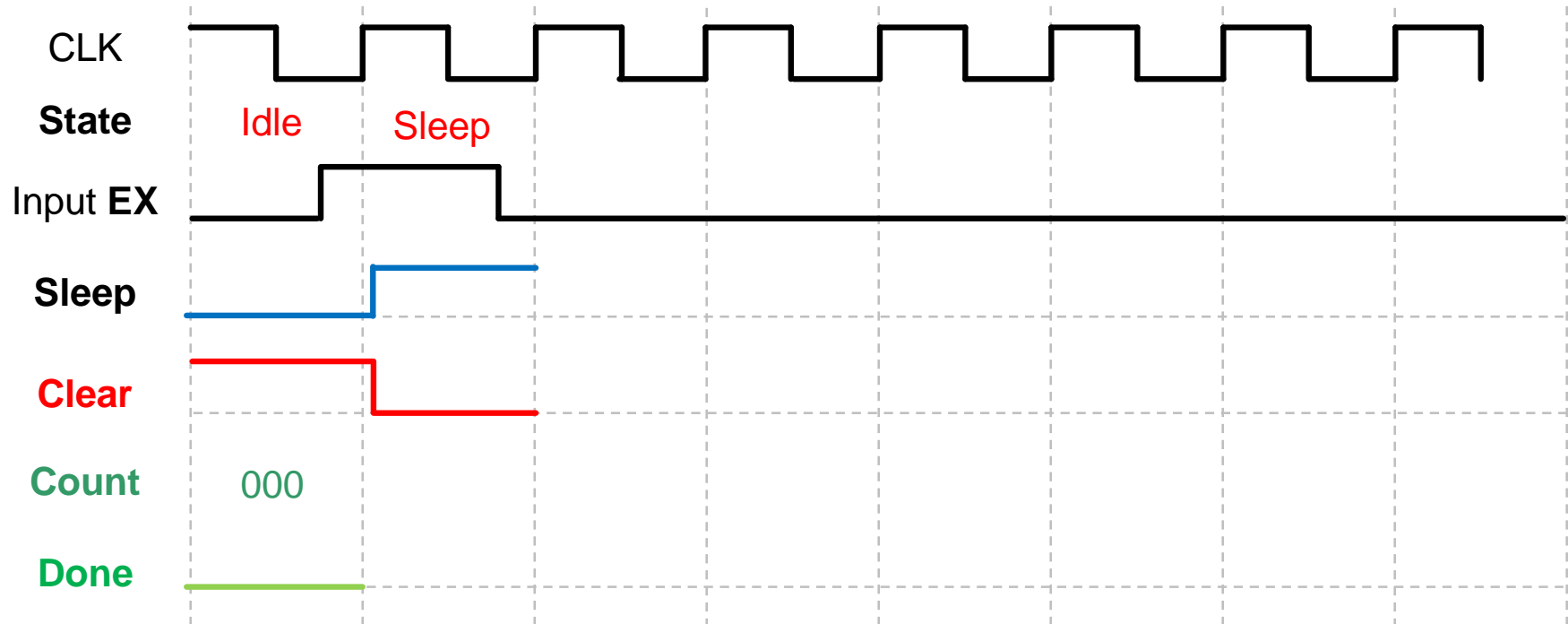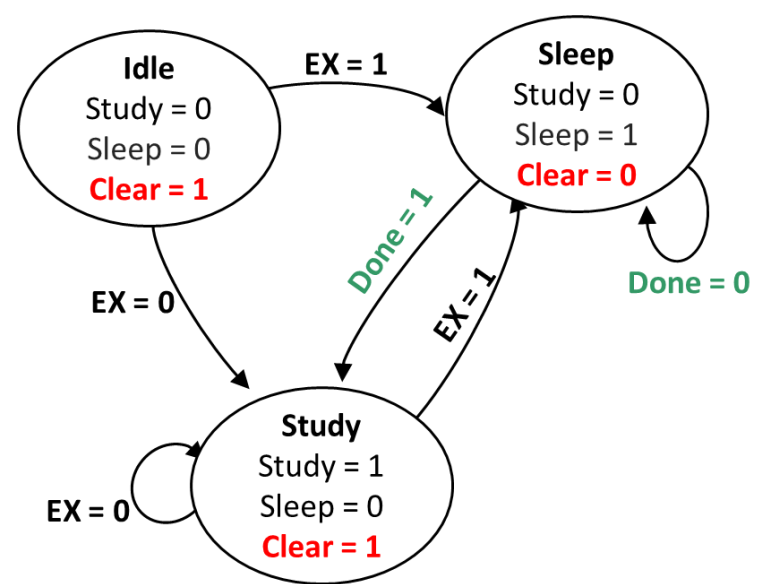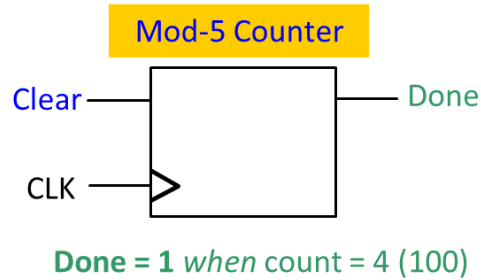Fill in the timing diagram for Bob  
FSM and the counter.



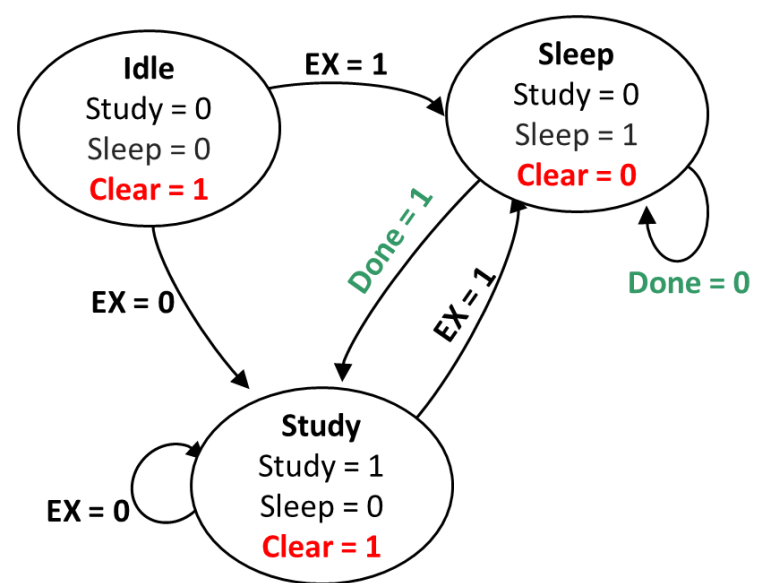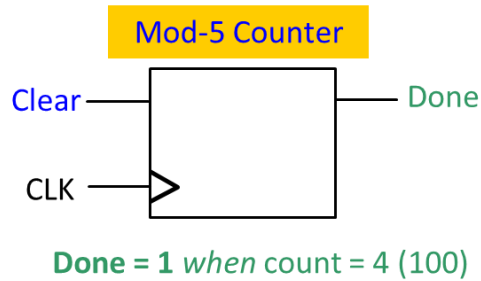

## Timing Diagram:

