

EE2026

Digital Design

MODELING STYLES IN VERILOG


Chua Dingjuan elechuad@nus.edu.sg

Lab 1 Debrief...


In Lab 1... Design Workflow!




RTL Schematic

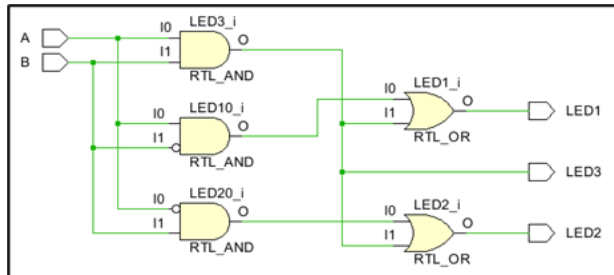

Synthesized Schematic

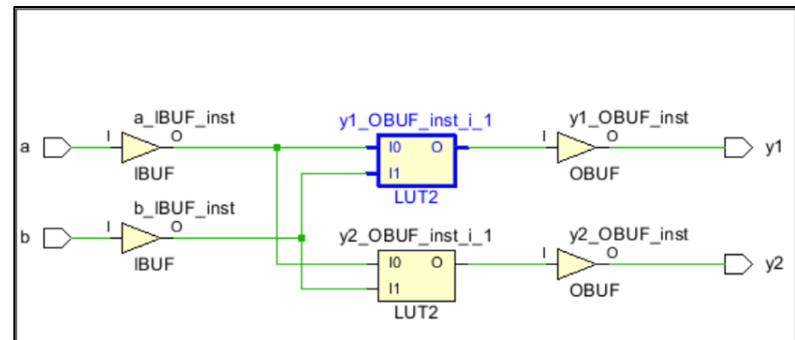

Simulation Results

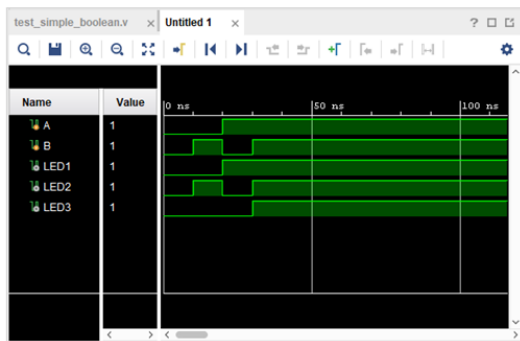

.xdc (Constraints Mapping)

```
Project Summary | my_basys3_constraints.xdc |  
C:/Users/Christopher/Desktop/Lab_1/src/constrains_1newmy_basys3_constraints.xdc  
  
10  
11  
12  
2121  
2122
```

Bad Example 1 – Multi-Driven Net

```
module notgood(...);
```

There are two conflicting instructions presented!

```
    assign x = a | b;
```

Signal x is connected to TWO drivers. Thus, the Multiple Driver Nets error would occur.

```
    assign x = a + b;
```

```
endmodule
```



Bad Example 2 – Multi-Driven Net

```
module notgood  
(input a,b);
```

```
    reg z;
```

```
    assign z = a | b;
```

```
endmodule
```


Assign statements are used for wire or net types.

Thus error states that <z> signal should be a net type!

```
module lablpost(input a,b,  
                output x, y);  
    reg z;  
    assign z = a + b;  
endmodule
```

Error: Target <z> of concurrent assignment or output port connection should be a net type.


Pictorial Summary of Module Structure

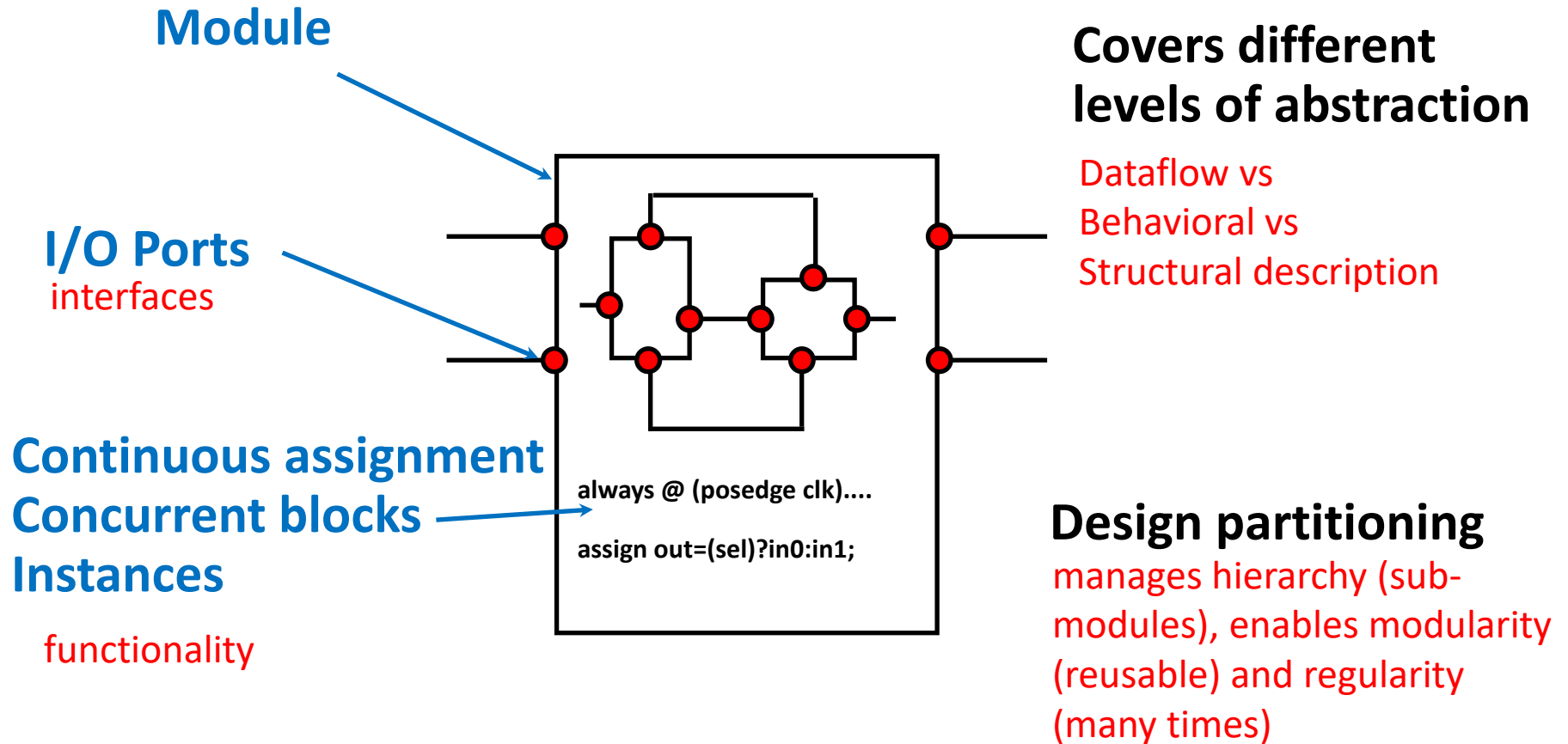



Continuous Assignment (Dataflow)

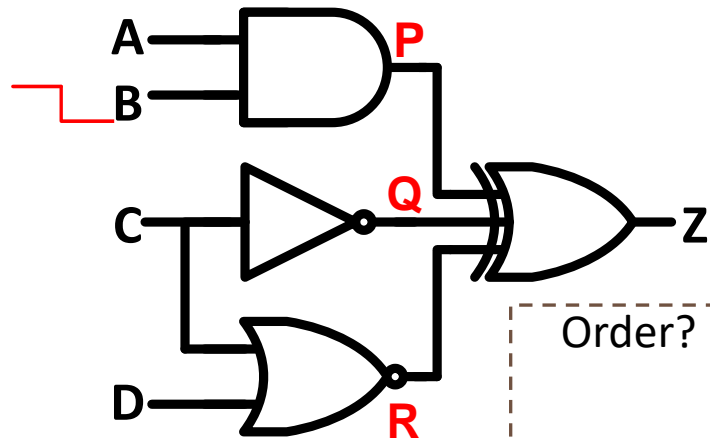assign statements are often used to model combinational logic




```
module bigbox (input a, b, c, d,  
               output z);
```

```
  wire p, q, r; internal connections
```

```
    assign z = p ^ q ^ r; 1  
    assign q = ~c;         2  
    assign p = a & b;      3  
    assign r = ~(c | d);  4
```

```
endmodule
```

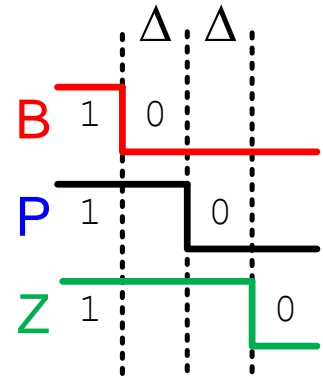

- Whenever there's an **event** on the RHS signal, expression is evaluated and assigned (Δ) \rightarrow *continuously monitored*
- Multiple statements can be executed in parallel (concurrently)
- **wire** is used to represent an internal connection


Useful Operators

- Boolean (bit-wise), logical, arithmetic, concatenation.
- Use brackets for readability, take note if **synthesizable*.

<div>High</div> <div>↑</div> <div>Precedence</div> <div>↓</div> <div>Low</div>	Operator	Description	Examples: $a = 4'b1010$, $b = 4'b0000$
	!, ~	Logical negation, Bit-wise NOT	!a = , !b = , ~a=4'b , ~b=4'b
	&, , ^	Reduction (Outputs 1-bit)	&a = 0, a=1, ^a = 0
	{ __, __ }	Concatenation	{b, a} = 8'b00001010
	{ n{ __ } }	Replication	{ 2 {a} } = 8'b10101010
	*, /, %, ,	Multiply, *Divide, *Modulus	3 % 2 = 1, 16 % 4 = 0
	+, -	Binary addition, subtraction	a + b = 4'b1010
	<< , >>	Shift Zeros in Left / Right	a << 1 = 4'b0100, a >> 2 = 4'b0010
	<, <=, >, >=	Logical Relative (1-bit output)	(a > b) =
	==, !=	Logical Equality (1-bit output)	(a == b)= (a != b)=
	&, ^,	Bit-wise AND, XOR, OR	a&b = a b =
	&&,	Logical AND, OR (1-bit output)	a&&b = a b =
	?:	Conditional Operator	<out> = <condition> ? If_ONE : if_ZERO

Conditional Operator...

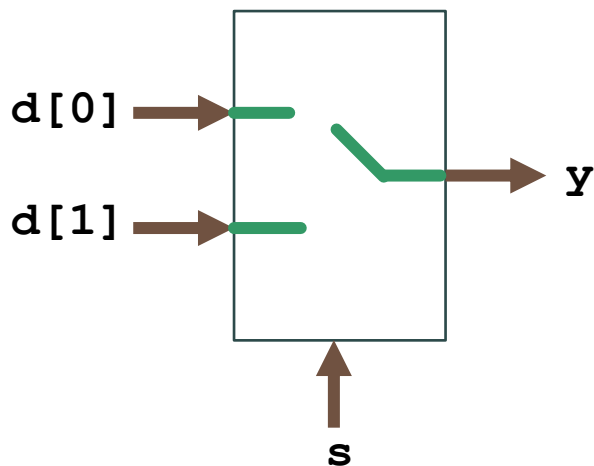The `?:` conditional operator allows us to select the output from a set of inputs based on a condition.



```
module mystery ( input s, input [1:0] d,  
                 output y );
```

```
assign y = s ? d[1] : d[0];
```

`<output> = <condition> ? If_ONE : If_ZERO`

`s = 1 → y = d[1], s = 0 → y = d[0]`


```
endmodule
```

- This expression is evaluated whenever there is an event on any input.
- What is this block?

Procedural Assignment : `always`

Behavioral, higher-level description of logic.

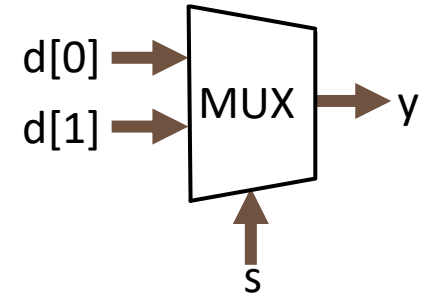2 assignment types : **Blocking & Non-Blocking**



```

module mux21 ( input s, input d[1:0],
               output reg y );
  
```

Anything assigned in an `always` block must be declared as type `reg`

```

always @ (s, d)
  
```

Conceptually, the `always` block runs *once* when any signal in *sensitivity list* (s,d) changes value.

```

begin
  
```

```

    if (sel == 1'b0)
        y = d[0];
    else
        y = d[1];
  
```

Statements executed sequentially & evaluated instantaneously. → Order matters!

```

end
  
```

`begin` and `end` behave like parentheses/brackets for conditional statements.

```

endmodule
  
```

Some notes on: `always`

- `always@(*)` includes all signals that are read in statements.
- Statements within `always` block are executed *sequentially*.
- Variables within sensitivity list are very important!
- `if--else if--else`, `case`, `for`, `while` can only be used in procedural assignments (always blocks)
- Multiple always blocks run in parallel, concurrently, watch out for multi-driven nets and race conditions. (next slide)
- No ~~`assign`~~ in always blocks!

Registers

- Anything assigned in an `always` block must be declared as type `reg`
- In Verilog, the term register (`reg`) simply means a variable that can hold a value. (cf. `wire` which must be driven)

Bad Example – Multi-Driven Net

```
module notgood(...);
```

```
    always @ (*)
```

```
        y = y + 1;
```

```
    always @ (*)
```

```
        y = y + 3;
```

```
endmodule
```



There are two conflicting instructions presented.

The first instruction would be to increment y by 1, while the second instruction would be to increment y by 3. The compiler would not be able to know which instruction should be executed.

Thus, the Multiple Driver Nets error would occur.

 **Implementation** (5 errors)

 **Opt Design** (5 errors)

 [DRC 23-20] Rule violation (MDRV-1) Multiple Driver Nets - Net y_OBUF[0] has multiple drivers: y_reg[0],
 [Vivado_Td 4-78] Error(s) found during DRC. Opt_design not run.

Ref – Conditional Statements

If - else if - else

```
if ( expr )  
    statement;
```

```
if ( expr )  
    statement;  
else  
    statement;
```


```
if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else  
    statement;
```

case

```
case ( expr )  
  
    value1 : statement;  
    value2 : statement;  
    value3 : statement;  
    ...  
    default : statement;  
  
endcase
```


Equivalence
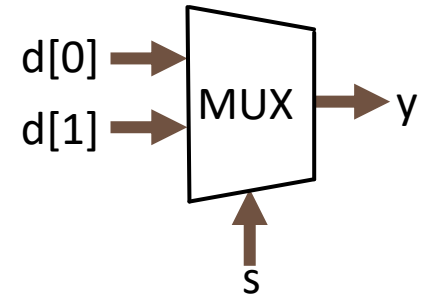
```
module mux21 ( input s, input [1:0] d, output reg y );  
  
always @ (s, d)  
begin  
    if (s == 1'b0)  
        y= d[0];  
    else  
        y= d[1];  
end  
endmodule
```



```
module mux ( input s, input [1:0] d, output y );  
  
assign y = s ? d[1] : d[0];  
  
endmodule
```

Equivalence...

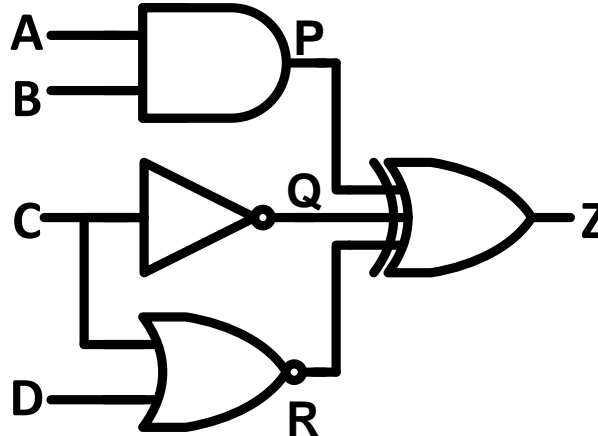

```
module bigbox
(input a,b,c,d, output z);
```

```
wire p, q, r;
```

```
assign q = ~c;
```

```
assign z = p ^ q ^ r;
```

```
assign p = a & b;
```

```
assign r = ~(c | d);
```

```
endmodule
```

```
module bigbox
(input a,b,c,d, output ____ z);
```


```
always @ (      )
begin
```

```
end
endmodule
```

Structural Modeling – Primitives

Structural modeling can be used to connect multiple modules and gates.

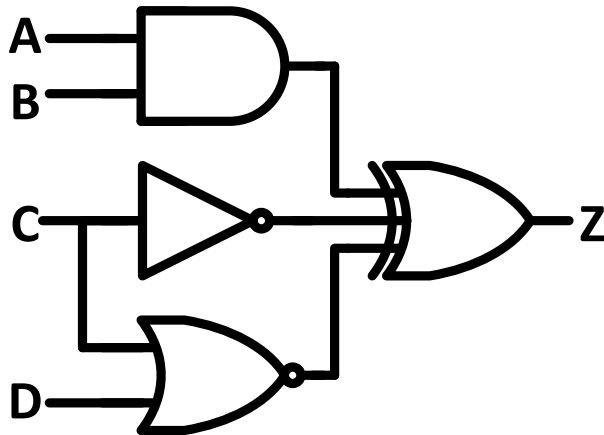Verilog provides a standard set of primitive such as basic logic gates.



Dataflow

```
module bigbox (input a,b,c,d, output z);  
  
    assign z = (a & b) ^ ~c ^ ~(c | d) ;  
  
endmodule
```


Structural (using primitives)

```
module bigbox (input a,b,c,d, output z);  
    wire p, q, r;  
  
    and u1 (p, a, b); //output, then inputs  
    not u2 (      );  
    nor u3 (      );  
    xor u4 (      );  
  
endmodule
```



Structural Modeling

Structural modeling can be used to connect multiple modules via port connection by name and position.
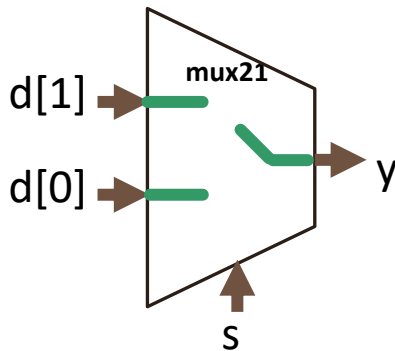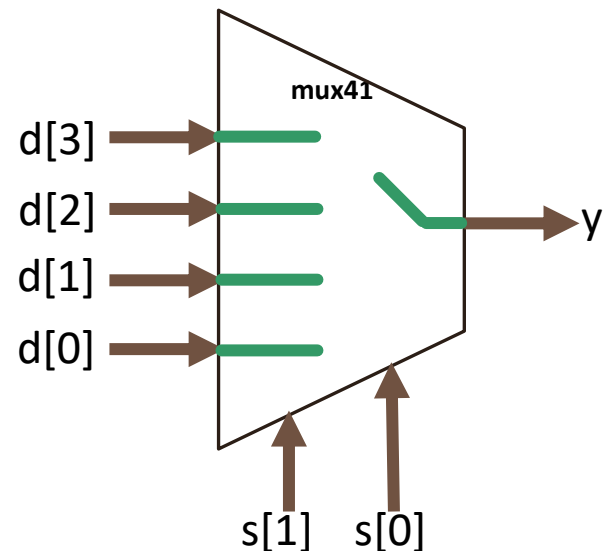
```
module mux21( input s,  
             input [1:0] d,  
             output y);  
  
    assign y = s ? d[1] : d[0];  
  
endmodule
```




```
module mux41( input [1:0] s,  
             input [3:0] d,  
             output y);  
  
    ... .. ?  
  
endmodule
```



Structural Modeling

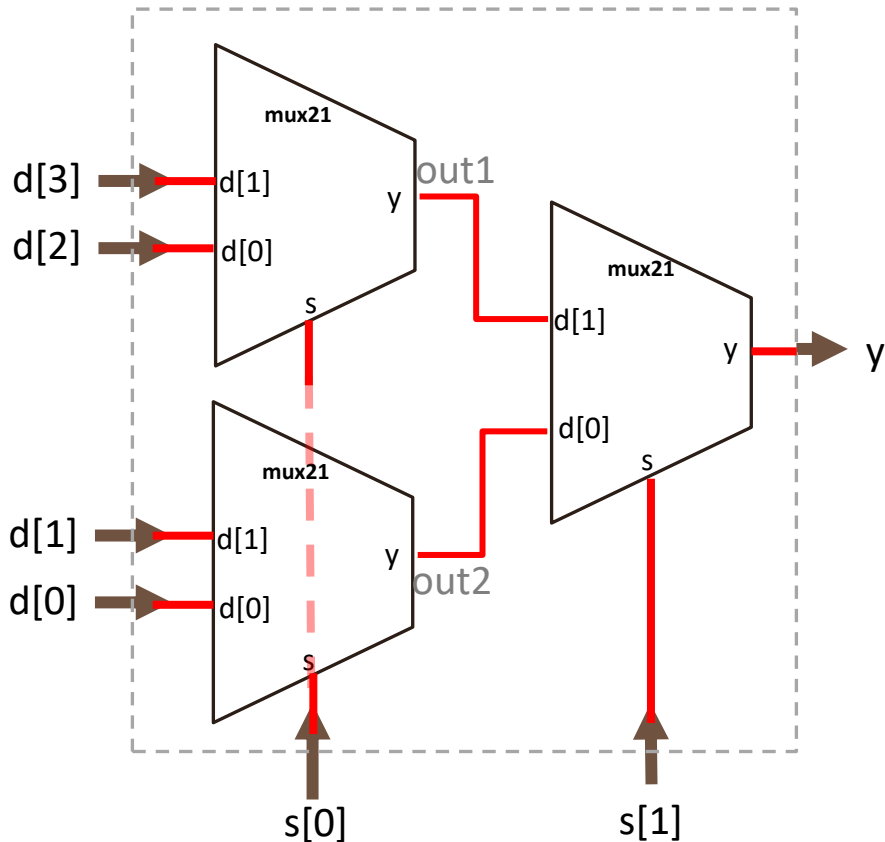For example, a 4-to-1 multiplexer can also be implemented by combining several 2-to-1 multiplexers.




```
module mux21( input s, input [1:0] d,  
              output y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

Port Connection by Position

```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
    wire out1, out2;  
  
    //check for port order!  
    mux21 u1 (s[0], d[3:2], out1);  
  
    mux21 u2 (                );  
  
    mux21 u3 (                );  
  
endmodule
```

Structural Modeling

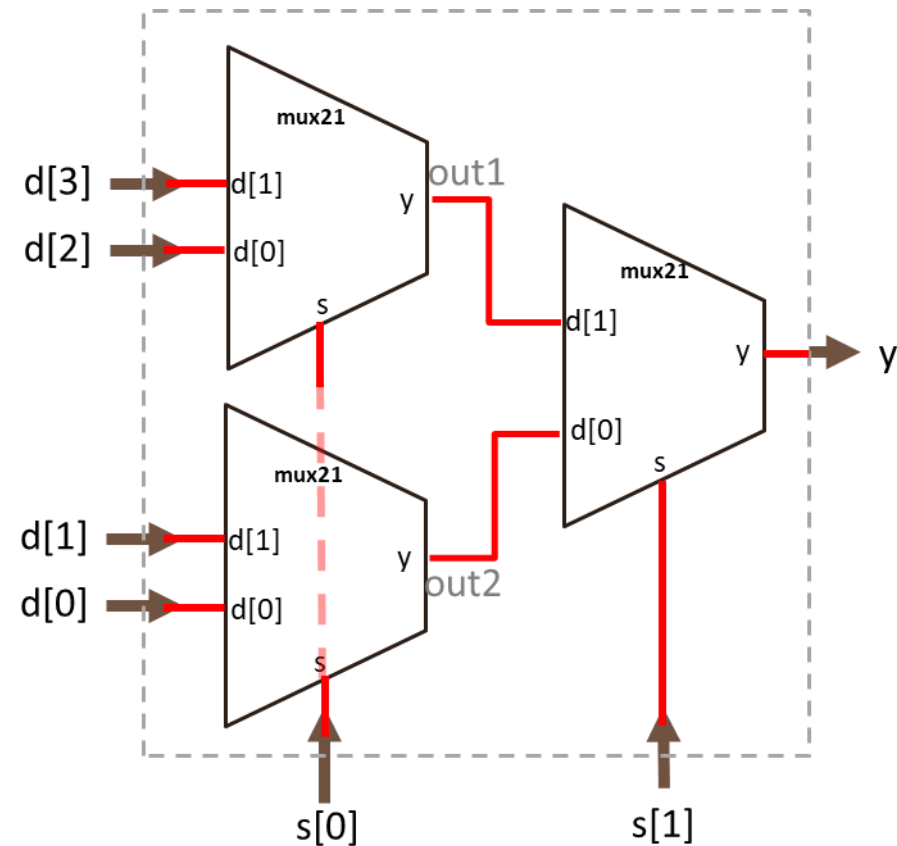For example, a 4-to-1 multiplexer can also be implemented by combining several 2-to-1 multiplexers.




Port Connection by Name

```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
  wire out1, out2;  
  
  mux21 u1 (.s ( s[0]),  
            .d ( d[3:2] ),  
            .y ( out1 ) );  
  
  mux21 u2 (.s ( s[0]),  
            .d ( d[1:0] ),  
            .y ( out2 ) );  
  
  mux21 u3 (.s ( s[1]),  
            .d ( {out1, out2} ),  
            .y ( y ) );  
  
endmodule
```

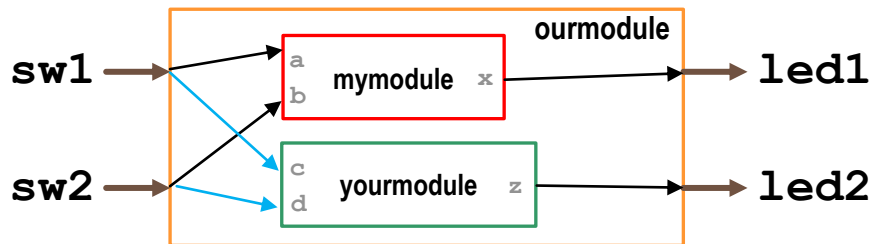Example - Structural Modeling

- For modular designs, the top design is often specified as interconnected blocks.
- Two examples below demonstrate port connection by position / name.

```
module mymodule (input a, b, output x);  
...  
endmodule
```



Port Connection by Position

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
    mymodule M1 (sw1, sw2, led1);  
    yourmodule M2 (sw1, sw2, led2);  
  
endmodule
```

```
module yourmodule (input c, d, output z);  
...  
endmodule
```


Port Connection by Name

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
    mymodule M1 ( .a (sw1),  
                  .b (sw2),  
                  .x (led1) );  
  
    yourmodule M2( .z(led2),  
                  .c (sw1),  
                  .d(sw2) );  
  
endmodule
```

Recall Simulation?


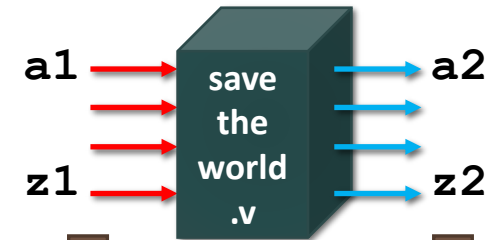
```
module savetheworld (input a1, ... z1,  
                    output a2, ..., z2);  
    .....  
    .....  
    .....  
endmodule
```



How do we know our design actually works?

- Functional Simulation
(Xilinx)

Method


- Designer applies input values to the code
- Simulator produces corresponding outputs in truth tables / timing diagrams
- Simulators usually assume negligible propagation gate delays.

Verilog Code

```
module  
    .....  
    .....  
endmodule
```

Test Bench
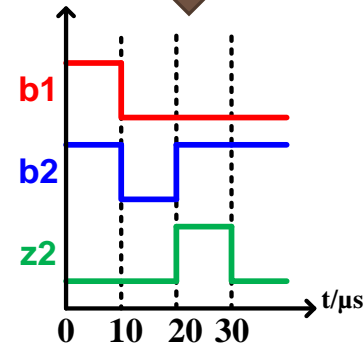
```
call module  
a1=9;  
b1=1;  
//wait for 10u  
#10  
b1=0;
```



Simulation Testbench Example

```
module mux21( input s,  
              input [1:0] d,  
              output y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

```
module mux_test();  
  
    reg [1:0] ip = 0;  
    reg sel = 0;  
    wire op;  
  
    mux21 dut (sel, ip, op);  
  
    initial begin  
        ip = 2'b10;  
        sel = 1'b0;  
        #10; //wait 10 time units  
    end  
  
endmodule
```

