



HOMEWORK 2

Issued on Oct. 5, 2021 (Tuesday)

Due on Oct. 19, 2021 (Tuesday, 11:59pm)


Submit your homework online <https://canvas.ust.hk>

Do not do your work on the question papers. Use separate blank papers


Q1. Compute and write the answers in polar form, i.e., $r\angle\theta^\circ$.

a. $\frac{2j}{10\angle 30^\circ}$ b. $\frac{15e^{j\frac{\pi}{2}}}{-3}$ c. $\frac{5\angle 60^\circ}{j+2}$ d. j^j

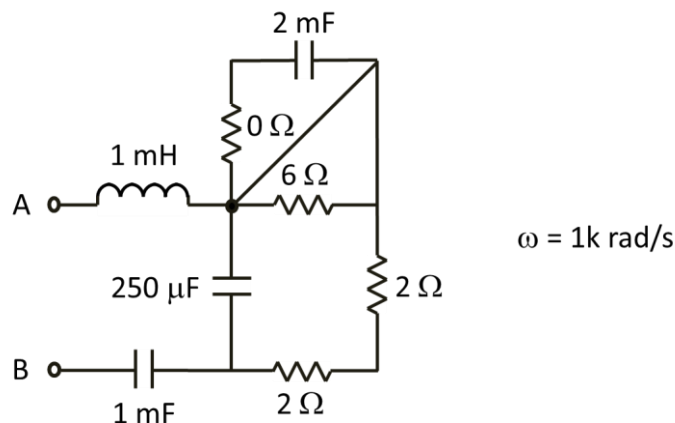Q2. Find the impedance Z_{AB} and write the answer in rectangular form.




Q3. Consider the following circuit.

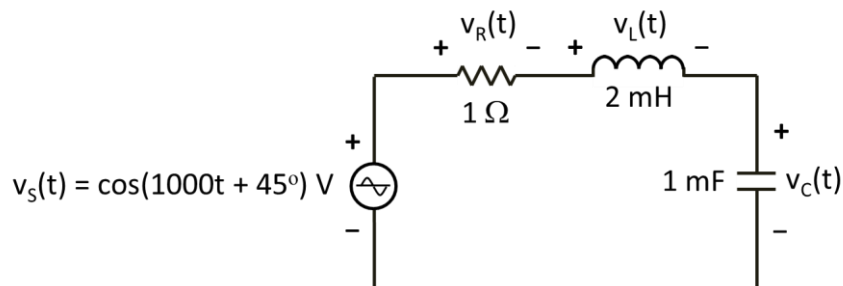


- (a) Draw all the impedances (Z_R , Z_L and Z_C) in one impedance diagram.
- (b) Draw all the phasor voltages (V_S , V_R , V_L and V_C) in one phasor diagram.
- (c) Evaluate $v_S(t)$, $v_R(t)$, $v_L(t)$ and $v_C(t)$ at $t = 1$ ms.

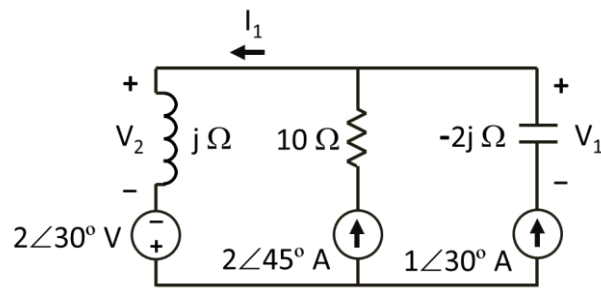
Q4. Find I_1 , V_1 and V_2 , and write the answers in polar form.



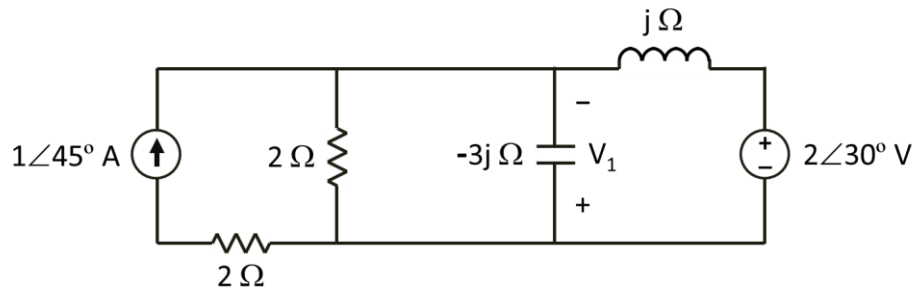
Q5. Find V_1 and write the answer in polar form.



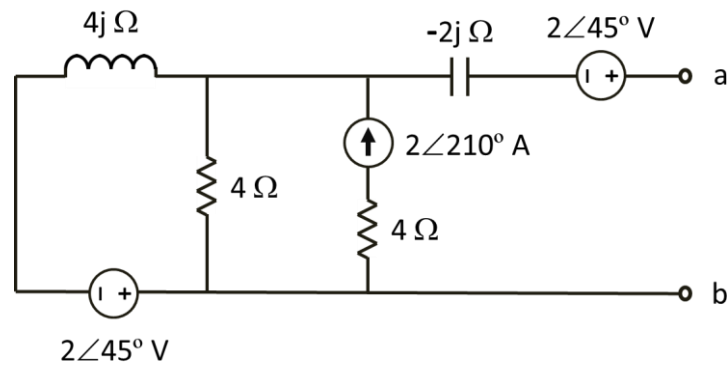
Q6. Find and draw the Thevenin's equivalent circuit with respect to the terminals a and b, and write the answers in polar form.



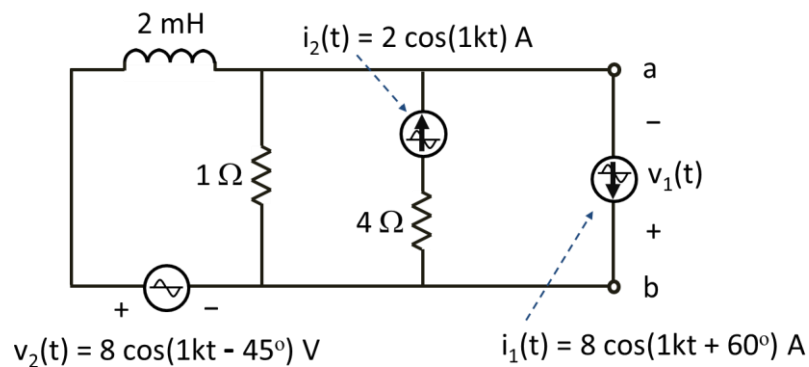
Q7. Use Norton's theorem to find $v_1(t)$ in the network.



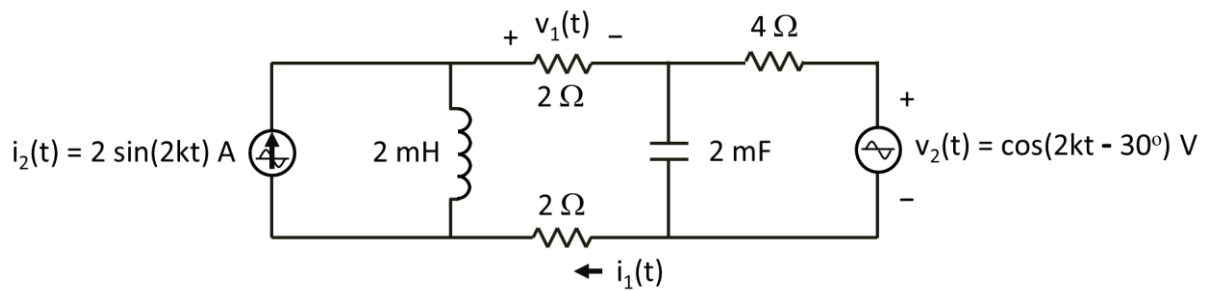
Q8. Use source transformation(s) to find $i_1(t)$ and $v_1(t)$ in the network.



Q9. Find $i_1(t)$ and $v_1(t)$.

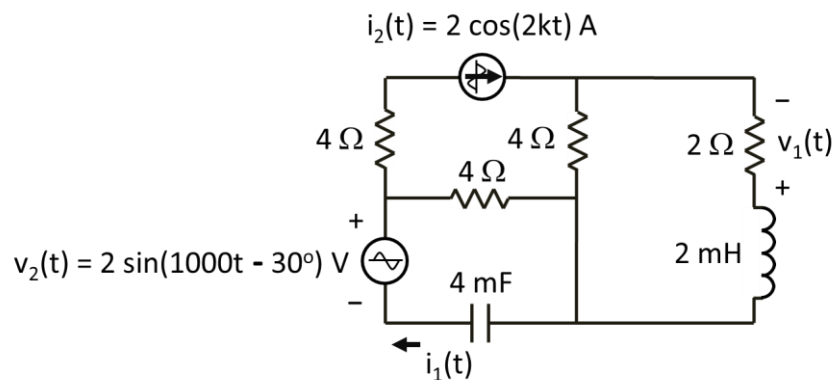

Q10. Consider the following circuit.

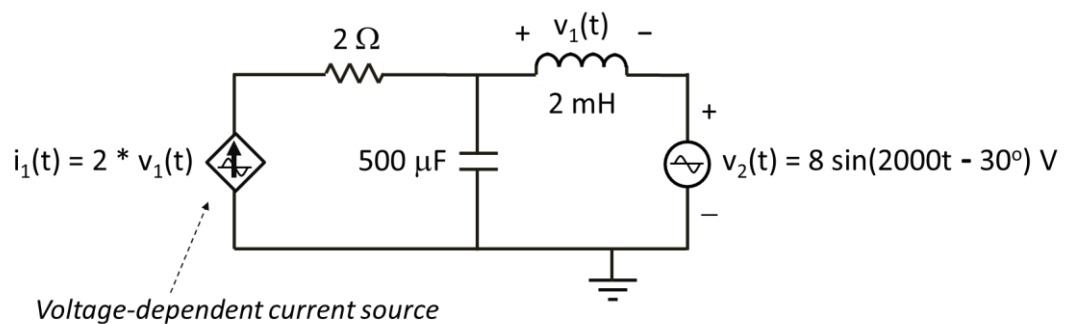

- Compute the average AC power for each circuit element.
- Specify whether each circuit element is supplying AC power, absorbing AC power (dissipating power), or neither.
- Verify that the AC power balance is satisfied.