




ELEC1100 - Tutorial 4


Transistor & H-bridge

Introduction to Lab#04

Review: PWM Control

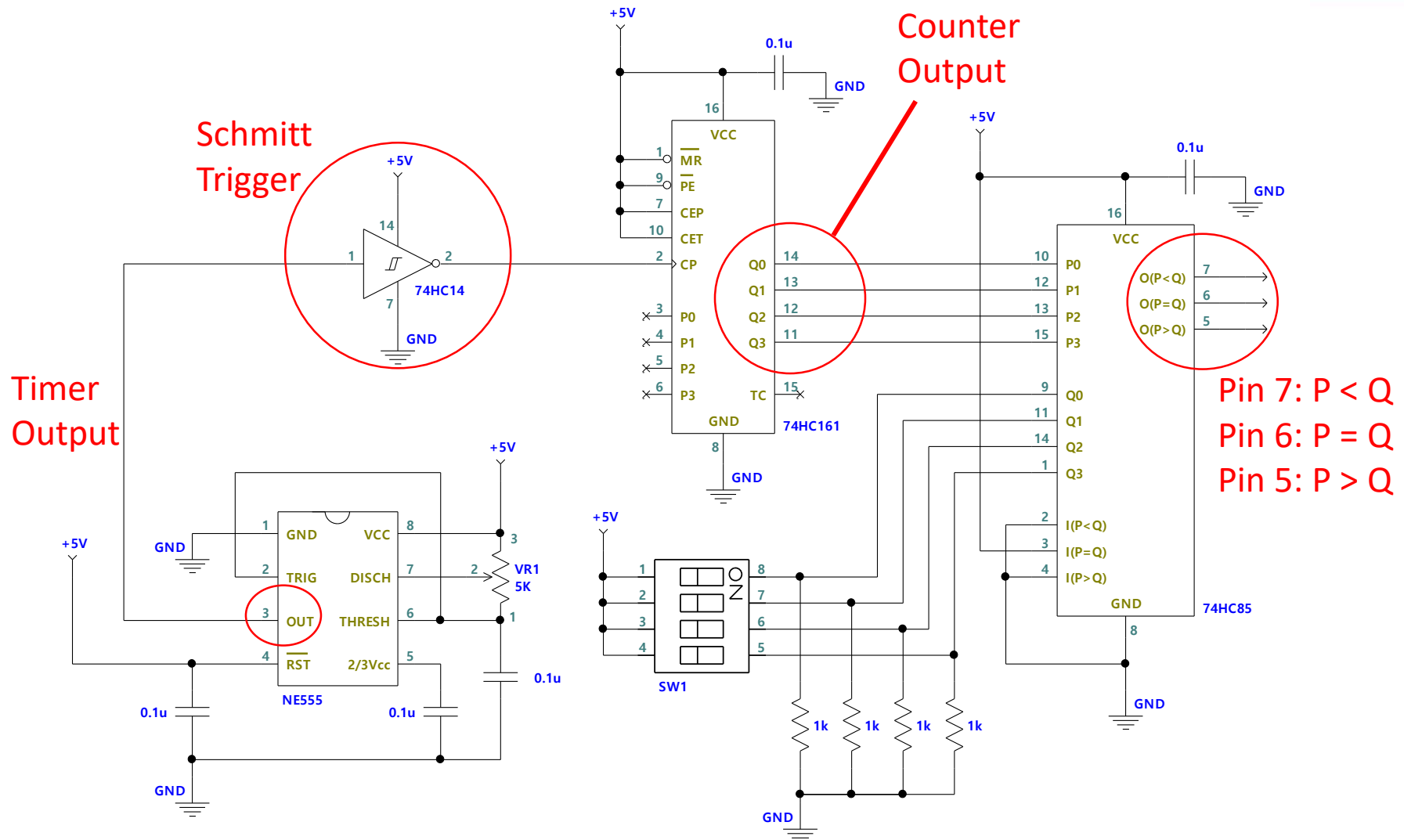


Between NE555 & 74HC85

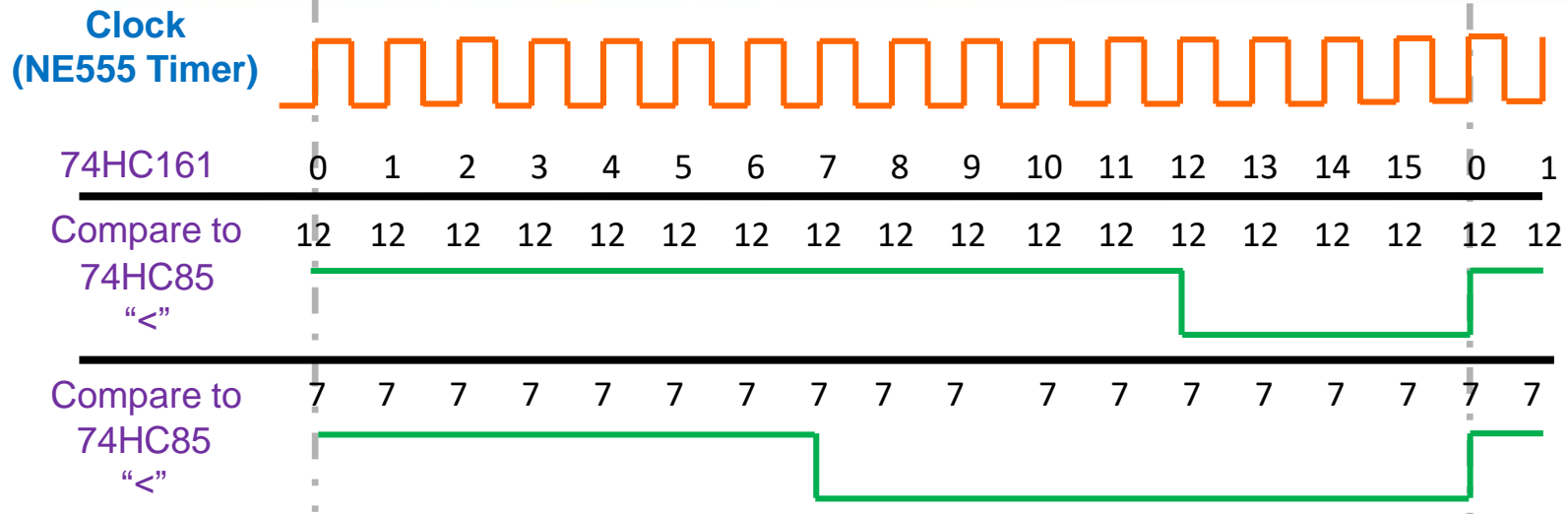

| | NE555 Timer (clock) | 74HC85 Comparator (PWM at pin 7 "less than") |
|------------|--|---|
| Frequency | $f_{555} = \frac{1}{T} = \frac{1}{0.7(R_A + 2R_B)C_1}$ | $f_{85} = \frac{f_{555}}{16}$ |
| Duty Cycle | $\frac{R_A + R_B}{R_A + 2R_B}$ | $\frac{Q}{16}$ |

***Q is the manual input to 74HC85*

74HC85 Outputs

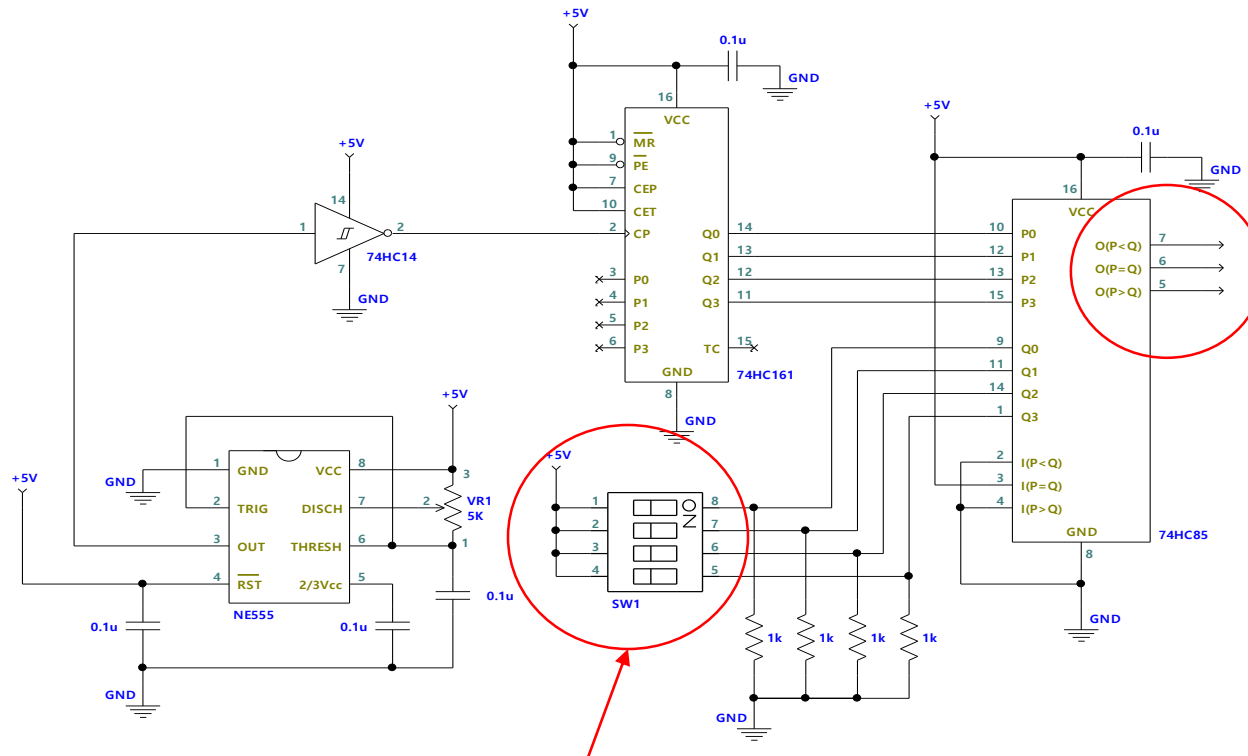

Manual input Q

Pin 7: $P < Q$

Pin 6: $P = Q$

Pin 5: $P > Q$

0101 = 5


Pin 7: 5/16

Pin 6: 1/16

Pin 5: $(16-5-1)/16$


Given that Q ($Q_3Q_2Q_1Q_0$) = 0101, what is the duty cycle value at Pin 7/6/5 of the 74HC85 comparator?

At Physical Lab

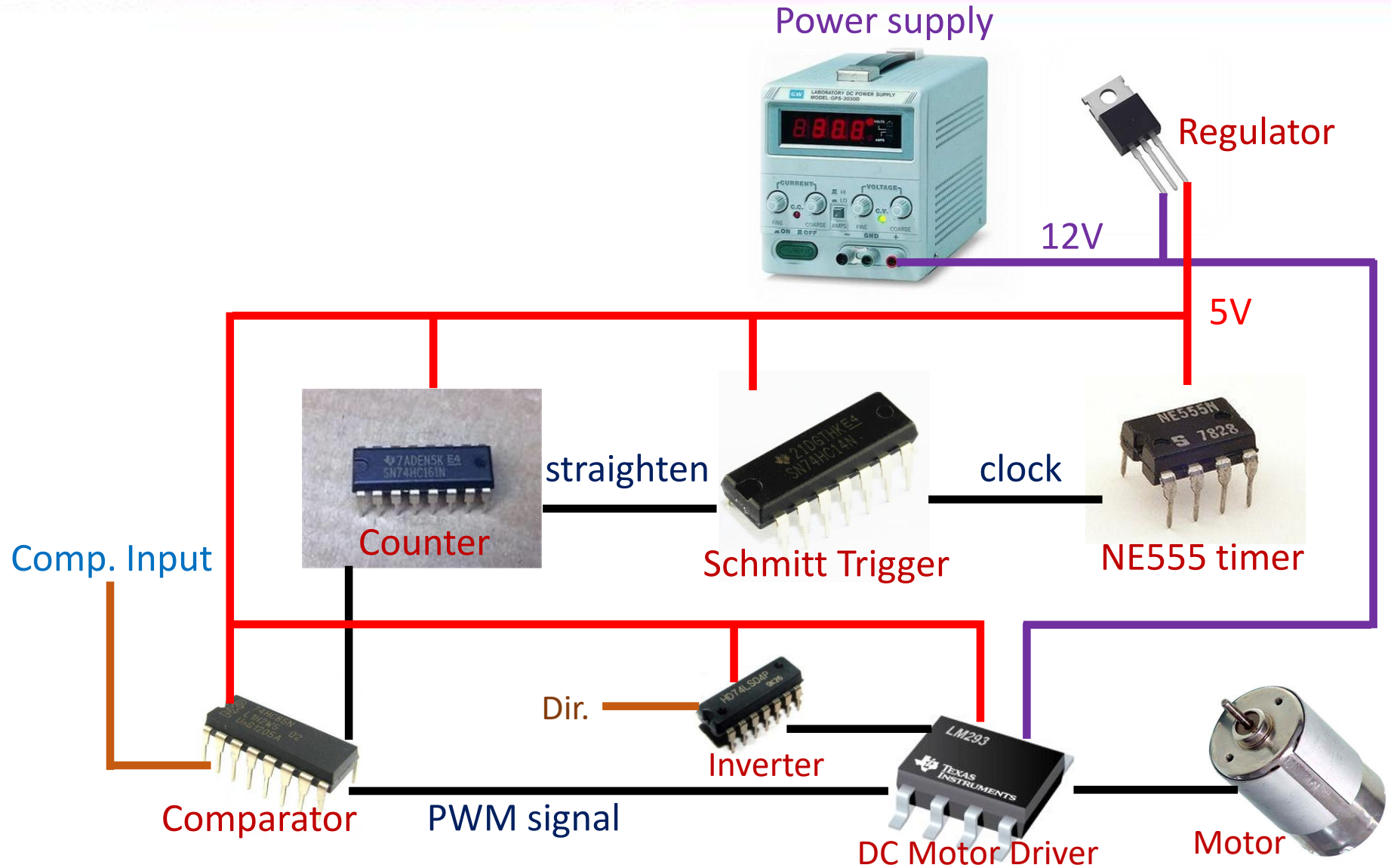

Use of BJT


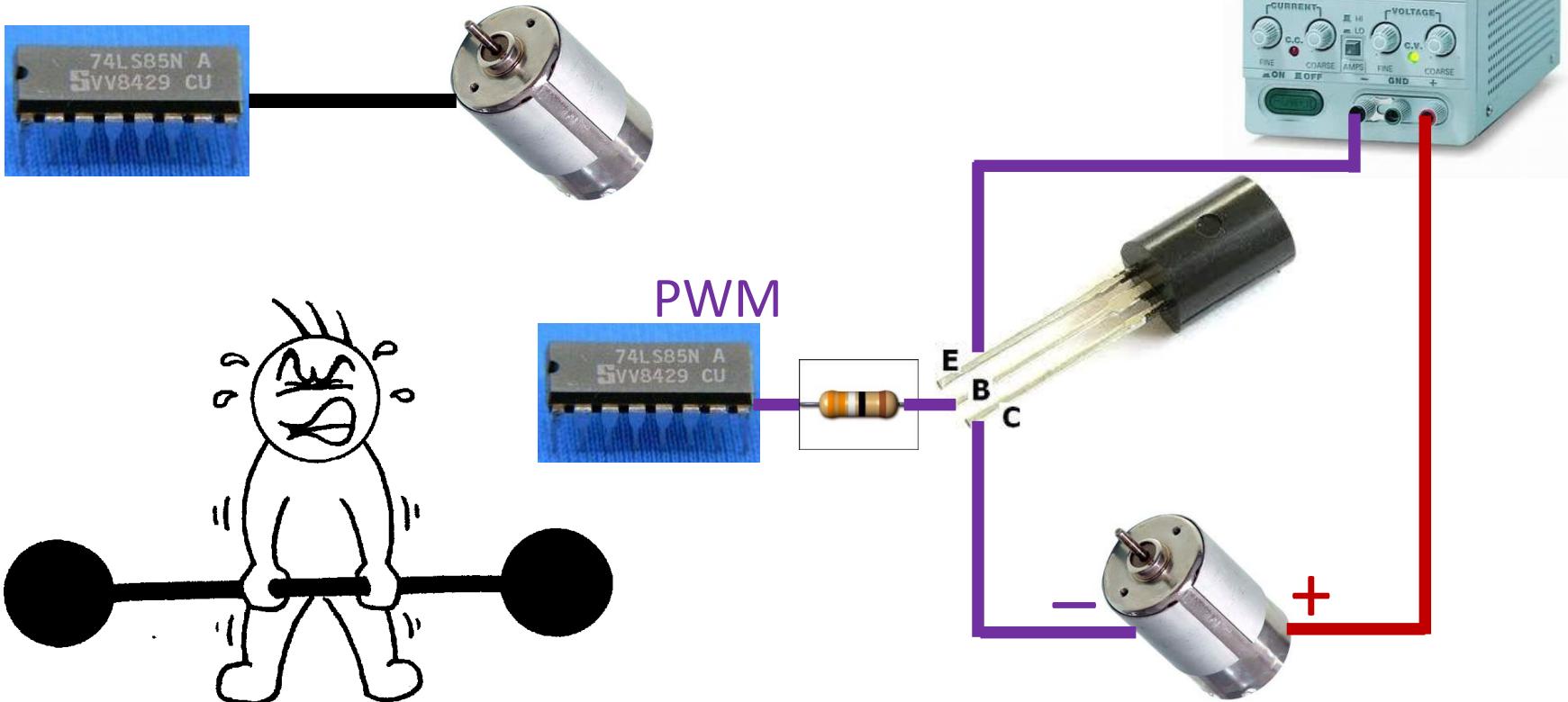
❖ However, if you use the PWM signal on a motor, it will/may/will **not** work. **WHY?**



Transistor analysis

❖ Consider this circuit:

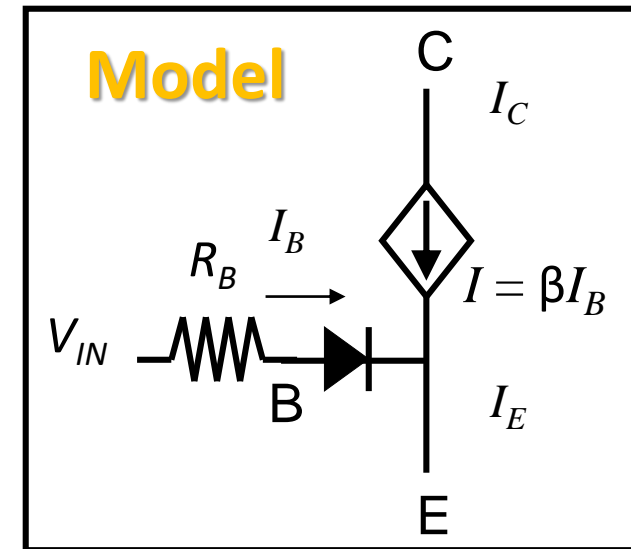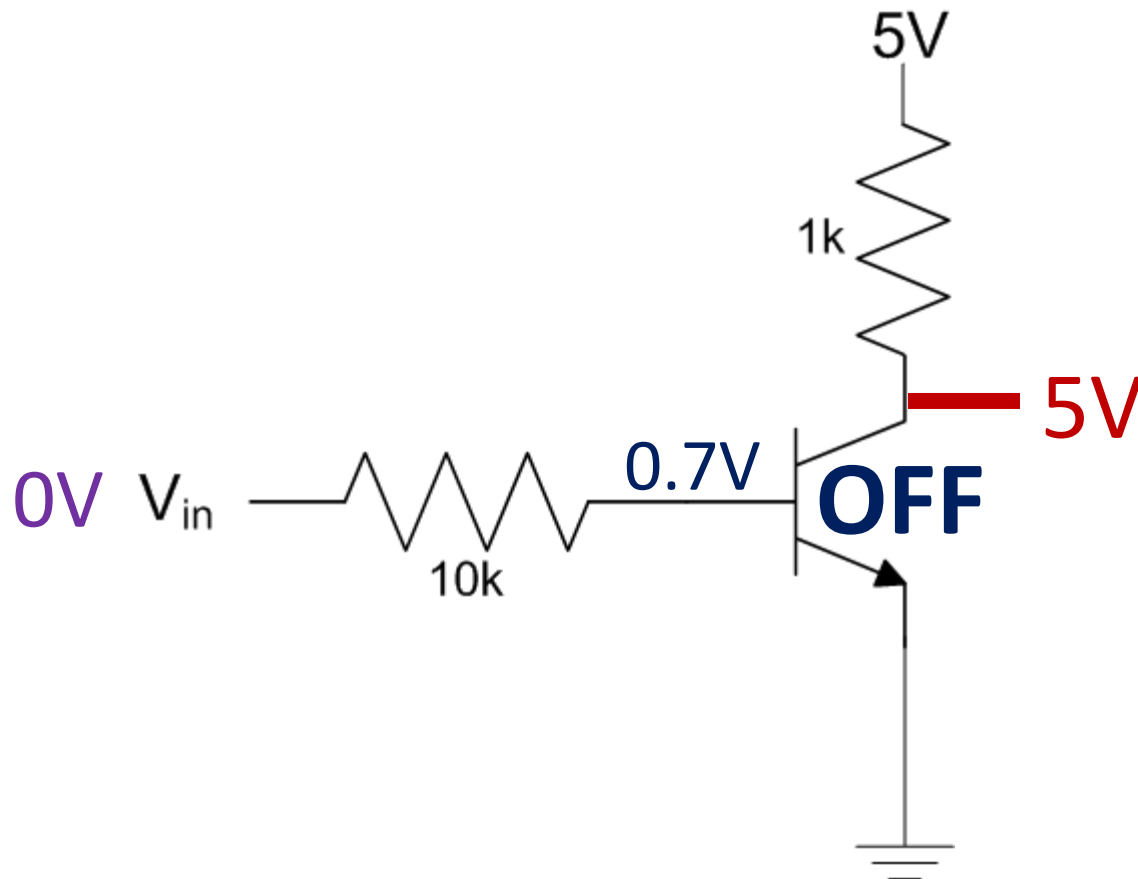
Turn on voltage $V_{be} = 0.7$ Current Gain $\beta = 100$



Transistor analysis

❖ Consider this circuit:

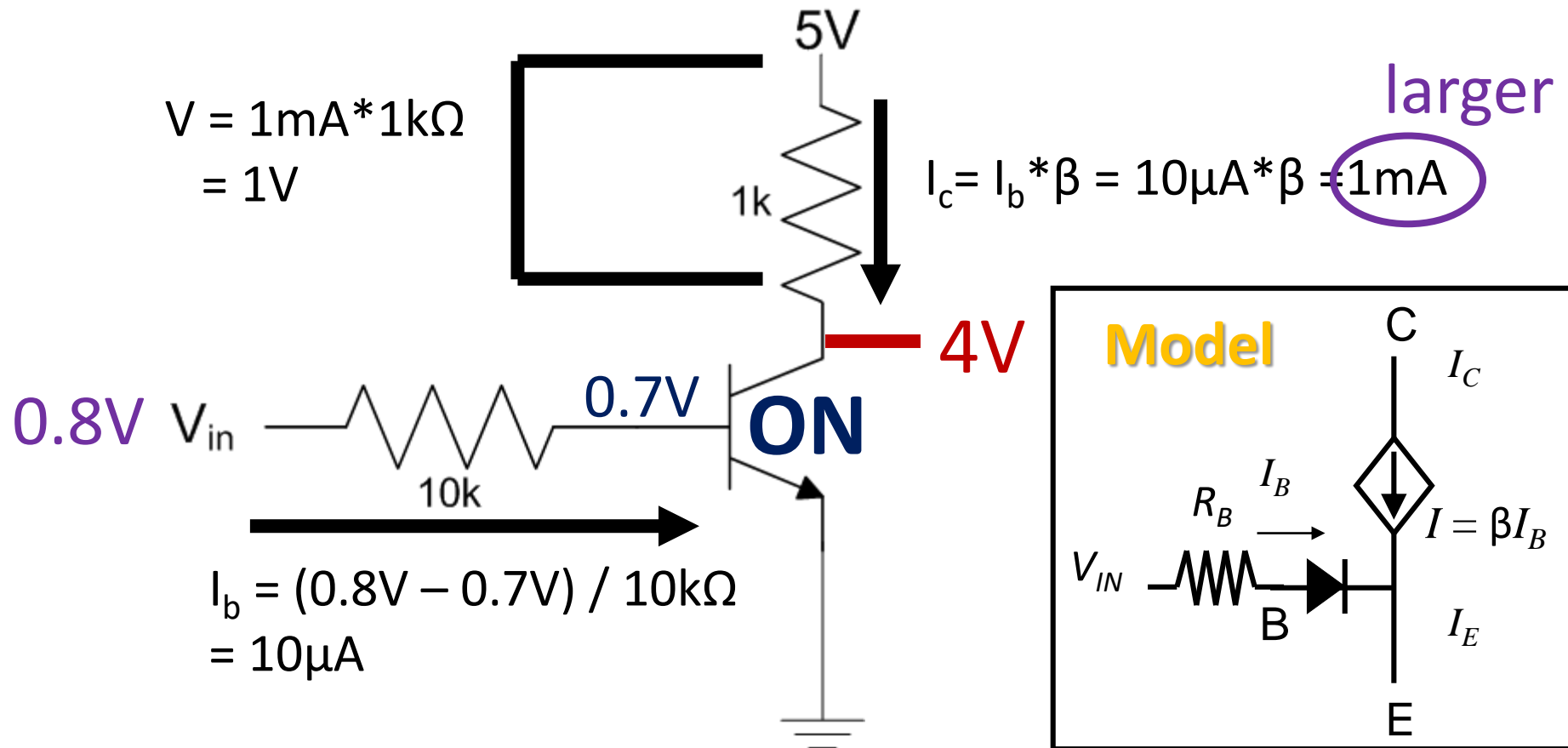Turn on voltage $V_{be} = 0.7$ Current Gain $\beta = 100$




Transistor analysis

❖ How about if $V_{in} = 1V$?

Turn on voltage $V_{be} = 0.7$

Current Gain $\beta = 100$

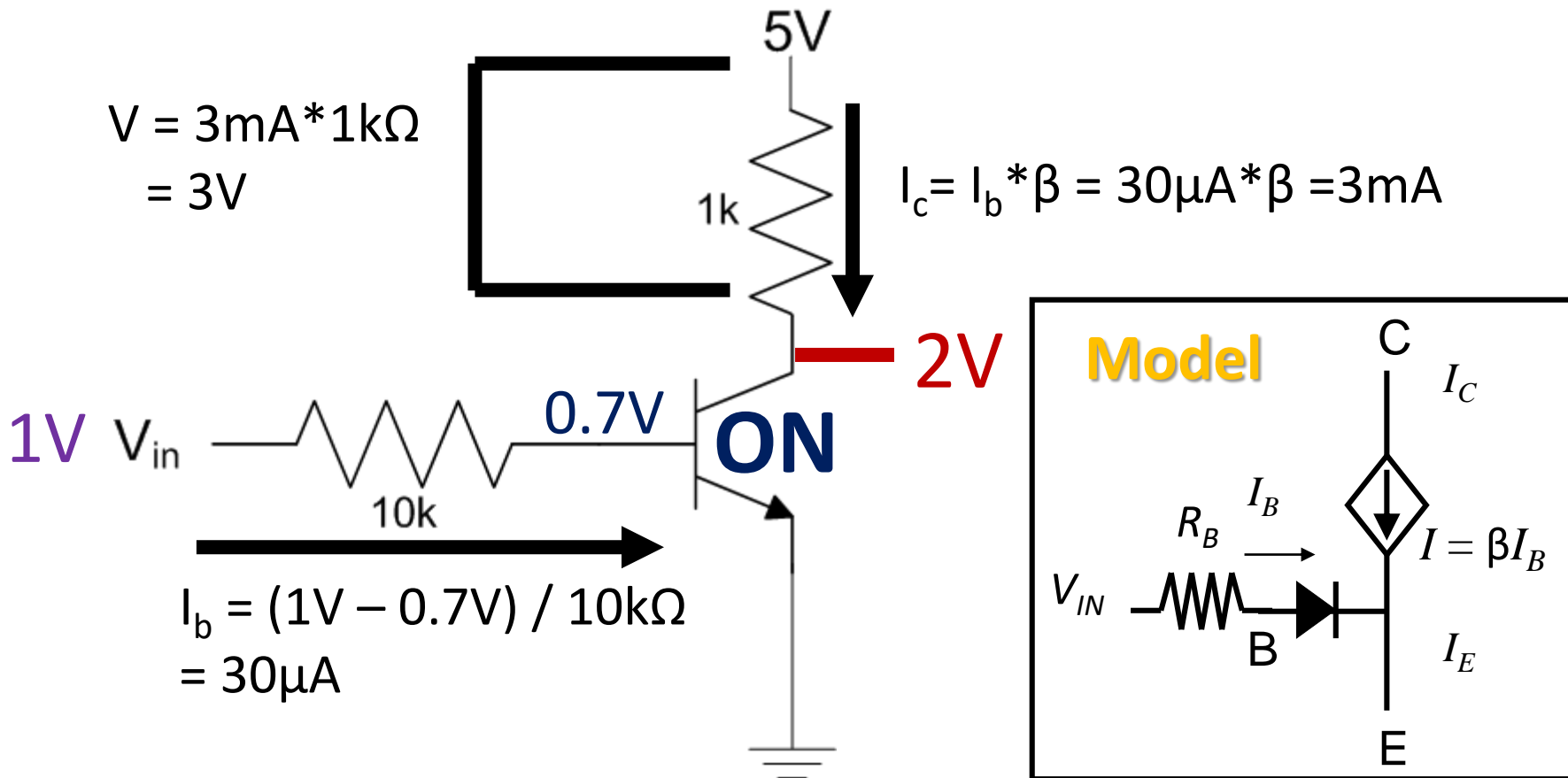


Transistor analysis

❖ How about if $V_{in} = 5V$?




Turn on voltage $V_{be} = 0.7$

Current Gain $\beta = 100$

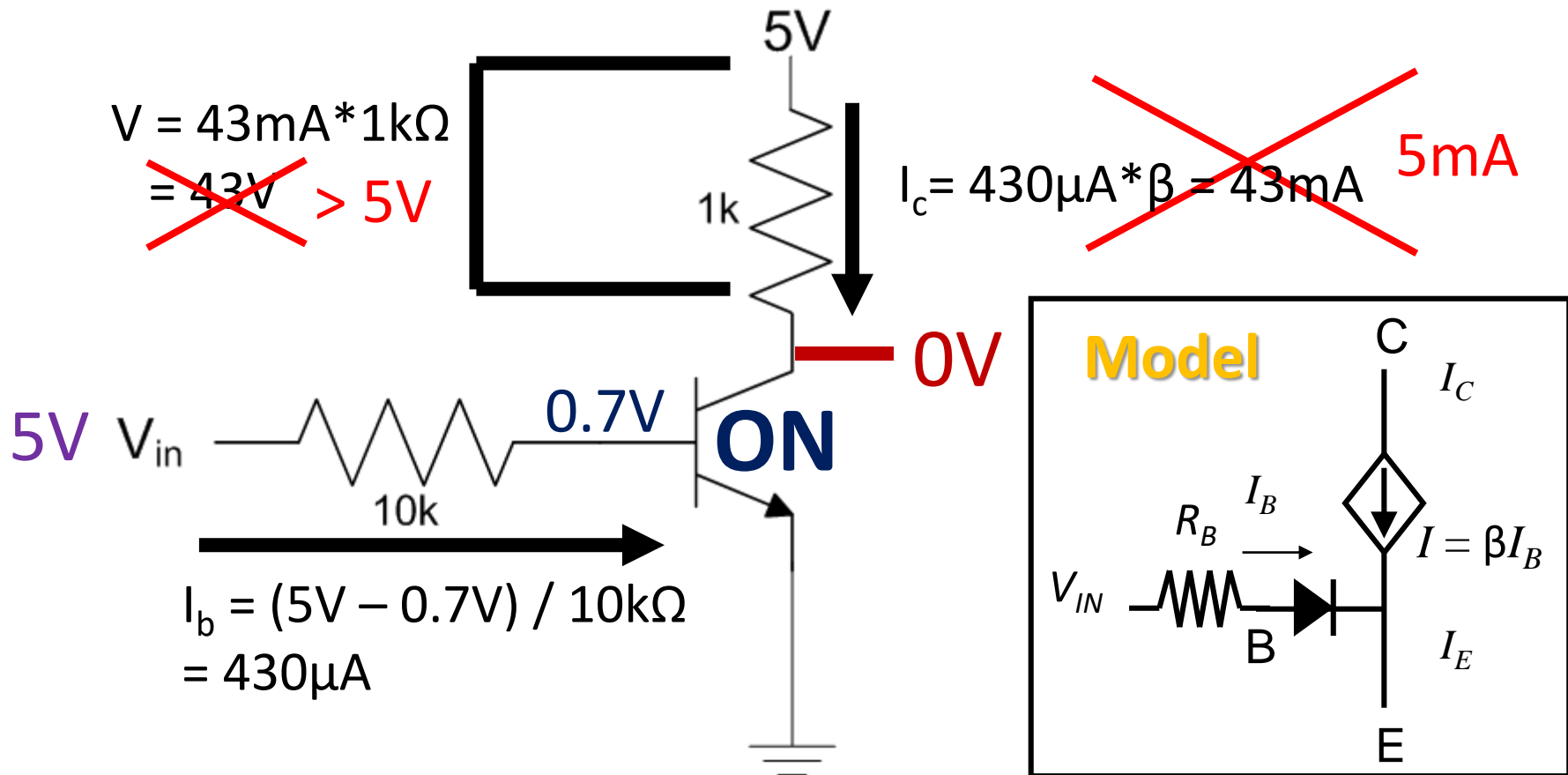


Breadboard Time!

Lab#04: Simulation 1

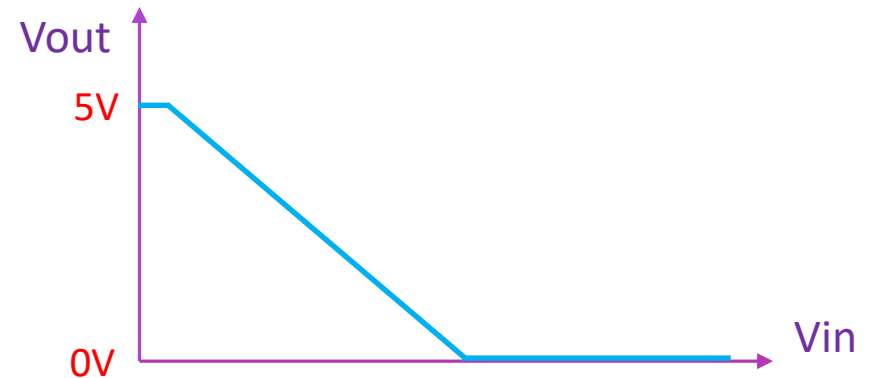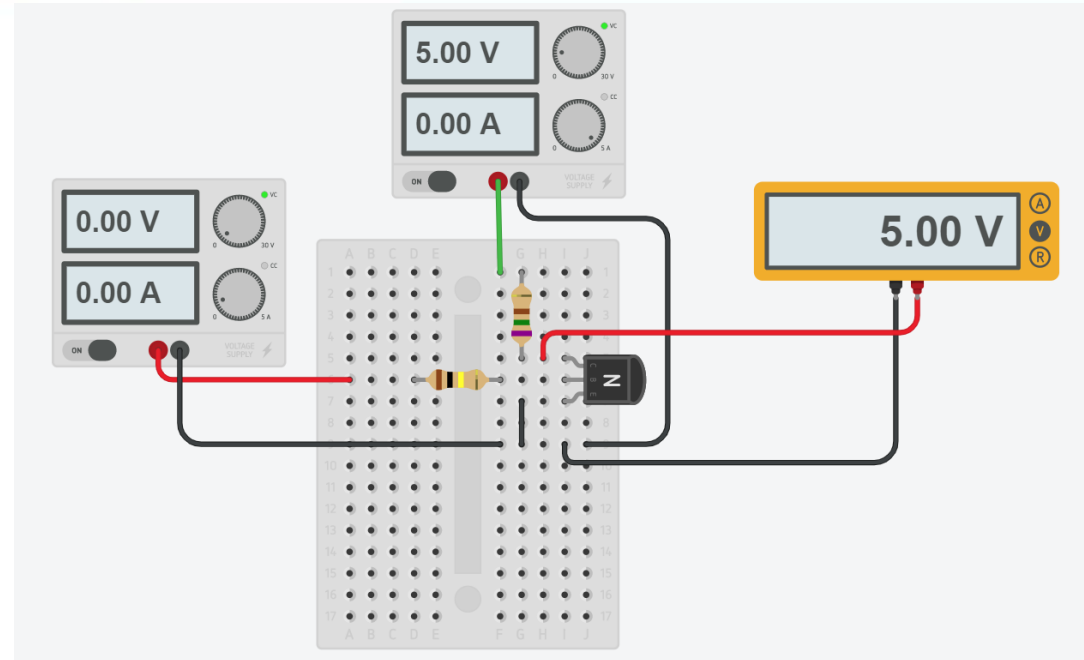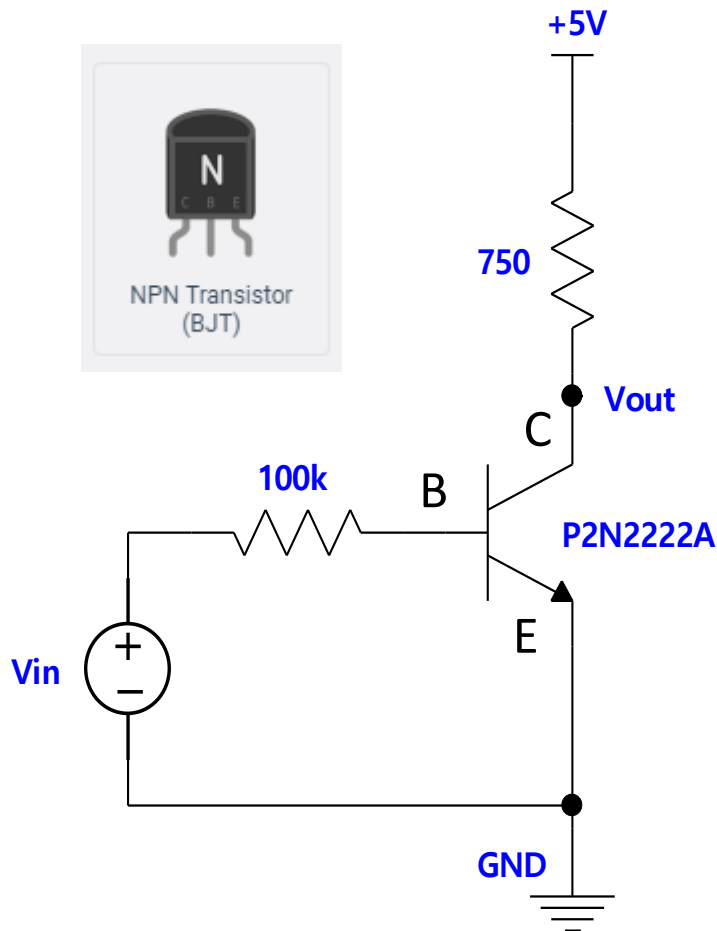

H-bridge





Lab#04: Simulation 2

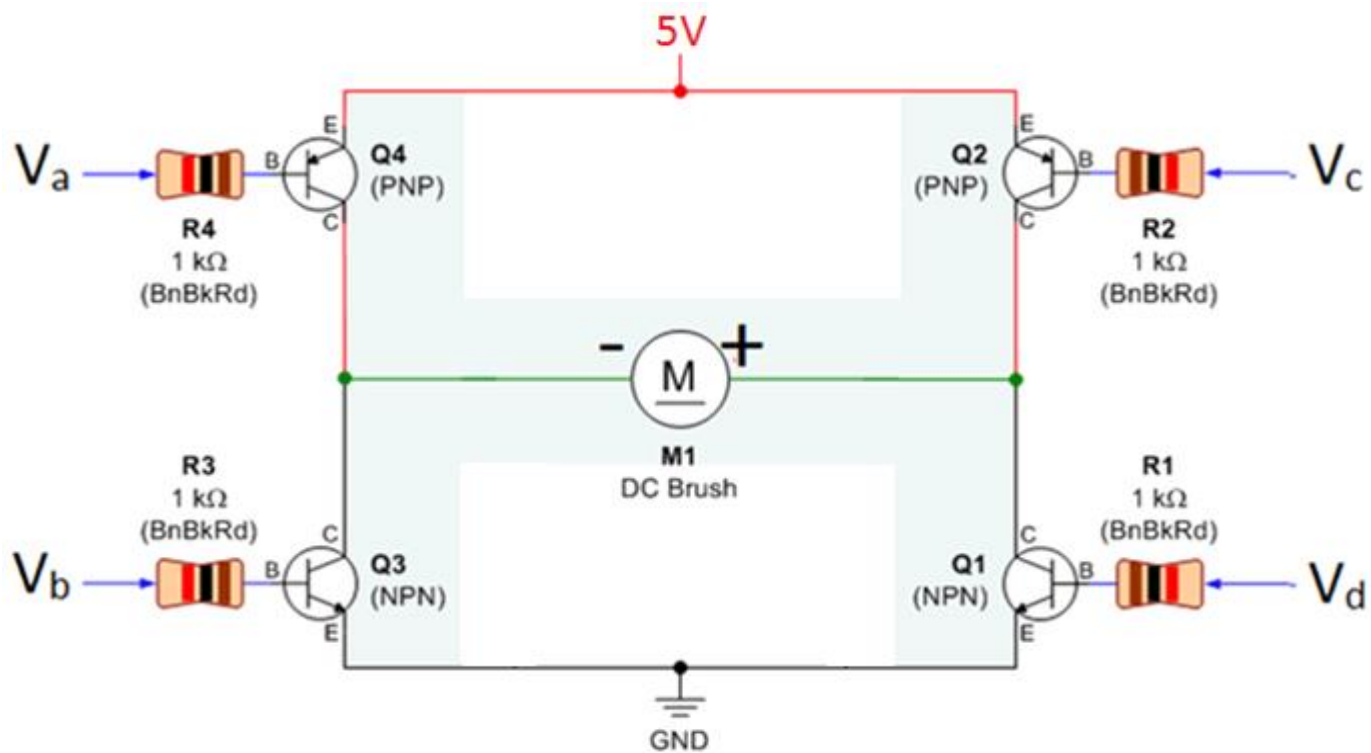

- $V_a = ?$ $V_b = ?$ $V_c = ?$ $V_d = ?$

H-bridge Motor Driver


Lab#04: Simulation 2

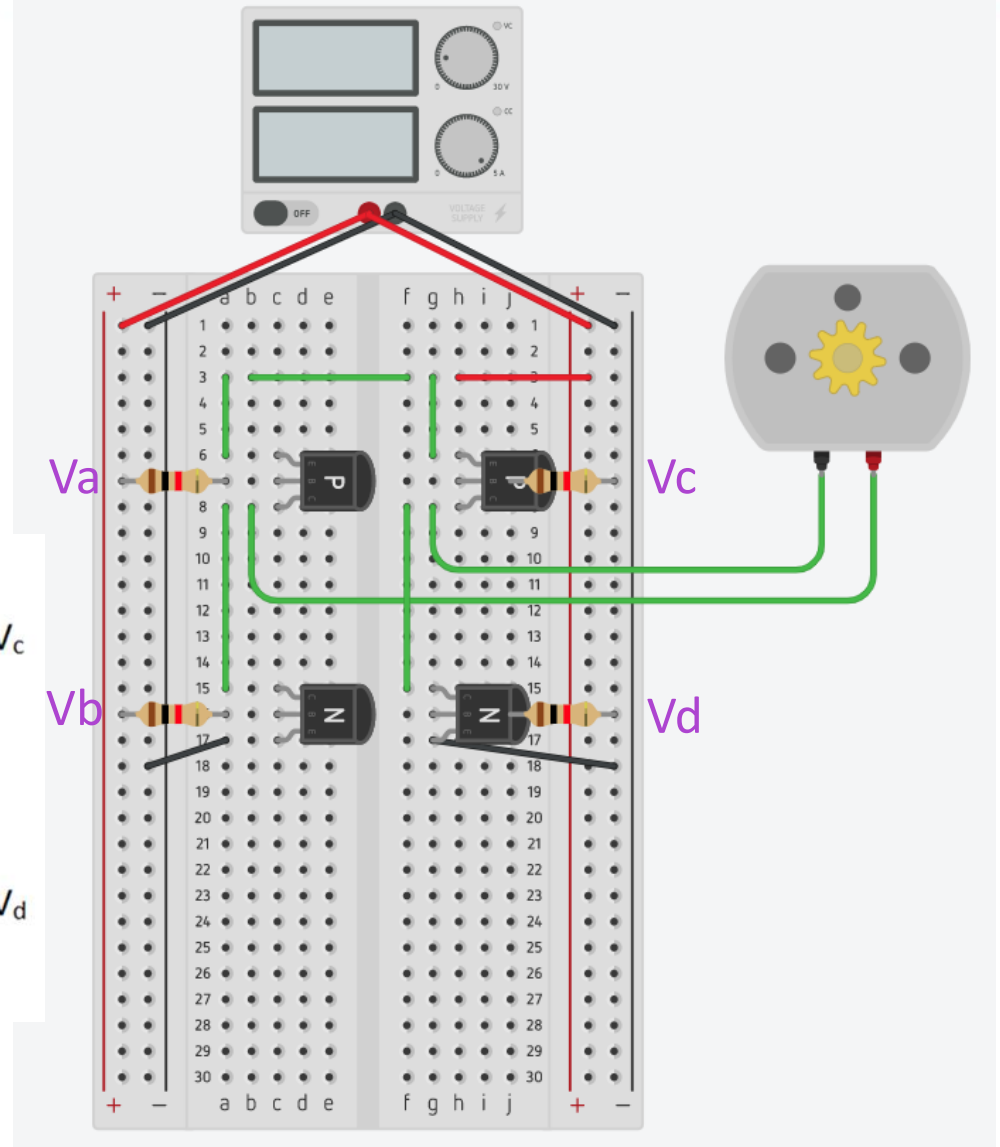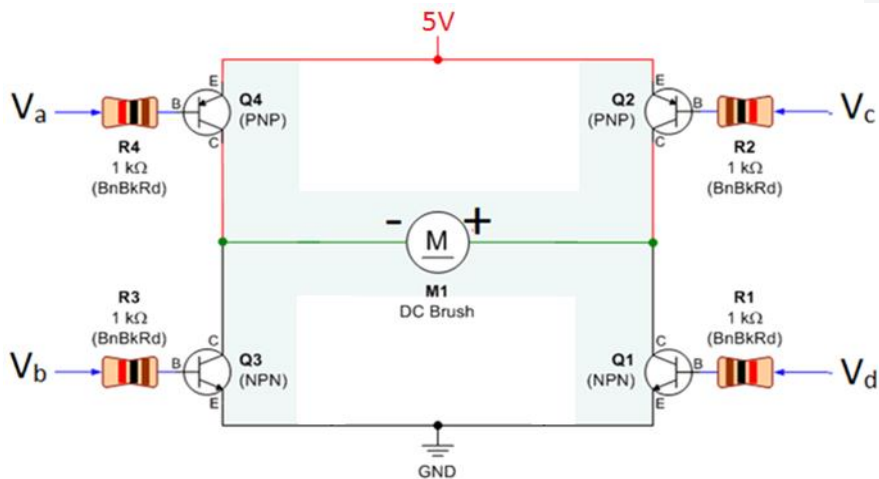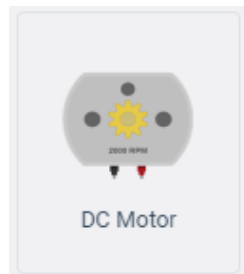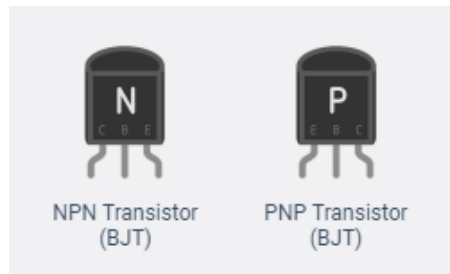


L293D Motor Driver Circuit

Lab#04: Simulation 3

LM7805 DC Regulator

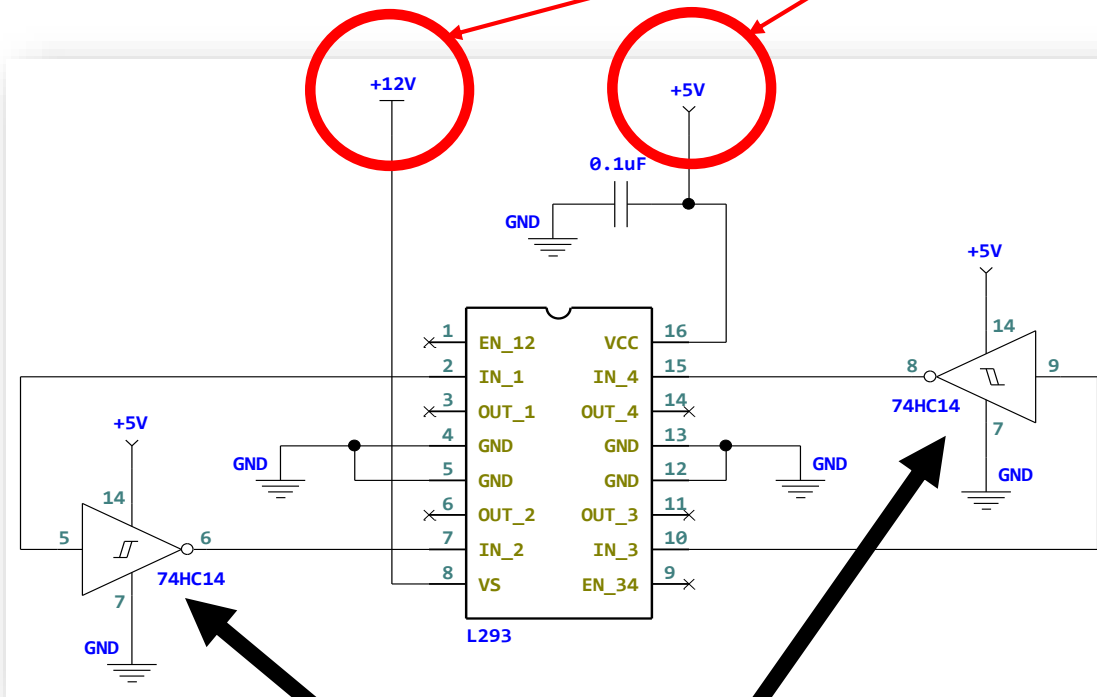


74HC14
(Schmitt Trigger from Lab#03)

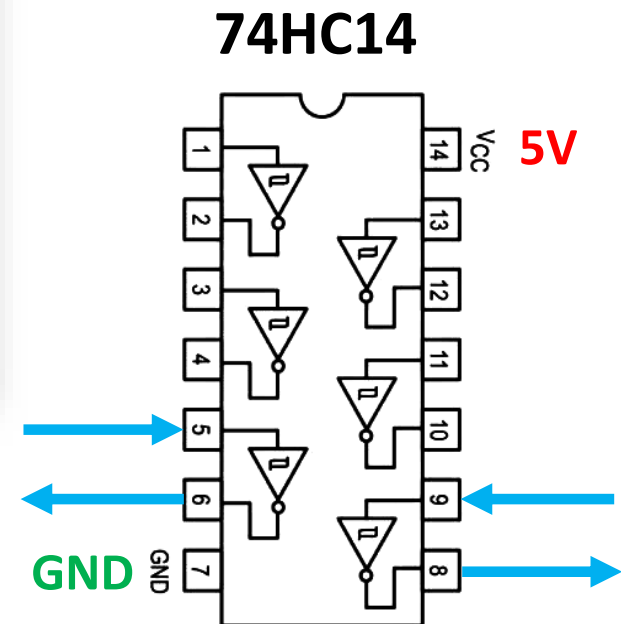


L293D Motor Driver Circuit

Lab#04: Simulation 3

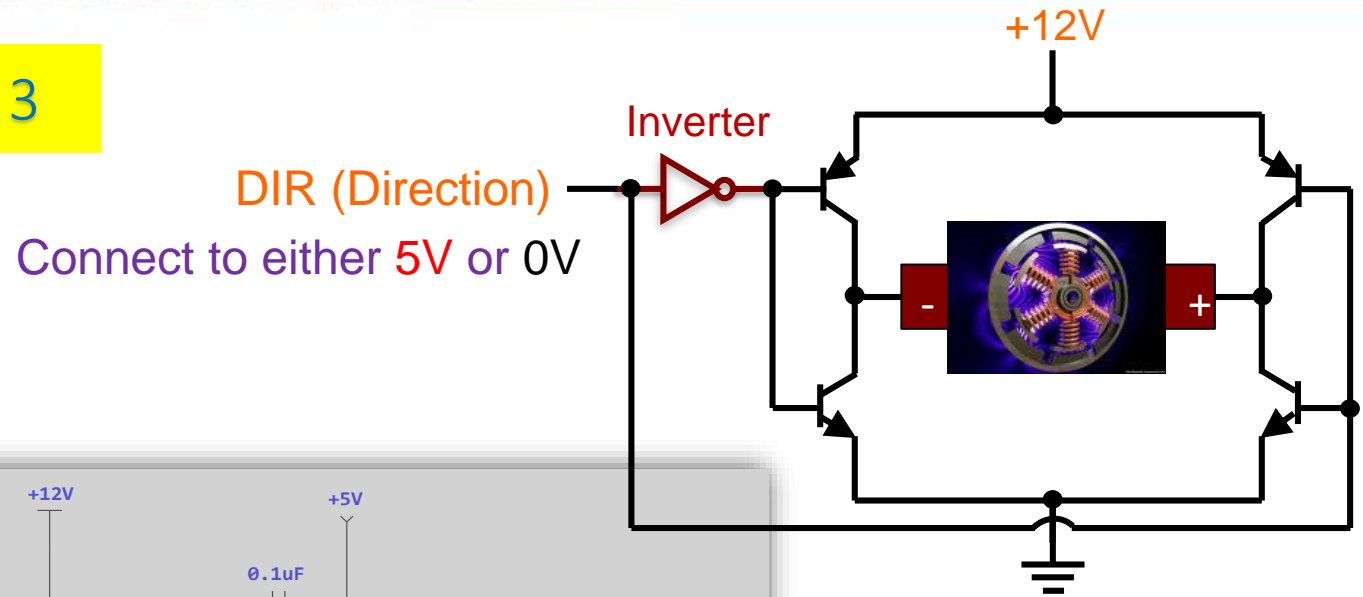

L_DIR

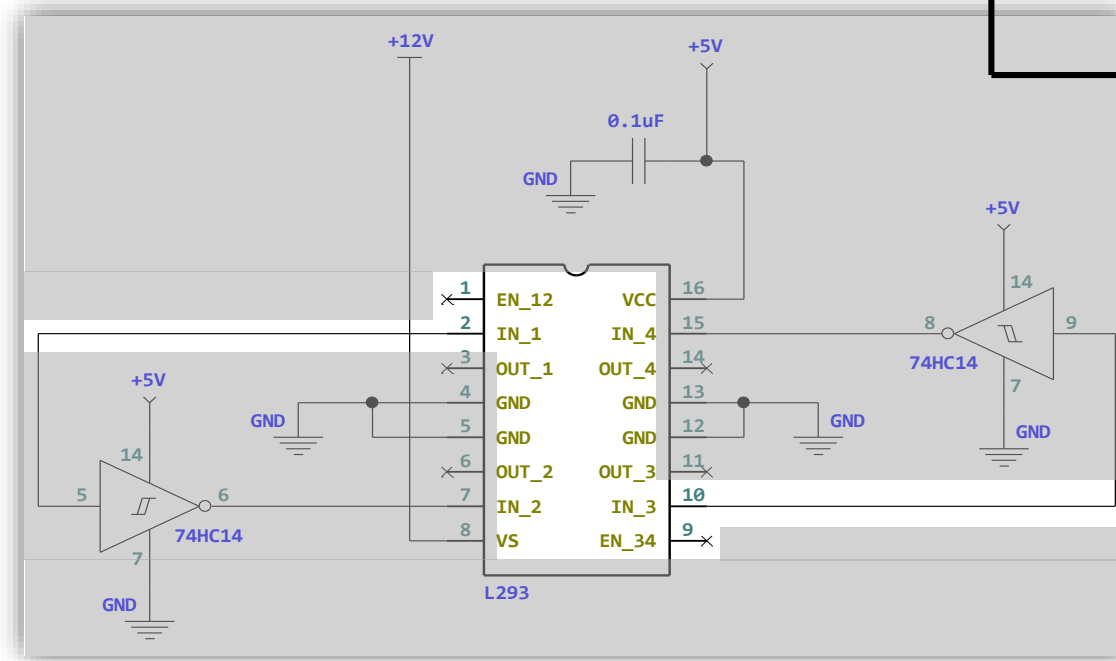

R_DIR



L293D Motor Driver Circuit

Lab#04: Simulation 3

