


- DC Analysis

- AC Analysis


(Sinusoidal Steady state Analysis)


} *Different ?*

DC analysis

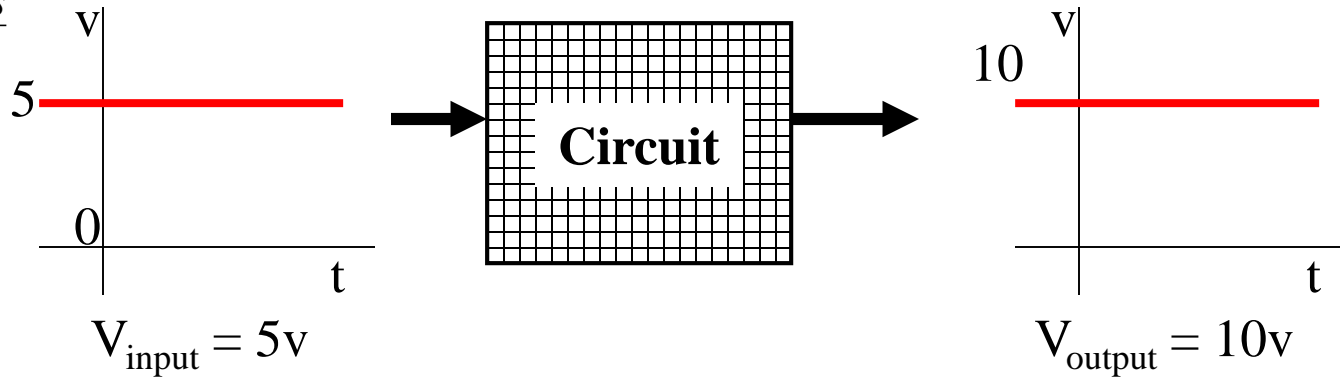


AC analysis

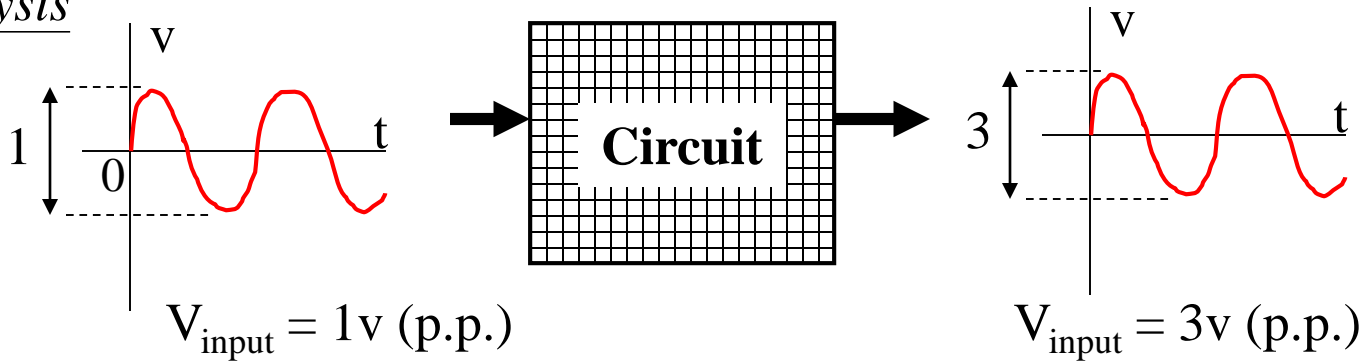


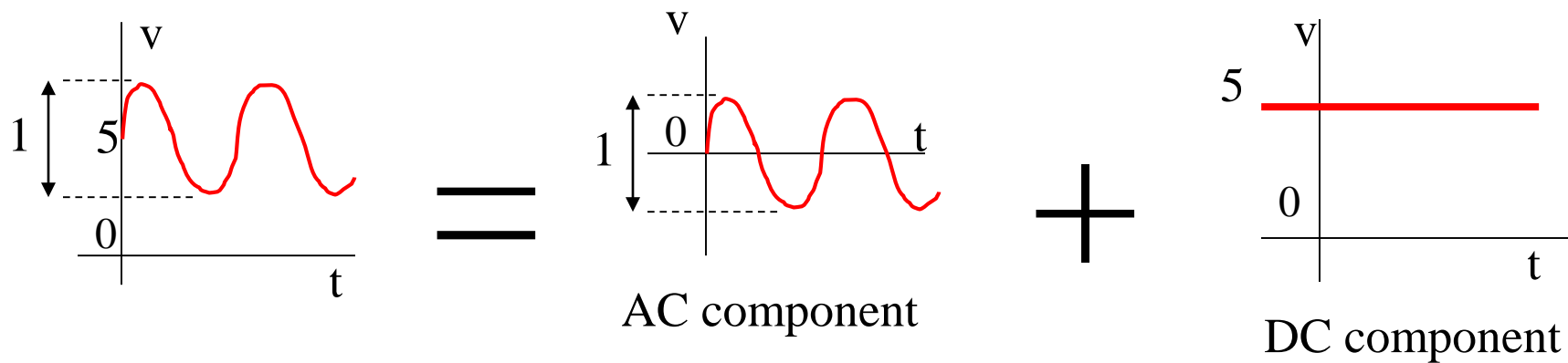

Ex.

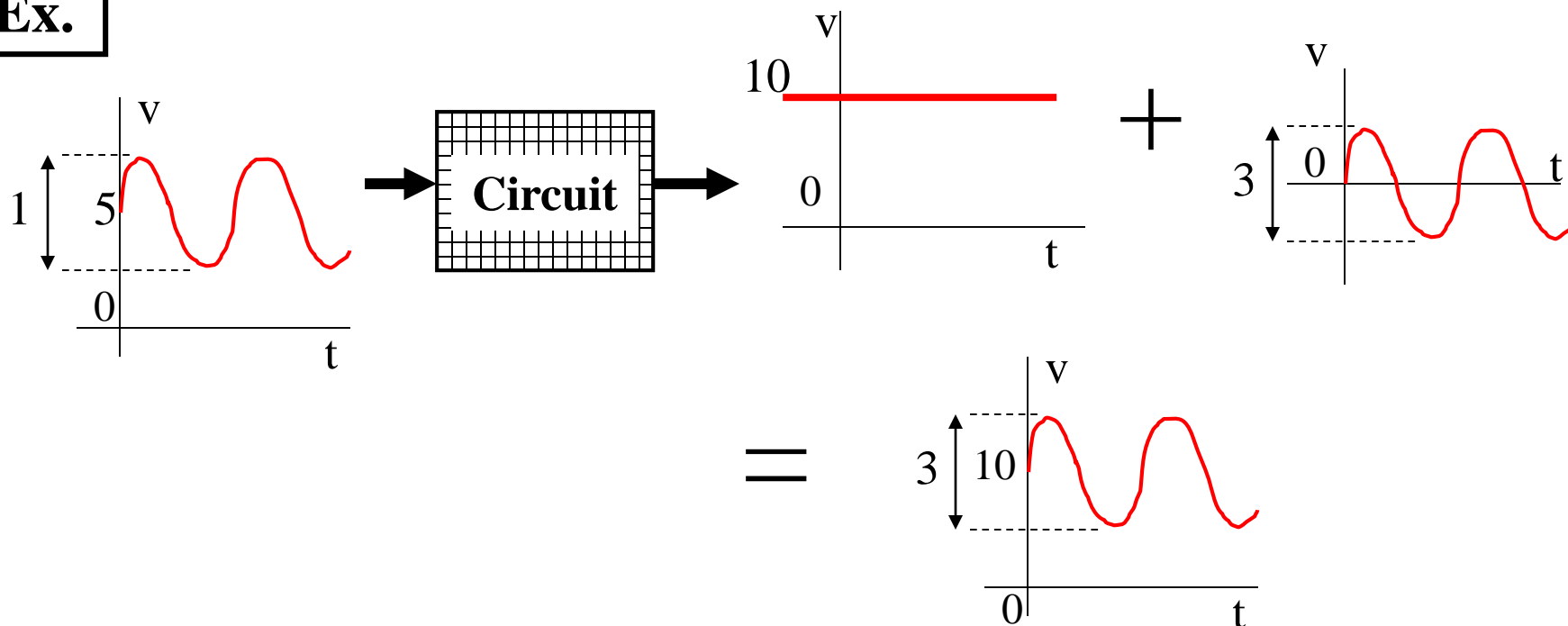

AC analysis

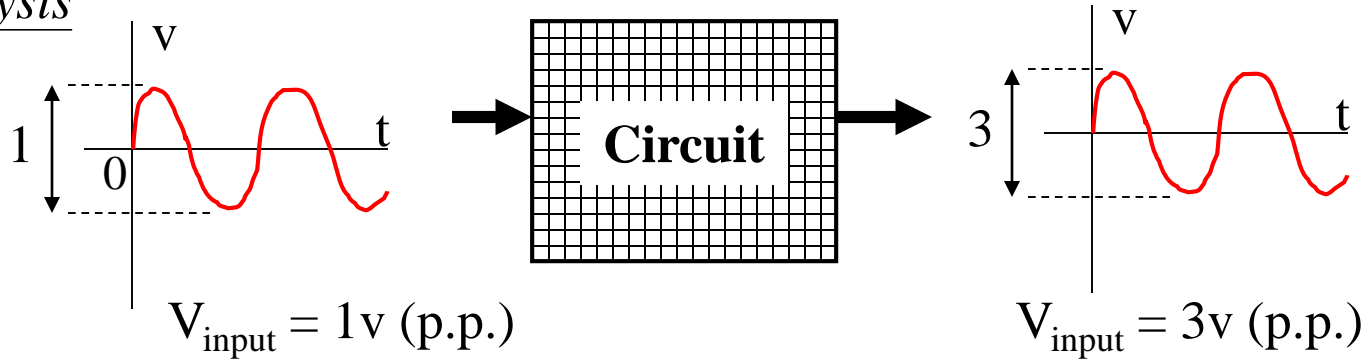


AC Analysis

Input Source

- sin wave [e.g. $\sin(100t)$]
- cos wave [e.g. $\cos(100t)$]
- triangular wave
- square wave

We only need to consider sin/cos (sinusoidal) wave in AC analysis.


Euler's Identity

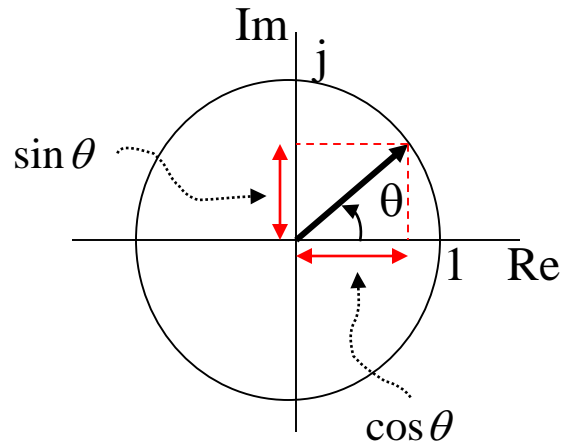

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$|e^{j\theta}| = 1$$

$$|\cos \theta + j \sin \theta| = \sqrt{\cos^2 \theta + \sin^2 \theta} = 1$$

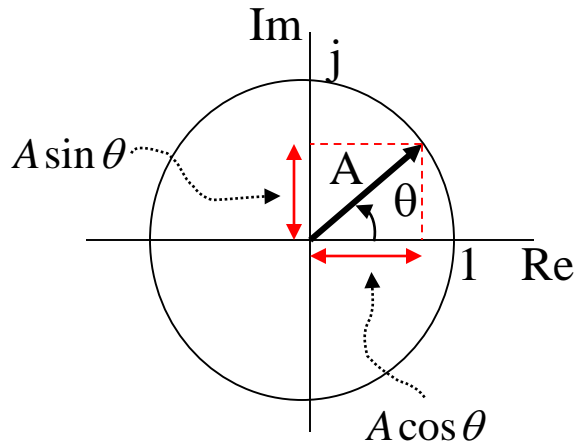

$$Ae^{j\theta} = A \cos \theta + jA \sin \theta = A \angle \theta$$

Rectangular form

Polar form

$$\sin \omega t = \cos(\omega t - 90^\circ)$$

$$\cos \omega t = \sin(\omega t + 90^\circ)$$

$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta$$

$$\omega = 2\pi f \quad e^{\pm j\pi} = -1$$

$$a + jb = \left(\sqrt{a^2 + b^2} \right) * e^{j(\tan^{-1} b/a)}$$

$$j = \frac{1}{-j} \quad (-j)(j) = 1$$

Addition (Subtraction)

$$n_1 = 8 + j16$$

$$n_2 = 12 - j3$$

$$n_1 + n_2 = (8 + 12) + j(16 - 3) = 20 + j13$$

$$n_1 - n_2 = (8 - 12) + j(16 - (-3)) = -4 + j19$$

Addition (Subtraction)

$$n_1 = 5\angle 18.3^\circ \qquad n_2 = 12\angle 115^\circ$$

$$\begin{aligned} n_1 + n_2 &= (4.75 + j1.57) + (-5.07 + j10.88) \\ &= -0.32 + j12.45 \\ &= 12.45\angle 91.47^\circ \end{aligned}$$

$$\begin{aligned} n_1 - n_2 &= (4.75 + j1.57) - (-5.07 + j10.88) \\ &= 9.82 - j9.31 \\ &= 13.53\angle -43.47^\circ \end{aligned}$$

Multiplication

$$n_1 = 4 + j5$$

$$n_2 = 2 - j3$$

$$\begin{aligned} n_1 n_2 &= (4 + j5)(2 - j3) \\ &= 8 - j12 + j10 + 15 \\ &= 23 - j2 \\ &= 23.09 \angle 355^\circ \end{aligned}$$

$$n_1 = 6.4 \angle 51.34^\circ$$

$$n_2 = 3.6 \angle -56.31^\circ$$

$$\begin{aligned} n_1 n_2 &= (6.4 \angle 51.34^\circ)(3.6 \angle -56.31^\circ) \\ &= 23.04 \angle 355^\circ \end{aligned}$$

Division

$$n_1 = 4 + j5$$

$$n_2 = 2 - j3$$

$$\begin{aligned}\frac{n_1}{n_2} &= \frac{4 + j5}{2 - j3} = \frac{(4 + j5)(2 + j3)}{(2 - j3)(2 + j3)} \\ &= \frac{8 + j12 + j10 - 15}{4 + 9} \\ &= -0.54 + j1.69\end{aligned}$$

$$= 1.78 \angle 107.6^\circ$$

$$n_1 = 6.4 \angle 51.34^\circ$$

$$n_2 = 3.6 \angle 303.7^\circ$$

$$\begin{aligned}\frac{n_1}{n_2} &= \frac{6.4 \angle 51.34^\circ}{3.6 \angle 303.7^\circ} \\ &= 1.78 \angle -252.36^\circ \\ &= 1.78 \angle 107.6^\circ\end{aligned}$$

$Z = \text{Impedance } (\Omega)$

$Y = \text{Admittance (S)} = \frac{1}{Z}$

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

$$V = I * R$$

$$V = I * Z$$

Ex.

$$v_1(t) = 12 \cos(180t - 3.14)$$

$$\text{Frequency (Hz)} = ?$$

$$\omega = 180 = 2\pi f$$

$$f = 28.6 \text{ Hz}$$

Ex.

$$I = 12 \angle 50^\circ \quad R = 4 \Omega$$

use cos function

$$\text{frequency} = 60 \text{ Hz}$$

$$V_R(t) = ?$$

$$V = I * Z = (12 \angle 50^\circ)(4) = 48 \angle 50^\circ$$

$$v(t) = A \cos(\omega t + \theta)$$

$$\omega = 2\pi(60) = 377 \text{ rad/s}$$

$$\theta = 50 / 360 * 2\pi$$

$$v(t) = 48 \cos\left(377t + \frac{50}{360} * 2\pi\right) V$$

$$v(t) = 48 \cos(377t + 50^\circ) V$$

Ex.

$$v_c(t) = 100 \cos(377t + 0.262)$$

$$\mathbf{i}_C(t) = ?$$

$$C = 100 \mu F$$

$$V_C = 100 \angle \left(\frac{0.262}{2\pi} * 360 \right)^\circ = 100 \angle 15^\circ$$

$$Z = \frac{1}{j\omega C} = \frac{1}{j(377)(100 * 10^{-6})} = -j26.525 \Omega$$


$$V_C = I_C * Z_C$$

$$I = \frac{V}{Z} = \frac{100 \angle 15^\circ}{-j26.525} = \frac{100 \angle 15^\circ}{26.525 \angle -90^\circ} = 3.77 \angle 105^\circ$$


$$v(t) = A \cos(\omega t + \theta)$$

$$\mathbf{i}(t) = 3.77 \cos \left(377t + \frac{105}{360} * 2\pi \right)$$

Ex.

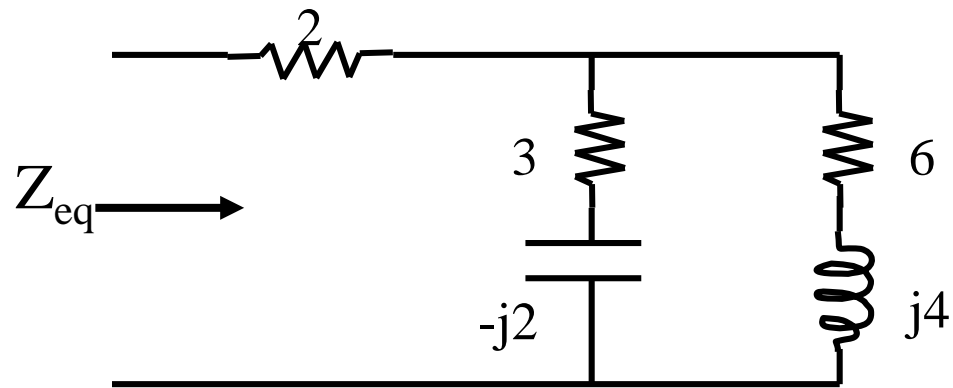


$$Z_{eq} = ?$$

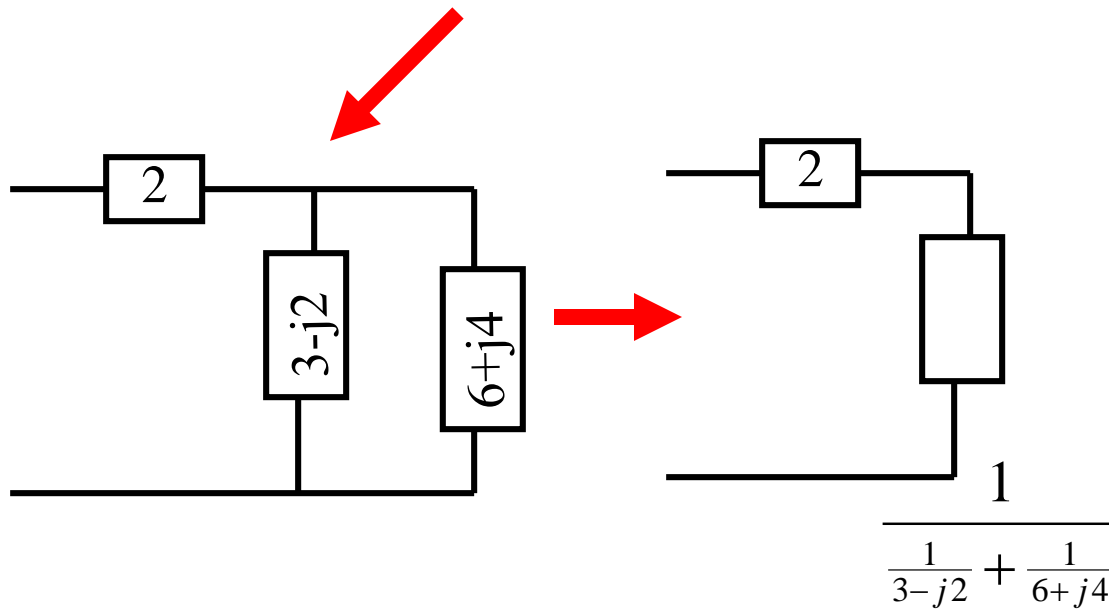

$$Z_{eq} = 2 + \frac{1}{\frac{1}{3-j2} + \frac{1}{6+j4}}$$
$$= 4.79 \angle -7.33^\circ$$

Ex.

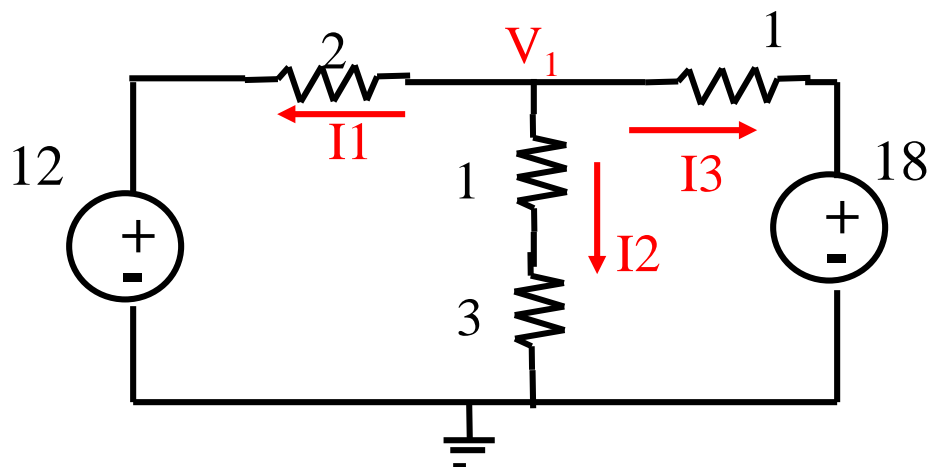

$I_1, I_2, I_3 = ?$


$$\frac{V_1 - 12}{2} + \frac{V_1 - 0}{4} + \frac{V_1 - 18}{1} = 0 \quad \Rightarrow \quad V_1 = 13.714$$

$$I_1 = \frac{13.714 - 12}{2} = 0.857$$

$$I_2 = \frac{13.714 - 0}{4} = 3.429$$

$$I_3 = \frac{13.714 - 18}{1} = -4.286$$

Ex.

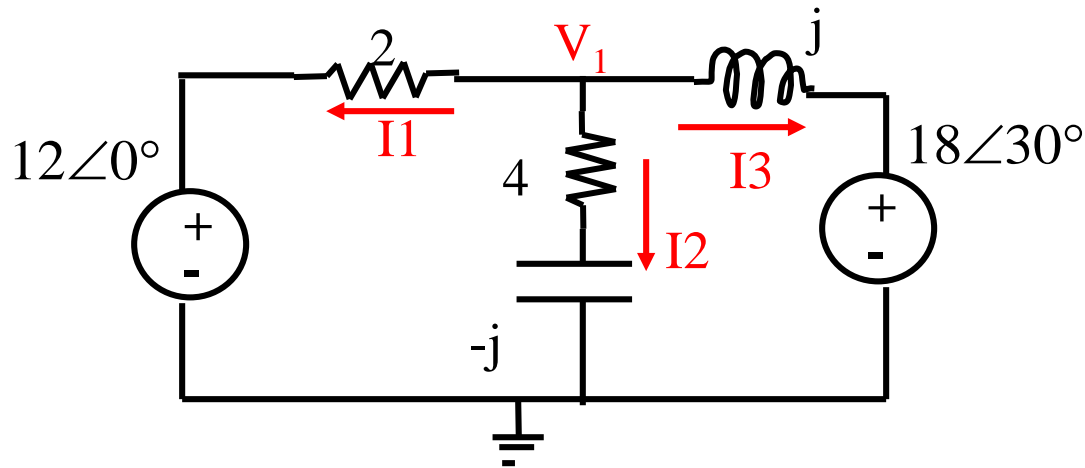

$I_1, I_2, I_3 = ?$

$$\frac{V_1 - 12\angle 0}{2} + \frac{V_1 - 0}{4 - j} + \frac{V_1 - 18\angle 30}{j} = 0 \Rightarrow V_1 = 18.11\angle 5.9^\circ$$

$$I_1 = \frac{18.11\angle 5.9 - 12\angle 0}{2} = 3.14\angle 17.2^\circ$$

$$I_2 = \frac{18.11\angle 5.9 - 0}{4 - j} = 4.39\angle 19.84^\circ$$

$$I_3 = \frac{18.11\angle 5.9 - 18\angle 30}{j} = 7.54\angle -161.2^\circ$$
