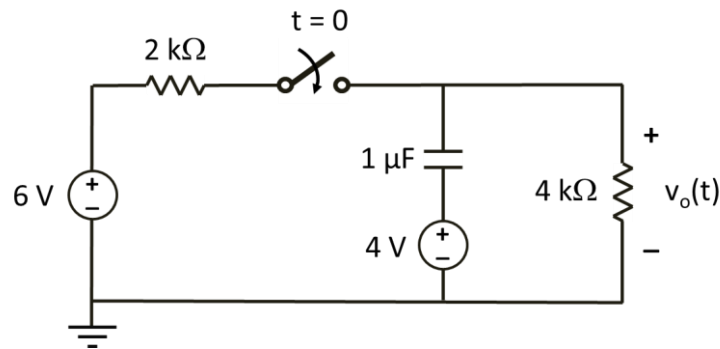




HOMEWORK 5 SOLUTION

- Q1. Assume the switch has been open for a long time. The switch is closed at $t = 0$. Find the equation of the voltage $v_o(t)$ for $t > 0$.



In the steady state up to $t = 0^-$, the capacitor behaves like an open circuit. No current goes through the 4-k Ω resistor. Hence, $v_o(0^-) = 0$ V.

At $t = 0^+$, the capacitor voltage is unchanged. Same is true for the 4-V source. Hence, $v_o(0^+) = v_o(0^-) = 0$ V.

In the steady state when $t \rightarrow \infty$, the capacitor behaves like an open circuit again.

$$v_o(\infty) = 6 \left(\frac{4}{2 + 4} \right) = 4 \text{ V}$$


Time constant:

$$\tau = R_{eq}C = (2\text{k}||4\text{k})1\mu = 1.333 \text{ ms}$$

Therefore, for $t > 0$

$$v_o(t) = 0 + (4 - 0) \left(1 - e^{-\frac{t}{1.333\text{m}}} \right) = 4(1 - e^{-750t}) \text{ V}$$

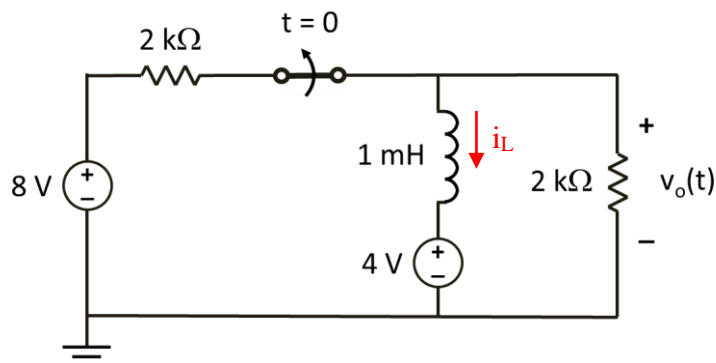- Q2. Assume the switch has been closed for a long time. The switch is opened at $t = 0$. Find the equation of the voltage $v_o(t)$ for $t > 0$.



In the steady state up to $t = 0^-$, the inductor behaves like a short circuit. Hence, $v_o(0^-) = 4$ V. Furthermore, KCL at the node v_o yields $i_L(0^-) = 0$ A.

At $t = 0^+$, the inductor current is unchanged. Hence, $i_L(0^+) = i_L(0^-) = 0$ A. Moreover, the switch is already opened. There is no current going through the 2-k Ω resistor on the right and $v_o(0^+) = 0$ V.

In the steady state when $t \rightarrow \infty$, the inductor behaves like a short circuit again and $v_o(\infty) = 4$ V.

Time constant: only the 2-k Ω resistor on the right takes part in the transient.

$$\tau = L/R_{eq} = 1\text{m}/2\text{k} = 0.5 \mu\text{s}$$


Therefore, for $t > 0$

$$v_o(t) = 0 + (4 - 0) \left(1 - e^{-\frac{t}{0.5\mu}} \right) = 4(1 - e^{-2000000t}) \text{ V}$$

Q3. Assume the switch has been open for a long time. The switch is closed at $t = 0$.


(a) Find the equation of the voltage $v_1(t)$ for $t > 0$.

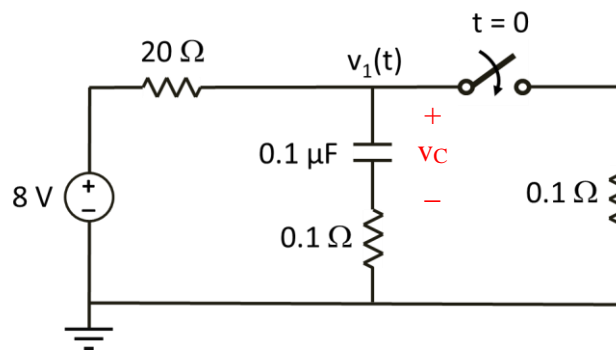(b) Plot $v_1(t)$ as a function of time starting from $t < 0$.



In the steady state up to $t = 0^-$, the capacitor behaves like an open circuit. No current goes through any resistor. Hence, $v_1(0^-) = v_C(0^-) = 8$ V.

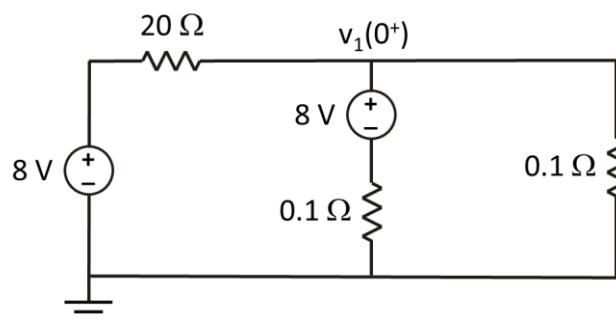At $t = 0^+$, the capacitor voltage is unchanged. Hence, $v_C(0^+) = v_C(0^-) = 8$ V. The capacitor behaves momentarily as an 8-V battery and the following circuit diagram applies



Apply KCL to the node v_1 ,

$$\frac{v_1 - 8}{20} + \frac{v_1 - 8}{0.1} + \frac{v_1}{0.1} = 0$$

$$v_1 - 8 + 200v_1 - 1600 + 200v_1 = 0$$

$$401v_1 = 1608$$

$$v_1(0^+) = 4.0100 \text{ V}$$

In the steady state when $t \rightarrow \infty$, the capacitor behaves like an open circuit again.

$$v_1(\infty) = 8 \left(\frac{0.1}{20 + 0.1} \right) = 0.0398 \text{ V}$$


Time constant:

$$\tau = R_{eq}C = (0.1 + 20 || 0.1)0.1\mu = 0.01995 \mu\text{s}$$

Therefore, for $t > 0$

$$v_1(t) = 0.0398 + (4.0100 - 0.0398)e^{-\frac{t}{0.01995\mu}} = 0.04 + 3.97e^{-50100000t} \text{ V}$$

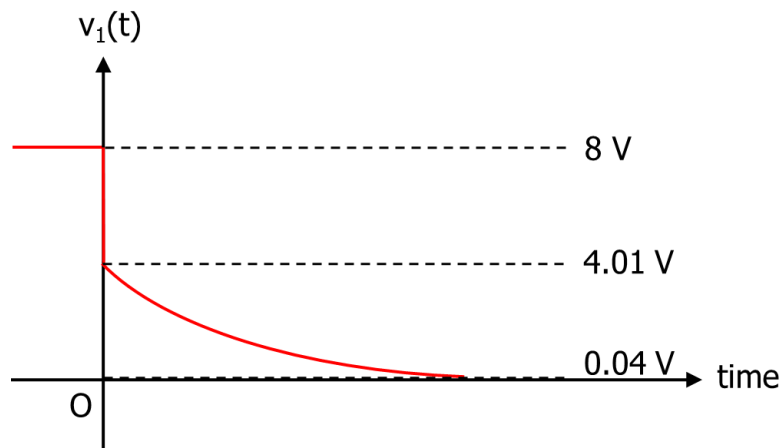
Following is a plot of $v_1(t)$ starting from $t < 0$.



Q4. Assume the switch has been open for a long time. The switch is closed at $t = 0$.


(a) Find the equation of the current $i_1(t)$ for $t > 0$.

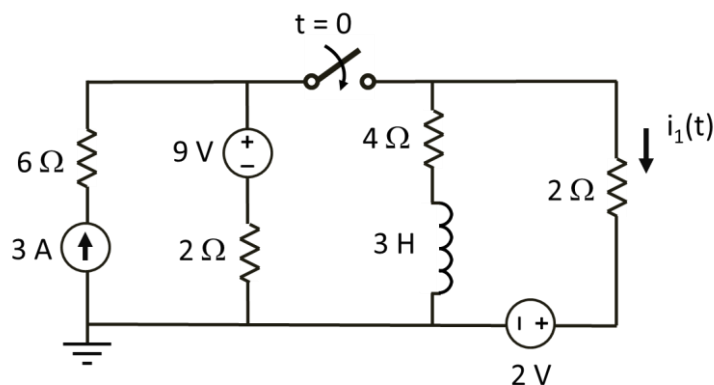(b) Plot $i_1(t)$ as a function of time starting from $t < 0$.



In the steady state up to $t = 0^-$, the inductor behaves like a short circuit. Hence, $i_1(0^-) = -2/6 = -0.3333 \text{ A}$.

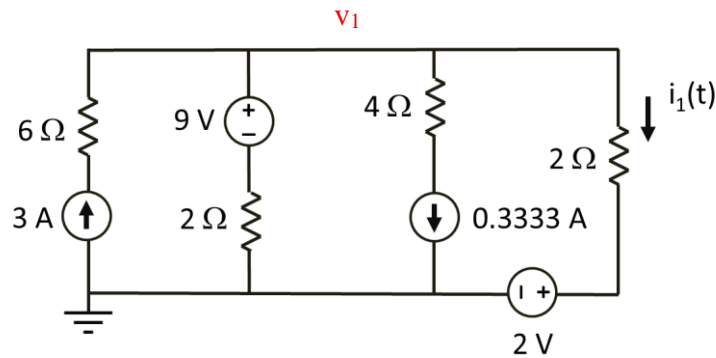
At $t = 0^+$, the inductor current is unchanged. The inductor behaves momentarily as a 0.3333-A current source and the following circuit diagram applies



Apply KCL to the node v_1 , noting that $v_1 = 2i_1 + 2$,

$$\begin{aligned} -3 + \frac{(2i_1 + 2) - 9}{2} + 0.3333 + i_1 &= 0 \\ -6 + 2i_1 + 2 - 9 + 0.6667 + 2i_1 &= 0 \\ 4i_1 &= 12.3333 \\ i_1(0^+) &= 3.083\text{ A} \end{aligned}$$

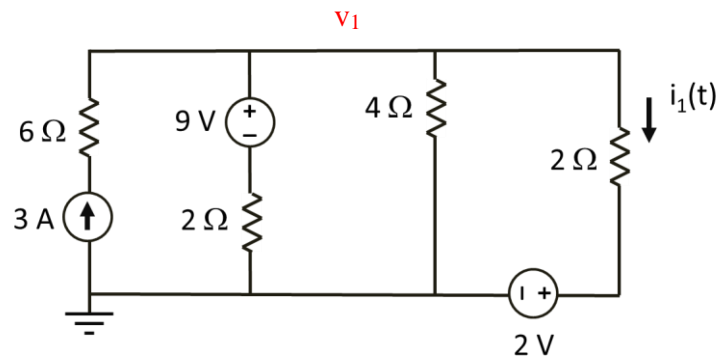In the steady state when $t \rightarrow \infty$, the inductor behaves like a short circuit again and the following circuit diagram applies



Apply KCL to the node v_1 , noting that $v_1 = 2i_1 + 2$,

$$\begin{aligned} -3 + \frac{(2i_1 + 2) - 9}{2} + \frac{2i_1 + 2}{4} + i_1 &= 0 \\ -12 + 4i_1 + 4 - 18 + 2i_1 + 2 + 4i_1 &= 0 \\ 10i_1 &= 24 \\ i_1(\infty) &= 2.4\text{ A} \end{aligned}$$


Time constant: the $6\text{-}\Omega$ resistor is open-circuited by the zeroed-out current source in the R_{eq} calculation.

$$\tau = L/R_{eq} = 3/(4 + 2||2) = 3/(4 + 1) = 0.6\text{ s}$$

Therefore, for $t > 0$


$$i_1(t) = 2.4 + (3.083 - 2.4)e^{-\frac{t}{0.6}} = 2.4 + 0.683e^{-1.67t} \text{ V}$$

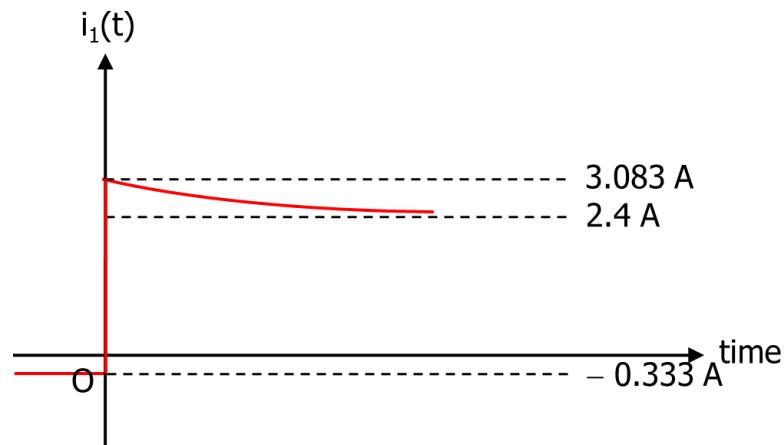Following is a plot of $i_1(t)$ starting from $t < 0$.



Q5. Find V_o and I_o in the circuit below with

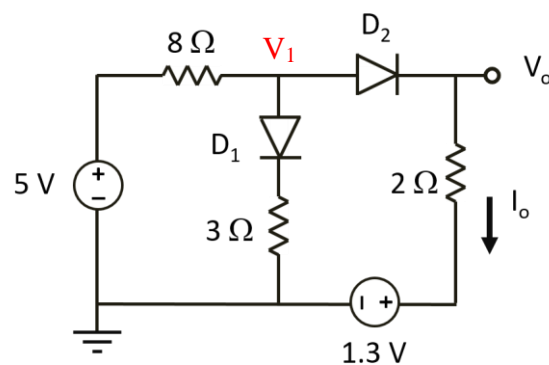- (i) ideal diode model,
- (ii) offset diode model ($V_F = 0.5 \text{ V}$).



- (i) Assume both diodes are ON. KCL at the node V_1 yields

$$\frac{V_1 - 5}{8} + \frac{V_1}{3} + \frac{V_1 - 1.3}{2} = 0$$

$$3V_1 - 15 + 8V_1 + 12V_1 - 15.6 = 0$$


$$23V_1 = 30.6$$

$$V_1 = 1.3304 \text{ V} = V_o$$

$$I_o = \frac{V_o - 1.3}{2} = \frac{1.3304 - 1.3}{2} = 0.0152 \text{ A} > 0$$

The results for V_1 , V_o and I_o are consistent with both diodes being ON.

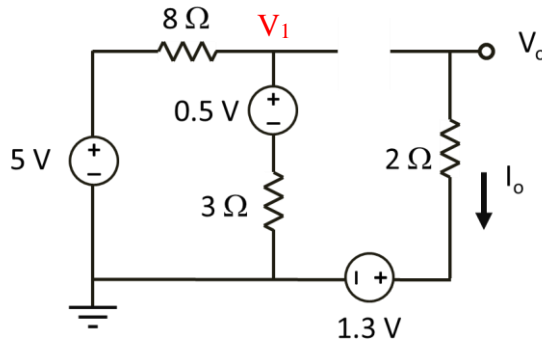- (ii) Assume D_1 ON and D_2 OFF. The circuit diagram looks like this



from which

$$\begin{aligned} V_o &= 1.3 \text{ V} \\ I_o &= 0 \text{ A} \end{aligned}$$

As a check, apply KCL to the node V_1 ,

$$\frac{V_1 - 5}{8} + \frac{V_1 - 0.5}{3} = 0$$


$$3V_1 - 15 + 8V_1 - 4 = 0$$

$$11V_1 = 19 \text{ V}$$

$$V_1 = 1.73 \text{ V} < V_o + V_F$$

This is consistent with D_2 being OFF.

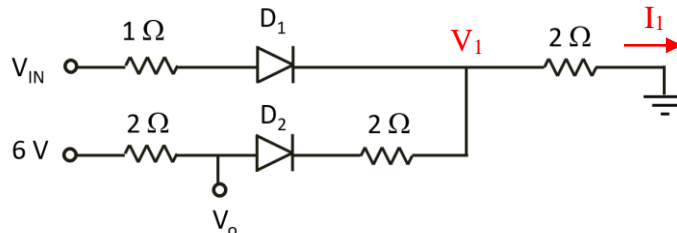- Q6. Plot V_o as a function of V_{IN} for V_{IN} from -5 V to 25 V in the circuit with
- ideal diode model,
 - offset diode model ($V_F = 0.5 \text{ V}$).



Qualitatively speaking, when V_{IN} starts from low, D_1 is OFF and V_1 is set by the 6-V source. When V_{IN} gets high enough, both D_1 and D_2 are ON and V_1 is set by both V_{IN} and the 6-V source. Finally, when V_{IN} gets sufficiently high, D_2 is OFF and V_1 is set by V_{IN} only.

- (i) Ideal diode model:

- (a) When D_1 is OFF and D_2 is ON, $V_o = 4 \text{ V}$ and $V_1 = 2 \text{ V}$. This is true for

$$-5 \text{ V} \leq V_{IN} < 2 \text{ V}$$

- (b) When D_1 is ON and D_2 is OFF, $V_o = 6 \text{ V} < V_1 = 2V_{IN}/3$. This is therefore true for

$$V_{IN} > 6 \times 3/2 = 9 \text{ V}$$

We now have everything we need to do the plot. The following are optional.


(c) $2 \text{ V} \leq V_{IN} \leq 9 \text{ V}$, both diodes are ON. Apply KCL to the node V_1 ,

$$\begin{aligned}\frac{V_1 - V_{IN}}{1} + \frac{V_1 - 6}{4} + \frac{V_1}{2} &= 0 \\ 4V_1 - 4V_{IN} + V_1 - 6 + 2V_1 &= 0 \\ 7V_1 &= 4V_{IN} + 6 \\ V_1 &= \frac{4V_{IN} + 6}{7}\end{aligned}\quad (1)$$

Notice that V_o is the center tap between the 6-V source and V_1 , and also from (1)

$$V_o = \frac{6 + V_1}{2} = \frac{6 + \frac{4V_{IN} + 6}{7}}{2} = \frac{2}{7}V_{IN} + \frac{24}{7}$$

Following is a plot of V_o vs. V_{IN} .

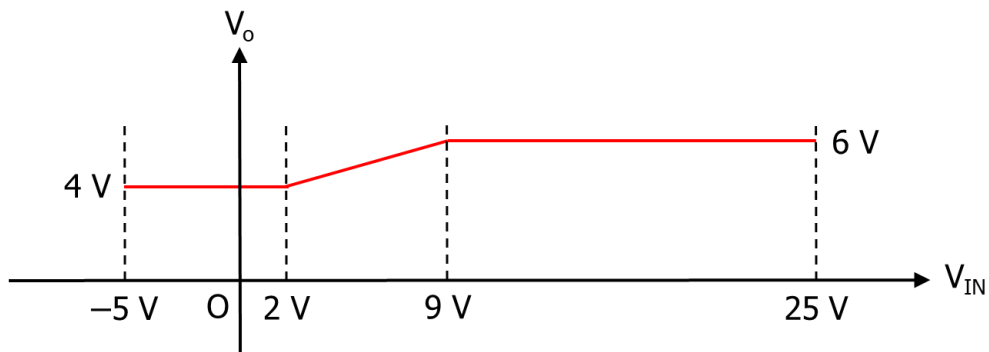

(ii) Offset diode model ($V_F = 0.5 \text{ V}$):

(a) When D_1 is OFF and D_2 is ON,

$$I_1 = \frac{6 - 0.5}{2 + 2 + 2} = 0.9167 \text{ A}$$

yielding

$$V_1 = 2I_1 = 1.833 \text{ V}$$

$$V_o = 6 - 2I_1 = 4.167 \text{ V}$$

This is true for

$$-5 \text{ V} \leq V_{IN} < V_1 + V_F = 1.833 + 0.5 = 2.333 \text{ V}$$

(b) When D_1 is ON and D_2 is OFF,

$$I_1 = \frac{V_{IN} - 0.5}{1 + 2}$$

yielding

$$V_1 = 2I_1 = \frac{2}{3}V_{IN} - \frac{1}{3}$$

This is true for $V_o = 6 \text{ V} < V_1 + V_F$, or


$$\left(\frac{2}{3}V_{IN} - \frac{1}{3}\right) + 0.5 > 6$$

$$2V_{IN} - 1 + 1.5 > 18$$

$$V_{IN} > 8.75 \text{ V}$$

We now have everything we need to do the plot. The following are optional.

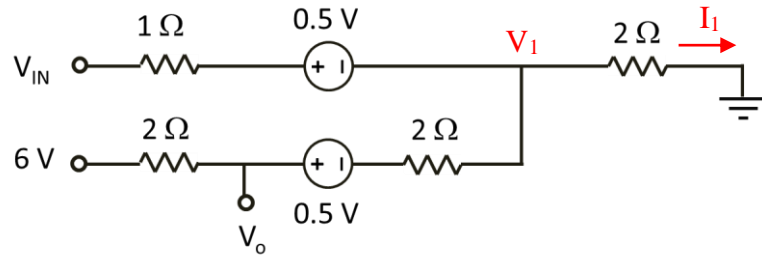(c) For $2.333 \text{ V} \leq V_{IN} \leq 8.75 \text{ V}$, both diodes are ON. The circuit diagram looks like



Apply KCL to the node V_1 ,

$$\frac{V_1 + 0.5 - V_{IN}}{1} + \frac{V_1 + 0.5 - 6}{4} + \frac{V_1}{2} = 0$$

$$4V_1 + 2 - 4V_{IN} + V_1 + 0.5 - 6 + 2V_1 = 0$$

$$7V_1 = 4V_{IN} + 3.5$$

$$V_1 = \frac{4V_{IN} + 3.5}{7} \quad (2)$$

Apply KCL to the node V_o and also from (2)

$$\frac{V_o - 6}{2} + \frac{V_o - 0.5 - V_1}{2} = 0$$


$$V_o - 6 + V_o - 0.5 - \frac{4V_{IN} + 3.5}{7} = 0$$

$$7V_o - 42 + 7V_o - 3.5 - 4V_{IN} - 3.5 = 0$$


$$14V_o = 4V_{IN} + 49$$

$$V_o = 0.2857V_{IN} + 3.5$$

Following is a plot of V_o vs. V_{IN} .

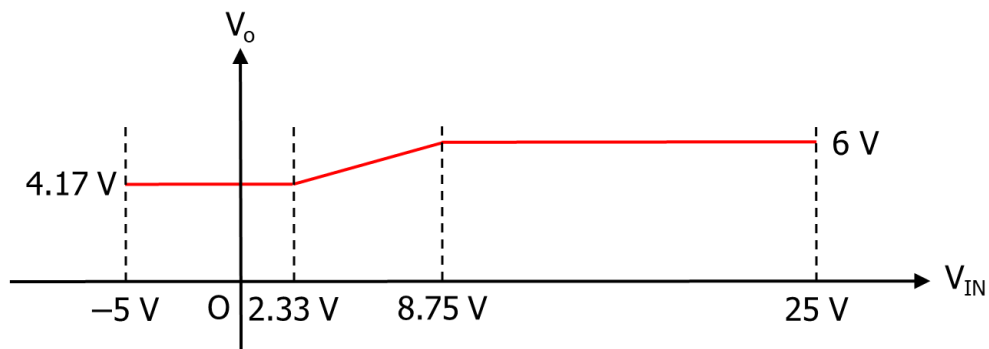

- Q7. In the figure, it shows a Zener diode voltage regulator circuit ($V_{Z0} = 5.6 \text{ V}$, $R_Z = 10 \Omega$).
- (a) Determine the output voltage V_o if $V_{IN} = 6.5 \text{ V}$.
- (b) Plot V_o as the function of V_{IN} for $6 \text{ V} < V_{IN} < 8 \text{ V}$.

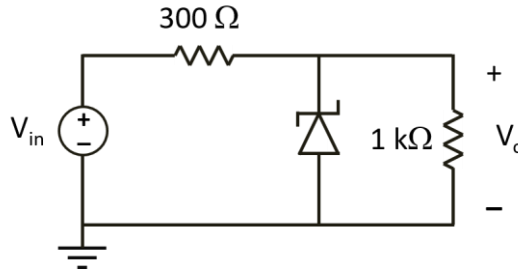

Case 1: Zener diode is OFF

$$V_o = V_{in} \left(\frac{1k}{300 + 1k} \right) = 0.76923V_{in}$$

This is true so long as $V_o < 5.6 \text{ V}$, which means $V_{in} < 7.28 \text{ V}$.


When $V_{in} = 6 \text{ V}$, $V_o = 4.615 \text{ V}$.

When $V_{in} = 6.5 \text{ V}$, $V_o = 5 \text{ V}$.

When $V_{in} = 7.28 \text{ V}$, $V_o = 5.6 \text{ V}$.

Case 2: Zener diode is ON. This happens when $V_o \geq 5.6 \text{ V}$, which means $V_{in} \geq 7.28 \text{ V}$.

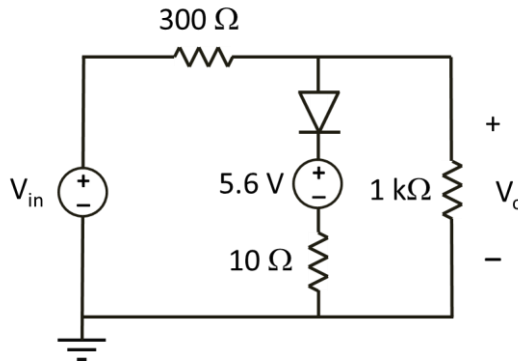Replacing the Zener diode by its circuit model, the circuit now looks like this



Apply KCL to the node V_o ,

$$\frac{V_o}{1k} + \frac{V_o - 5.6}{10} + \frac{V_o - V_{in}}{300} = 0$$


$$3V_o + 300V_o - 1680 + 10V_o - 10V_{in} = 0$$

$$313V_o = 1680 + 10V_{in}$$

$$V_o = 5.367412 + 0.031949V_{in}$$


When $V_{in} = 8 \text{ V}$, $V_o = 5.623 \text{ V}$.

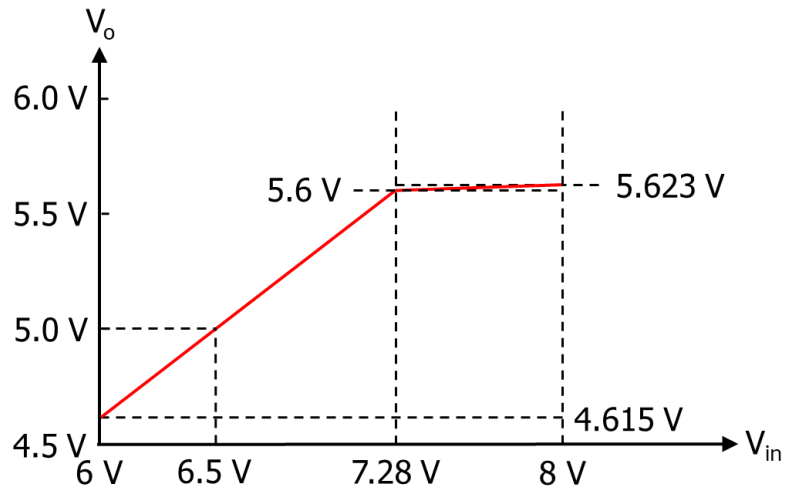Following is a plot of V_o vs. V_{in} . Once $V_o \geq 5.6 \text{ V}$, it is regulated to within a narrow range.




Q8. Find V_o assuming ideal op amp and offset diode model ($V_F = 0.5 \text{ V}$) for the case:

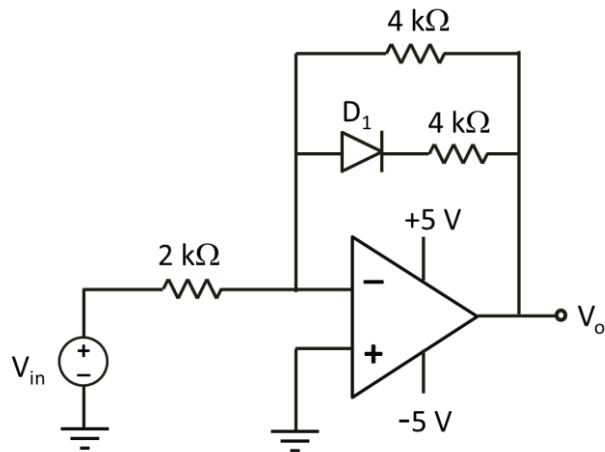- (i) when $V_{in} = 4 \text{ V}$,
- (ii) when $V_{in} = -4 \text{ V}$.



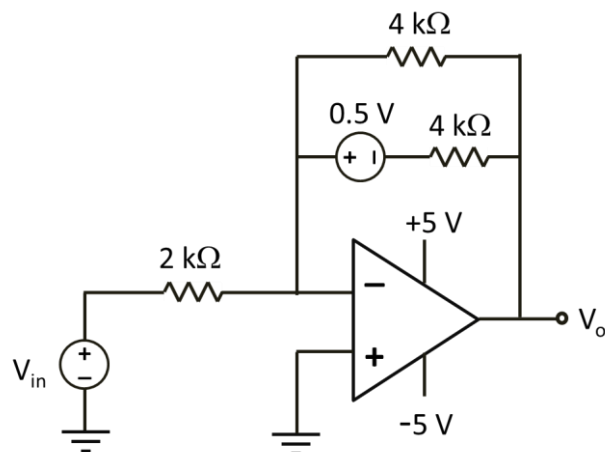(i) when $V_{in} = 4 \text{ V}$, D_1 is ON and the circuit diagram looks like this



Apply KCL to the node V_- , which is equal to V_+ at 0 V.

$$\frac{V_o}{4k} + \frac{V_o + 0.5}{4k} = -\frac{V_{in}}{2k}$$

$$V_o + V_o + 0.5 = -2V_{in}$$

$$V_o = -V_{in} - 0.25 = -4 - 0.25 = -4.25 \text{ V}$$

- (ii) when $V_{in} = -4 \text{ V}$, D_1 is OFF and the circuit is an inverting amplifier with a gain of -2 . Hence, V_o would like to go to 8 V . However, the op amp would be saturated, limiting output to

$$V_o = 5 \text{ V}$$