

Elec 2400 Tutorial



Ricky Choi , eericky@ust.hk

Room 2395

Office Hours : by appointments

- Tutorial Style


C	AB			
	00	01	11	10
0				
1				

Tutorial Notes


C	AB			
	00	01	11	10
0			0	
1		1		

PowerPoint

- DC circuits

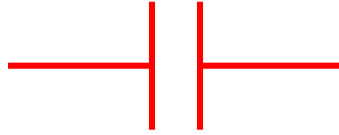

- Operational Amplifier circuits

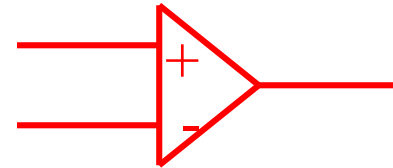

Voltage, Current, Resistor





How to measure voltage ?

(+) red

(-) black




Voltage Source

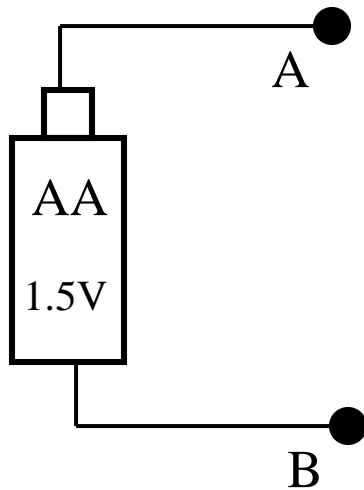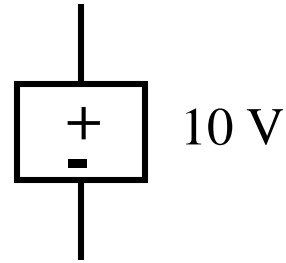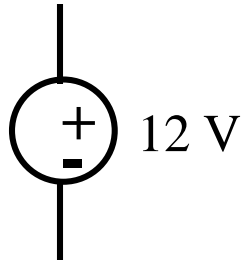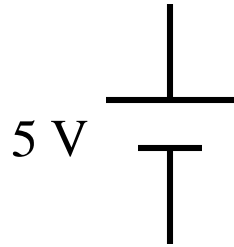


Voltage @ A = ?

Voltage @ B = ?

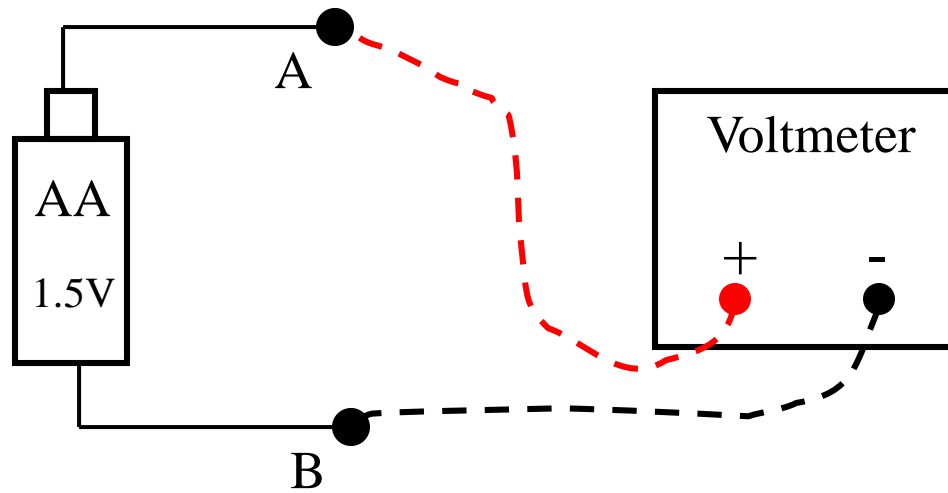


Voltmeter = ?
Reading

= 1.5 volt

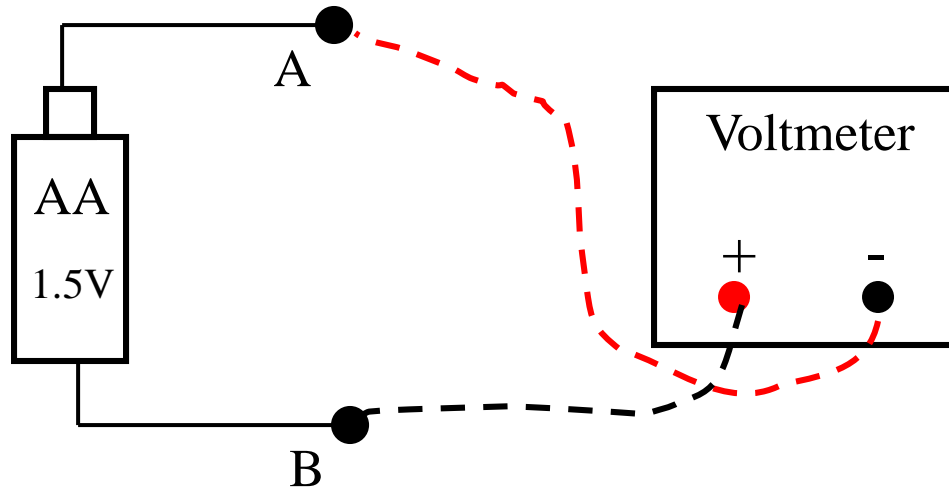

Voltmeter = ?
Reading


= - 1.5 volt

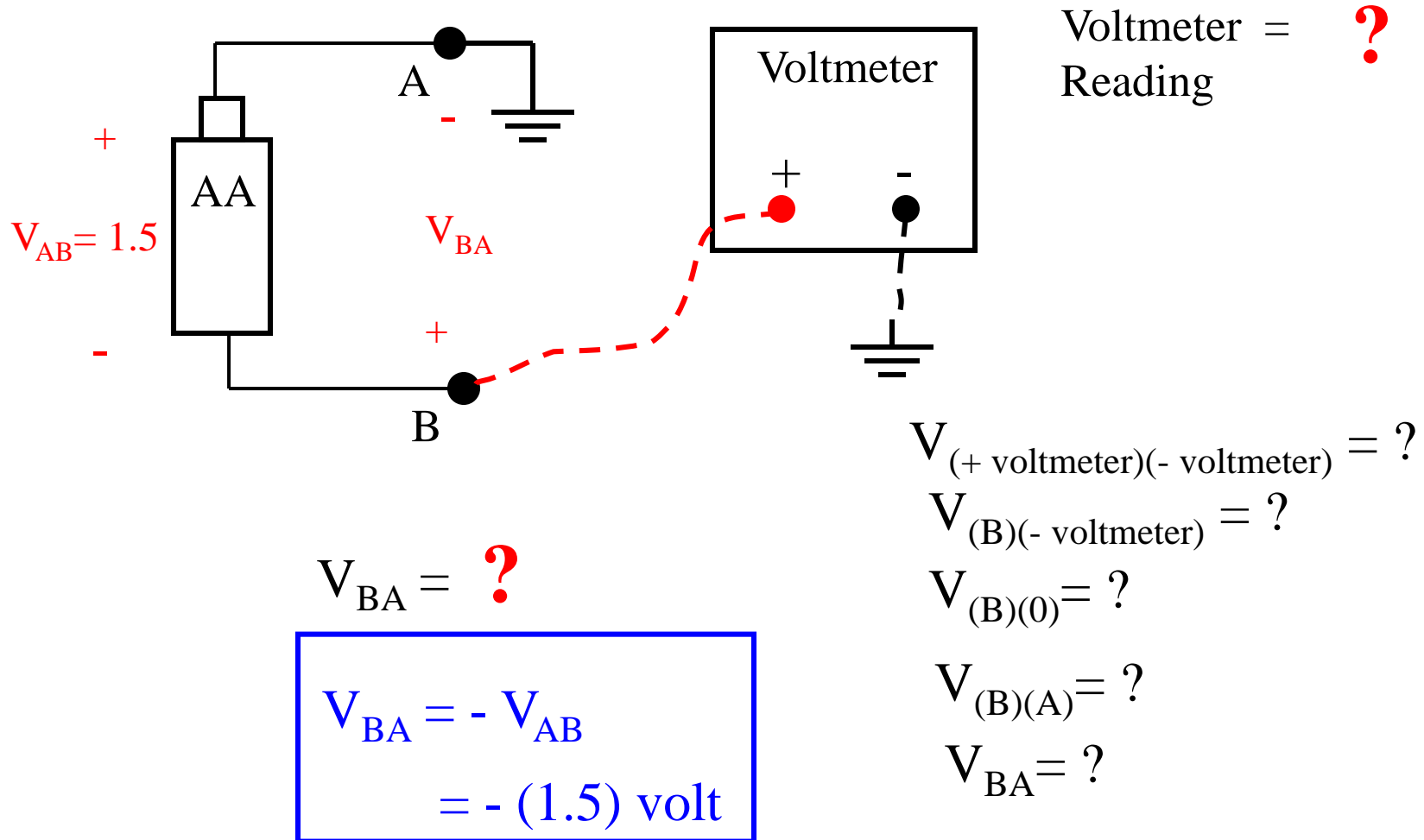

$$\begin{aligned}V_{CB} &= V_C - V_B \\ &= V_{C0} - V_{B0}\end{aligned}\quad \text{where } 0 = \text{gnd (reference pt)}$$

pick any reference point
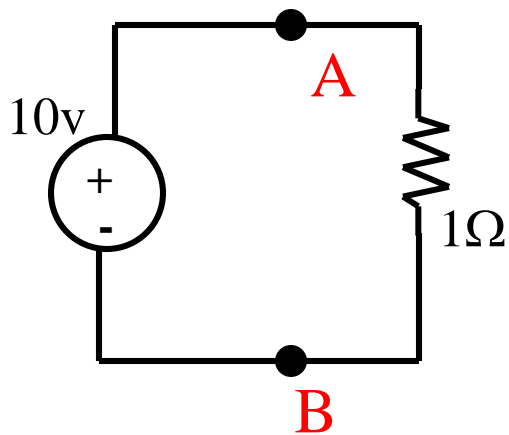
$$\begin{aligned}V_{CB} &= V_{CA} - V_{BA} \\ &= (V_C - V_A) - (V_B - V_A) \\ &= V_C - V_A - V_B + V_A \\ &= V_C - V_B\end{aligned}$$




$$V_A = ? \quad \boxed{V_{A0}}$$

$$V_B = ? \quad \boxed{V_{B0}}$$


?

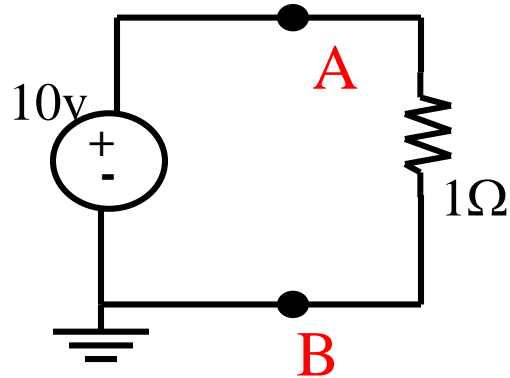Do not know the
answer, ground is
not connected




$$V_A = ? \quad \boxed{V_A = 10 \text{ volt}}$$
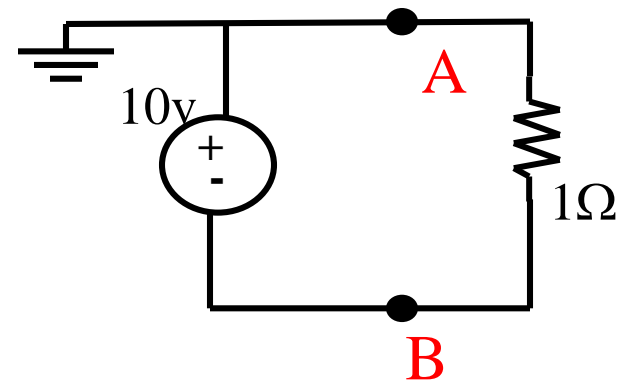
$$V_B = ? \quad \boxed{V_B = 0 \text{ volt}}$$



$$V_A = ? \quad \boxed{V_A = 0 \text{ volt}}$$
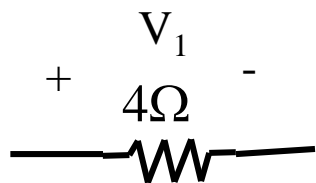
$$V_B = ? \quad \boxed{V_B = -10 \text{ volt}}$$




$$I_1 = 2\text{A}$$

$$\mathbf{V_1 = +I_1 R}$$

$$\mathbf{V_1 = +(2\text{A})(4\Omega)}$$

$$\mathbf{V_1 = 8\text{V}}$$

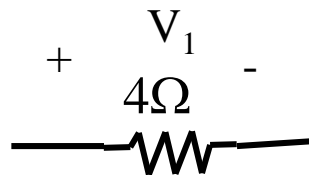


$$I_2 = -2\text{A}$$

$$\mathbf{V_1 = -I_2 R}$$

$$\mathbf{V_1 = -(-2\text{A})(4\Omega)}$$


$$\mathbf{V_1 = 8\text{V}}$$

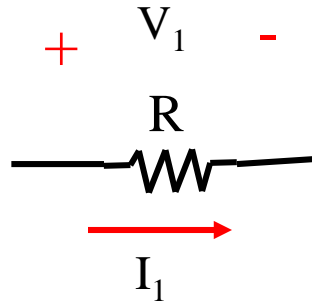

I_1 +ve or -ve ?


Can not be determined.

$$V_1 = + I_1 R$$

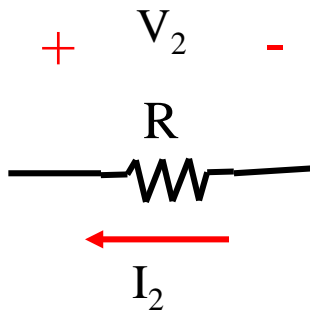

I_2 +ve or -ve ? Can not be determined.

$$V_2 = - I_2 R$$

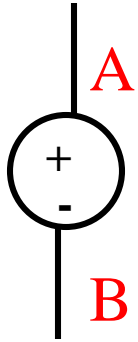

$V_A > V_B$ Yes / No ? Can not be determined.

$V_A < V_B$ Yes / No ? Can not be determined.

$V_A = V_B$ Yes / No ? Can not be determined.


$V_A = 0$ Yes / No ? Can not be determined.

$V_A > 0$ Yes / No ? Can not be determined.




$V_B = 0$ Yes / No ? Can not be determined.

$V_B > 0$ Yes / No ? Can not be determined.

Current Direction

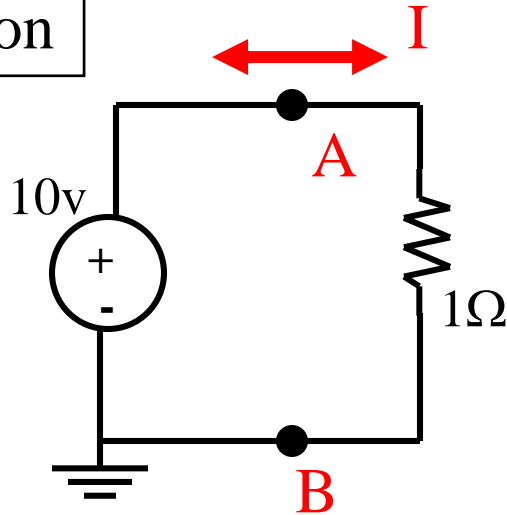


Direction of $I = ?$

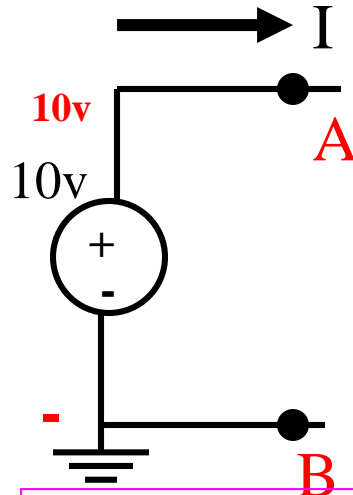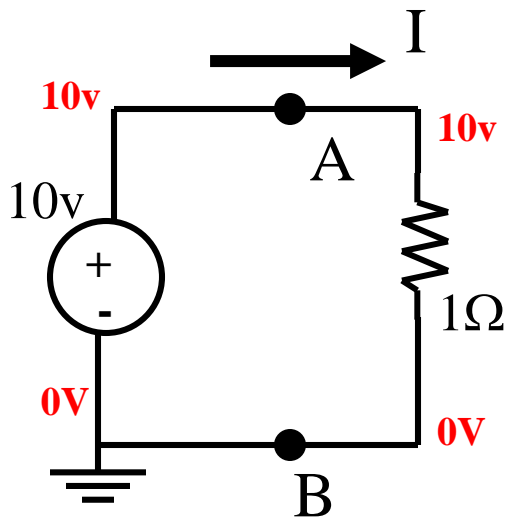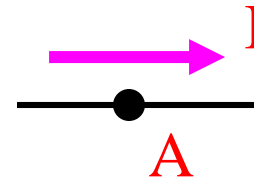



Energy Source

Deliver Energy



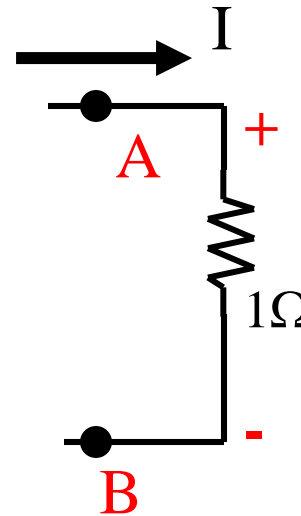



*Absorb Energy
/ Energy Dissipated*

?

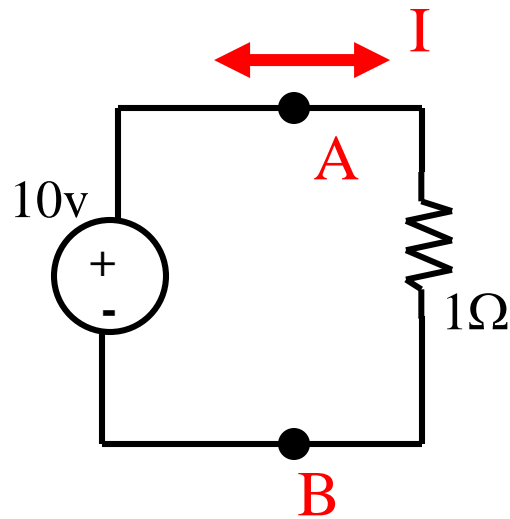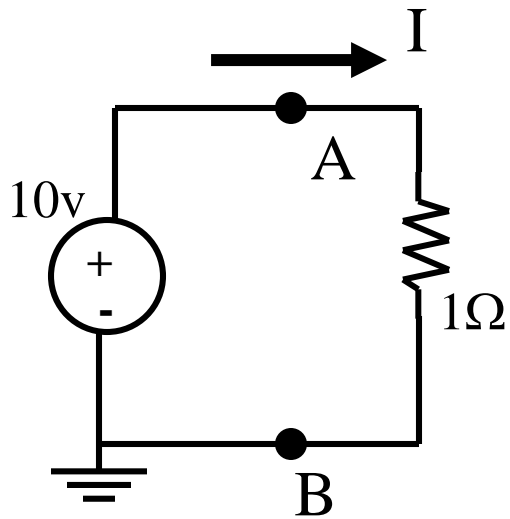

Direction of $I = ?$

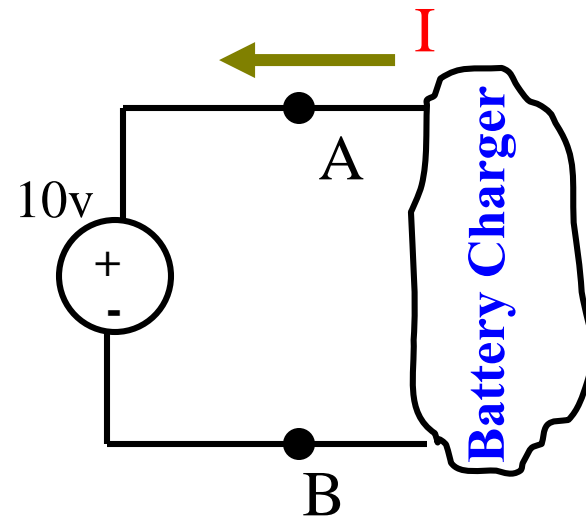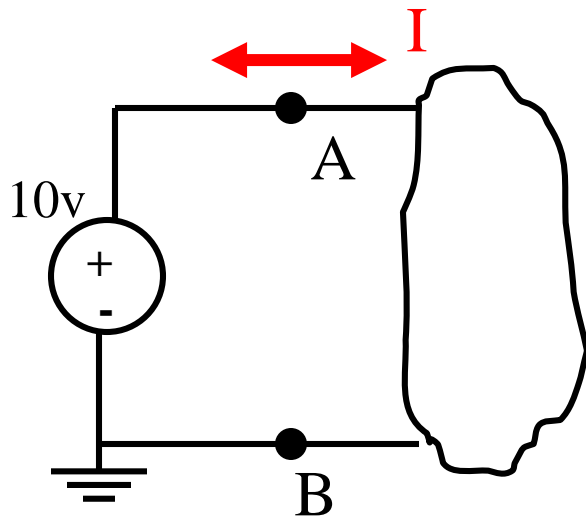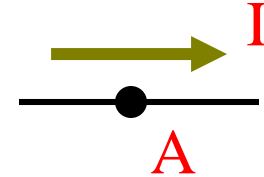


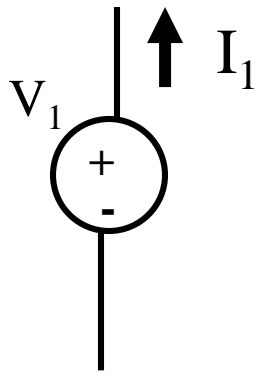

Absorbing / Delivering Power ? Can not be determined.

$$\mathbf{P_1 = -V_1 I_1}$$

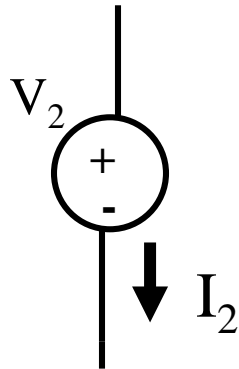
+ve \rightarrow Absorbing Power
Dissipated Power
-ve \rightarrow Delivering Power



Absorbing / Delivering Power ? Can not be determined.

$$\mathbf{P_2 = +V_2 I_2}$$

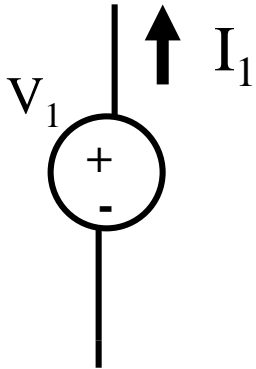+ve \rightarrow Absorbing Power
Dissipated Power
-ve \rightarrow Delivering Power



$$\mathbf{P}_1 = -\mathbf{V}_1 \mathbf{I}_1$$

Information

$$V_1 = 4 \text{ V}$$

$$I_1 = -2 \text{ A}$$

$$P_1 = -(4)(-2)$$

$$P_1 = +8 \text{ W} \quad \text{Absorbing Power}$$