
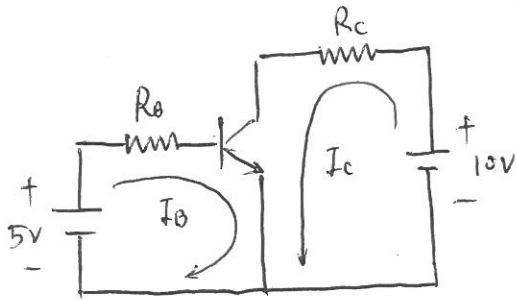


L9. Circuit Analysis

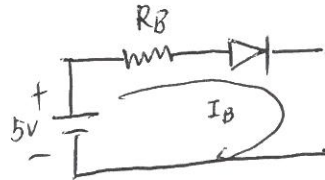We have done some circuit analysis, such as calculating I_B in the transistor circuit.



To do that, we look at the left loop:



and get $I_B = \frac{5 - 0.7}{R_B}$


- ① KVL (Component I-V)
- ② Circuit law

What is the physics background for this?

Are there any systematic ways for circuit analysis?

1. Terms for circuit analysis:

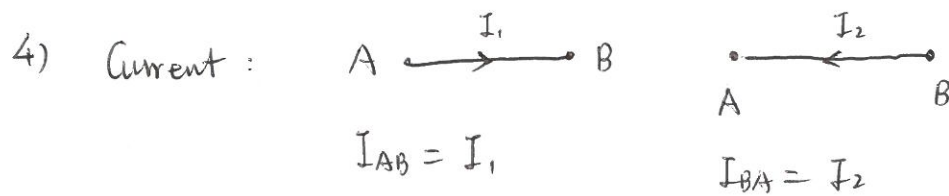- 1) Node: an electrical point connecting terminals of two or more circuit elements.
- 2) Branch: circuit element between two nodes.
- 3) Loop: any circuit branch that ends at its starting node, without passing an intermediate node more than once.




- ① Label direction
- ② Actual direction

$$I_{AB} = -I_{BA}$$

The actual current direction is labeled as the direction on which positive charges flow. So, $I_{AB} = I_A$ represent $I_{AB} = -I_A$ currents on different directions.


5) Voltage drop:

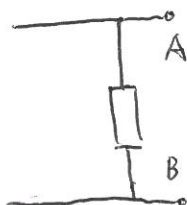

$$V_{AB} = V_A - V_B, \quad V_{BA} = -V_{AB}$$


$$V_A = V_A - \text{GND.}$$

6) Example: loops/nodes

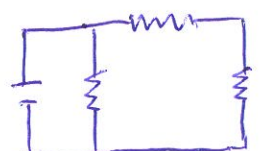

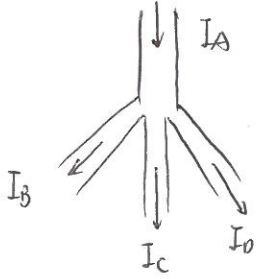2. Kirchhoff's current law (KCL)

Physics basis: Conservation of charges (charges can't be created or destroyed).



KCL: The algebraic sum of all branch currents entering and leaving a node is zero at all instants of time.

Three forms:

$$\begin{cases} \textcircled{1} \text{ Entering: } I_A - I_B - I_C - I_D = 0 \\ \textcircled{2} \text{ Leaving: } -I_A + I_B + I_C + I_D = 0 \\ \textcircled{3} \text{ Entering = Leaving: } I_A = I_B + I_C + I_D \end{cases}$$

① Capacitor $\frac{dq}{dt}$

3. Kirchhoff's voltage law (KVL)


(Gravitational field?)

Physics Basis: Conservation of energy \Rightarrow Consider moving a charge around a loop.

KVL: The algebraic sum of all branch voltages around any loop is zero at all instants of time.

② Phone example

Example:

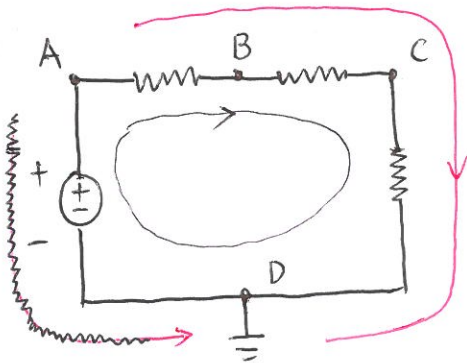

$$E_{AB} + E_{BC} + E_{CD} + E_{DA} = 0$$

$$Q(V_{AB} + V_{BC} + V_{CD} + V_{DA}) = 0 \quad Q \neq 0$$

$$\Rightarrow V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$


Two forms:

$$\begin{cases} V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0 \\ V_{AB} + V_{BC} + V_{CD} = -V_{DA} = V_{AD} \end{cases}$$

The algebraic sums of all branch voltages on any path between two nodes are equal.

4.

KVL Example :

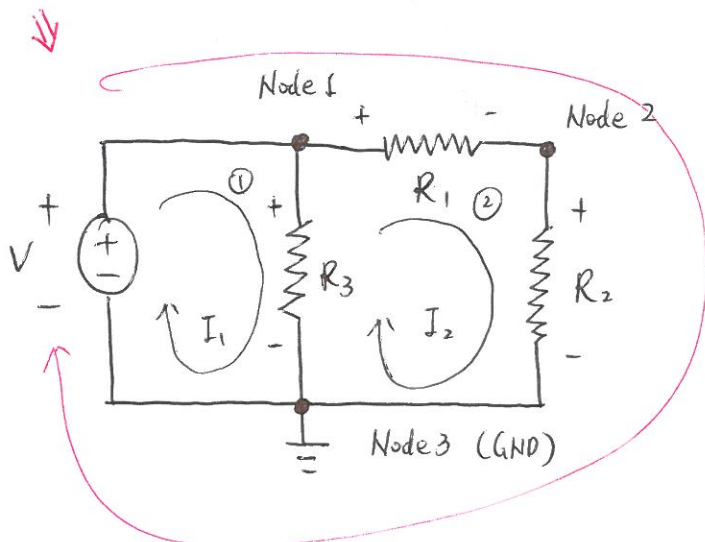

Given $V = 5V$, $R_1 = 50\Omega$, $R_2 = 75\Omega$, $R_3 = 25\Omega$,

Solve I_1, I_2 .

General procedure :

Step 1 : Define / Label loops. L_1 & L_2

Step 2 : Set up KVL equation for all loops.

$$V_{13} + V_{31} = 0$$

L_1 : $V_{13} - V = 0$ [Use the Loop current direction (arrow) to determine the "+" "-" sign before the voltage .

For example, \curvearrowright hits R_3 at the "+" terminal .

Then, "+" V_{13} . \curvearrowright hits the voltage source at the "-" terminal , So, "-" V .

~~X~~

$$L_2 : V_{12} + V_{23} - V_{13} = 0 \quad [V_{12} + V_{23} + V_{31} = 0]$$

Step 3 : Write voltages in terms of loop currents (I_1, I_2) . Ω 's law

$$\begin{cases} V_{13} - V = 0 \\ V_{12} + V_{23} - V_{13} = 0 \end{cases}$$

\Downarrow

$$\begin{cases} I_{13} \cdot R_3 - V = 0 \\ I_1 \cdot R_1 + I_2 \cdot R_2 - I_{13} \cdot R_3 = 0 \end{cases}$$

What is I_{13} ?

I_{13} is the "total" ^{actual} current entering R_3 from node 1. \Rightarrow So, $I_{13} = I_1 - I_2$

\Downarrow

$$\begin{cases} (I_1 - I_2) R_3 - V = 0 \\ I_1 R_1 + I_2 R_2 - (I_1 - I_2) R_3 = 0 \end{cases}$$

two equations & two unknowns.

\Downarrow

$$\begin{cases} R_3 I_1 - R_3 I_2 = V \\ -R_3 I_1 + (R_1 + R_2 + R_3) I_2 = 0 \end{cases}$$

Consider $V = 5V$

$R_1 = 50\Omega$

$R_2 = 75\Omega$

$R_3 = 25\Omega$

\Downarrow

step 4: Solve the equations.

$$\begin{cases} 25 I_1 - 25 I_2 = 5 & \textcircled{1} \\ -25 I_1 + (50 + 75 + 25) I_2 = 0 & \textcircled{2} \end{cases}$$


$$\textcircled{1} + \textcircled{2} \Rightarrow 125 I_2 = 5 \Rightarrow I_2 = 0.04 A$$

$\Downarrow \textcircled{1}$

$$\text{From } \textcircled{1}, 25 I_1 = 5 + 25 \times 0.04 = 6 \Rightarrow I_1 = 0.24 A.$$

Then, we can determine V_1, V_2, \dots

5. KCL Example : [Nodal Analysis]

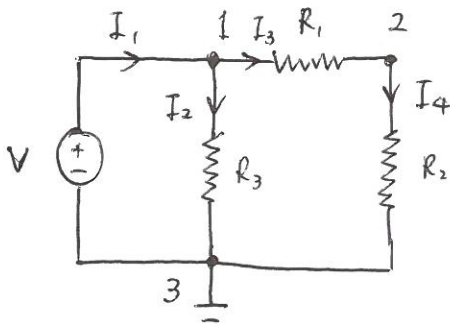

$$V = 5V$$

$$R_1 = 50\Omega$$

$$R_2 = 75\Omega$$

$$R_3 = 25\Omega$$

Determine all voltages & currents in the circuit.

Step 1 : For a circuit with "n" nodes ($n=3$, here), make one node as the GND (3, here) and apply KCL to the other "n-1" nodes.

Step 2 : Set up KCL equations for nodes 1 & 2. [We need to label some currents]

$$N_1 : I_1 = I_3 + I_2$$

$$N_2 : I_3 = I_4$$

Step 3 : Express branch currents in terms of node voltages (V_1, V_2) "Ohm's law"

$$N_1 : I_1 = \frac{V_1 - V_2}{R_1} + \frac{V_1}{R_3} \quad [\text{Note that we can't do this for } I_1.]$$

$$N_2 : \frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} \quad [\text{Three unknowns?}]$$

Step 4 : Express the node voltages in terms of known voltage ($V_1 = V$)

$$N_1 : I_1 = \frac{V - V_2}{R_1} + \frac{V}{R_3}$$

$$N_2 : \frac{V - V_2}{R_1} = \frac{V_2}{R_2}$$

two equations & two variables (I_1, V_2) \Rightarrow solve them.

Numerical Results :

$$\left\{ \begin{array}{l} I_1 = \frac{V-V_2}{R_1} + \frac{V}{R_3} \end{array} \right. \quad (1)$$

$$\left\{ \begin{array}{l} \frac{V-V_2}{R_1} = \frac{V_2}{R_2} \end{array} \right. \quad (2)$$

$$(2) \quad \frac{V}{R_1} = \frac{V_2}{R_1} + \frac{V_2}{R_2} \Rightarrow \frac{V}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_2 \Rightarrow \frac{V}{R_1} = \frac{R_1+R_2}{R_1 R_2} V_2$$

$$\Rightarrow V_2 = \frac{R_2}{R_1+R_2} V = \frac{75}{50+75} \times 5 = 3V$$

$$(1) \quad I_1 = \frac{5-3}{50} + \frac{5}{25} = \frac{12}{50} = \frac{6}{25} A$$


Then, we can determine other values

6. GND : *

For the above analysis, we use node 3 as GND.

We get I_1 I_2 I_3

$$V_1 = 5V, V_2 = 3V, V_3 = 0$$

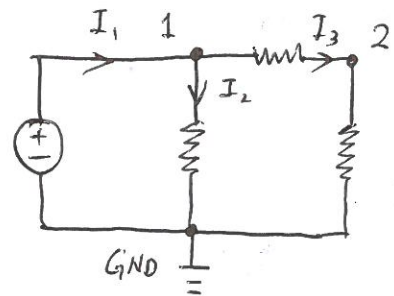

Now, what happens if we change the GND, say let $V_2 = 0$.


Will this change I_1 I_2 I_3 ? No

Will this change V_1 V_2 V_3 ? Yes, $\Rightarrow V_1 = 2V, V_2 = 0, V_3 = -3V$

But, $V_1 - V_2$, $V_1 - V_3$ & $V_2 - V_3$ don't change.

So, GND is just a reference.

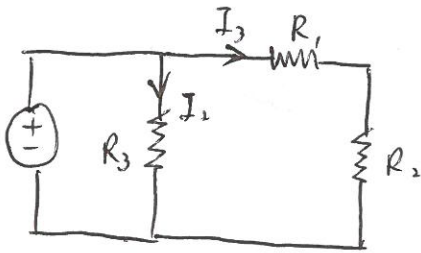Some students have found that, in fact, we don't need KCL & KVL for analysing the above circuit.




In fact, $I_1 = \frac{V}{R_3}$

$I_3 = \frac{V}{R_1 + R_2}$

But, the typical circuit we meet in practice is not that simple.

7. A complex example:

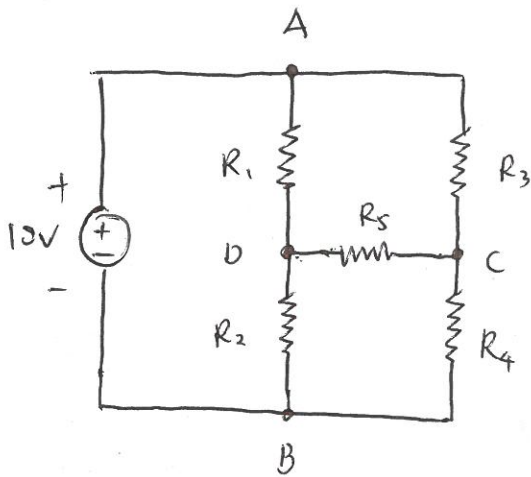


There are 4 nodes & 6 branches (containing one circuit component.)

Can we find a simple method to solve the circuit?

No.

No worries! We call KCL & KVL the "systematic" circuit analysis methods, because they can be utilized for solving "any" circuit.

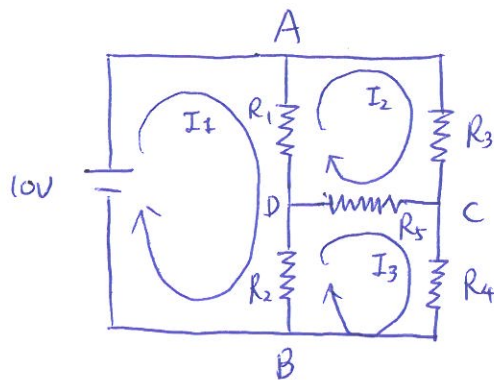Step 1: Label Loops to include all branches.



Note that there are other ways to label loops. (Compare to your lecture notes.)

Step 2: Write down the loop equations (KVL)

$$\left\{ \begin{array}{l} L1: V_{AD} + V_{DB} + V_{BA} = 0 \\ L2: V_{AC} + V_{CD} + V_{DA} = 0 \\ L3: V_{DC} + V_{CB} + V_{BD} = 0 \end{array} \right. \quad \text{Here, } V_{BA} = -10V$$

Step 3: Express voltages in terms of Loop Current.

V_{AD} is the voltage drop over R_1 . By Ohm's law, it should be $I_{AD} \times R_1$.

Here, I_{AD} is the effective current going through R_1 , with $I_{AD} = I_1 - I_2$.

Similarly, $I_{DB} = I_1 - I_3$. Thus, we have

$$L1: \underbrace{(I_1 - I_2)R_1}_{V_{AD}} + \underbrace{(I_1 - I_3)R_2}_{V_{DB}} - \underbrace{10}_{V_{BA}} = 0$$

$$L2: \underbrace{I_2 R_3}_{V_{AC}} + \underbrace{(I_2 - I_3)R_5}_{V_{CD}} + \underbrace{(I_2 - I_1)R_1}_{V_{DA} = -V_{AD}} = 0$$

$$L3: \underbrace{(I_3 - I_2)R_5}_{V_{DC}} + \underbrace{I_3 R_4}_{V_{CB}} + \underbrace{(I_3 - I_1)R_2}_{V_{BD}} = 0$$

→ Note that here we didn't label the positive & negative terminals, but just use the fact $V_{DA} = I_{DA} \cdot R_1$.
 $\downarrow \quad \downarrow$
 $D \Rightarrow A \quad D \Rightarrow A$

Step 4 : Reorganize the three equations with respect to I_1, I_2, I_3

$$\begin{cases} (R_1 + R_2)I_1 - R_1I_2 - R_2I_3 = 10 & L_1 & \textcircled{1} \\ -R_1I_1 + (R_1 + R_2 + R_5)I_2 - R_5I_3 = 0 & L_2 & \textcircled{2} \\ -R_2I_1 - R_5I_2 + (R_2 + R_4 + R_5)I_3 = 0 & L_3 & \textcircled{3} \end{cases}$$

3 Variables & 3 equations \Rightarrow Done!

After getting I_1, I_2, I_3 , we can determine currents going through all components. For example, $I_{R_1} = I_1 - I_2$, $I_{R_2} = I_1 - I_3$

* Remarks : Look at equations $\textcircled{1}$ $\textcircled{2}$ $\textcircled{3}$. What can you observe.

$$\textcircled{1} \Rightarrow (R_1 + R_2)I_1 - R_1I_2 - R_2I_3 = 10$$

Contribution of I_1 to loop 1 voltage.


I_1 goes through two resistors.

Contribution of I_3 to loop 1 voltage

I_3 goes through R_2

(In the opposite direction, "-")

Basically, loop 1 has three components

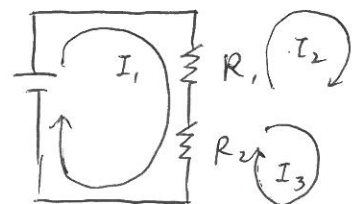


Three loop currents contribute to the

loop voltages through different components and in different ways ("+" "-")


8 Circuit Simplification

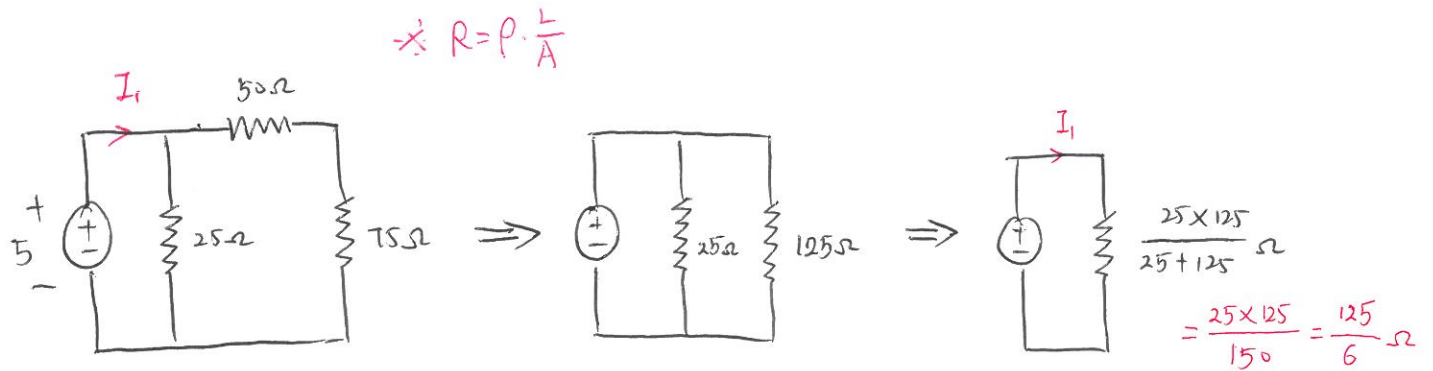For the above circuit, we can simplify the analysis without using KVL.



Some general rules:

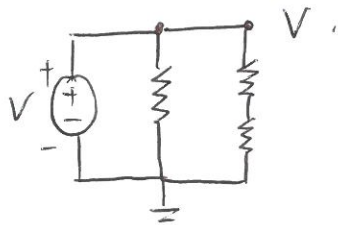* Branch voltage in parallel with a voltage source is known.



* Branch current in series with a current source is known.



* $\textcircled{1}$ KVL

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

* $\textcircled{2}$ KCL


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

This is just for fun. Read it if you are interested to see how we design a filter.

I-v for C,

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

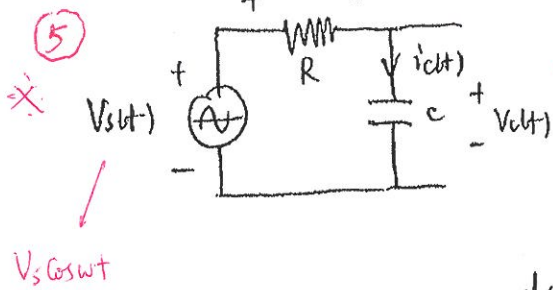

KVL: $V_s(t) = R i_C(t) + V_C(t)$

$$= RC \frac{dv_C(t)}{dt} + V_C(t)$$

$$V_s \cos(\omega t) = RC \frac{dv_C(t)}{dt} + V_C(t)$$

$$\Rightarrow \frac{dv_C(t)}{dt} + \frac{1}{RC} V_C(t) = \frac{V_s}{RC} \cos(\omega t) \quad (1) \text{ Define } RC = \tau$$

We need $V_C(t)$, whose derivative + itself is a sinusoid. \rightarrow it should be a sinusoid.

\Rightarrow Let's assume $V_C(t) = a \cos(\omega t) + b \sin(\omega t)$

$$\frac{dv_C(t)}{dt} = -a\omega \sin \omega t + b\omega \cos \omega t \quad (1) \Rightarrow -a\omega \sin \omega t + b\omega \cos \omega t + \frac{a}{\tau} \cos \omega t + \frac{b}{\tau} \sin \omega t = \frac{V_s}{\tau} \cos \omega t$$

$$\Rightarrow (b\omega + \frac{a}{\tau}) \cos \omega t + (\frac{b}{\tau} - a\omega) \sin \omega t = \frac{V_s}{\tau} \cos \omega t$$

$$\Rightarrow \left. \begin{aligned} b\omega + \frac{a}{\tau} &= \frac{V_s}{\tau} \\ \frac{b}{\tau} - a\omega &= 0 \Rightarrow b = a\omega\tau \end{aligned} \right\} \Rightarrow a\tau\omega^2 + \frac{a}{\tau} = \frac{V_s}{\tau}$$

$$\Rightarrow a = \frac{V_s}{1 + \omega^2\tau^2}$$

$$b = \frac{\omega\tau V_s}{1 + \omega^2\tau^2}$$

$$\Rightarrow V_C(t) = a \cos \omega t + b \sin \omega t$$

$$= \sqrt{a^2 + b^2} \left[\cos \omega t \frac{a}{\sqrt{a^2 + b^2}} + \sin \omega t \frac{b}{\sqrt{a^2 + b^2}} \right]$$

$$= \sqrt{a^2 + b^2} \cos(\omega t - \theta)$$


$$\theta = \tan^{-1}\left(\frac{b}{a}\right) = \tan^{-1}(\omega\tau)$$

$$= \frac{V_s}{\sqrt{1 + \omega^2\tau^2}} \cos(\omega t - \theta)$$

$$= \frac{V_s}{\sqrt{1 + R^2 C^2 \omega^2}} \cos(\omega t - \theta)$$

$$\theta = \tan^{-1}(\omega RC)$$

$\omega \uparrow$

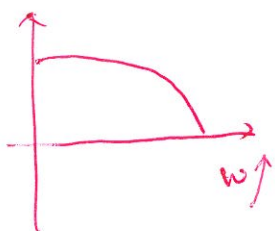

$$V_C(t) \rightarrow i_C(t) \rightarrow V_R(t)$$

Low-pass filter