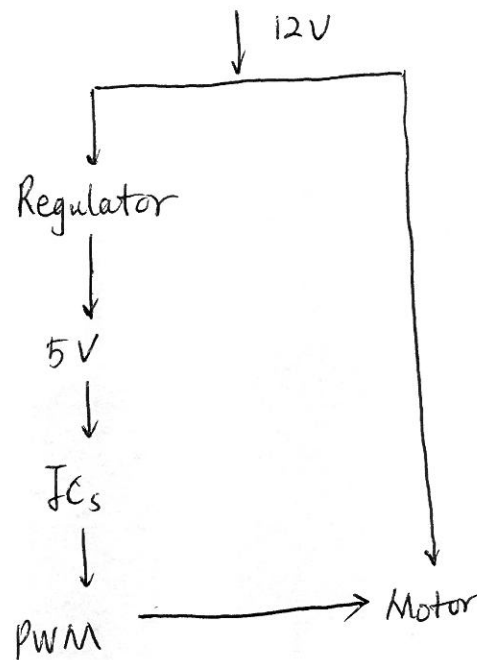



Review:



We have two problems here:

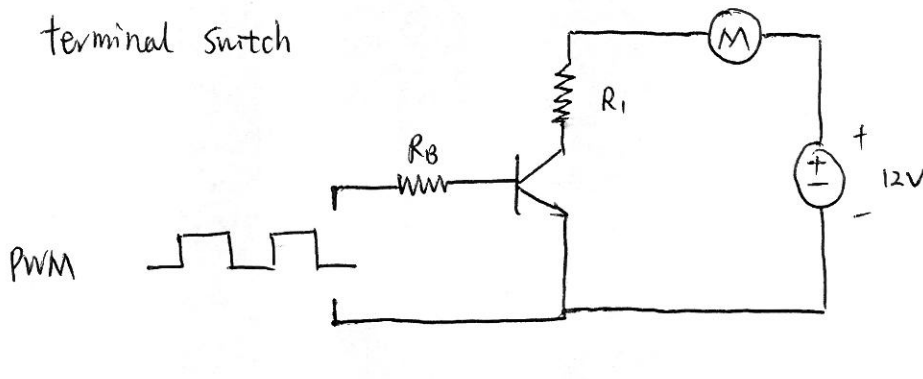- 1) Power control
- 2) Direction Control.

In last lecture, we have learned that transistor can work as a three terminal switch



Thus, we can use the weak PWM signal to control the high power source

L8: Motor Control & H-Bridge


1. History of transistors: Nobel Prizes!

2. Semi-conductor material

1) A silicon atom has four electrons in its outer shell



Silicon lattice is formed as

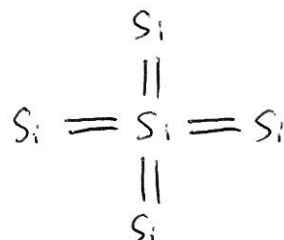


where 8 electrons form a bond.

With such a stable structure, silicon has neutral charges and the electrons are not easy to escape.

2) How about we make it not that pure by adding other atoms.

Consider the atom $\begin{array}{c} | \\ -N- \\ | \end{array}$ which has 5 electrons in the outer shell.


Then, we have another structure

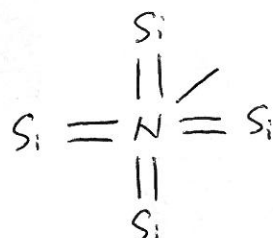

Here the additional electron is easier

to escape. We call it the N-type semiconductor because it has free "Negative" charges.

3) Similarly, we can add $\begin{array}{c} | \\ -P- \\ | \end{array}$ to $\begin{array}{c} | \\ -Si- \\ | \end{array}$ to obtain the structure

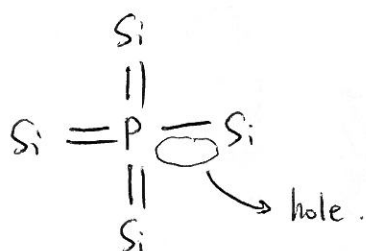



Obviously, we have one electron missing in constructing the bond. Here, "hole" can be regarded as a

"Positive" charge and we call this structure the P-type semiconductor.

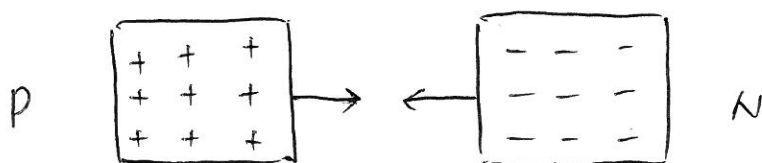
4). P-N Junction :

What if we put P-type and N-type together.



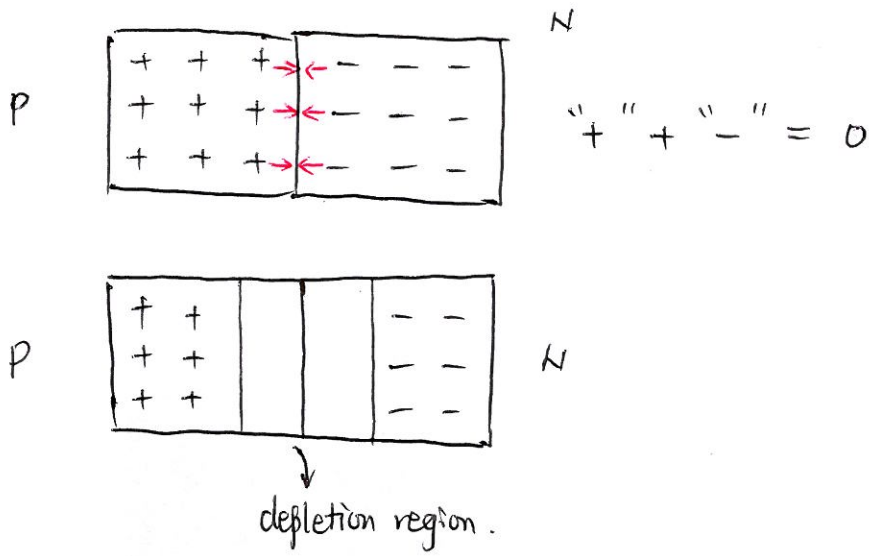

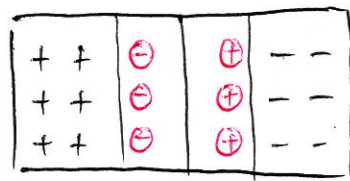Before meeting each other, P & N type materials are charge-neutral. After the above process, we have additional positive charges in the "N" region and negative charges in the "P" region.




$\oplus \ominus$: extra charges

$+ -$: free charges.


The extra charges will create an electrical field $\ominus \leftarrow \oplus$ which prevents the free charges to further flow.

5) Now, we have a diode.

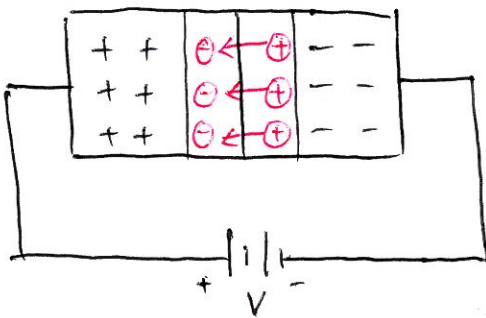


We need V to be greater than the electrical potential difference created by the extra charges ($V > 0.7V$) to turn the diode on.

Then, how about zener diode ?

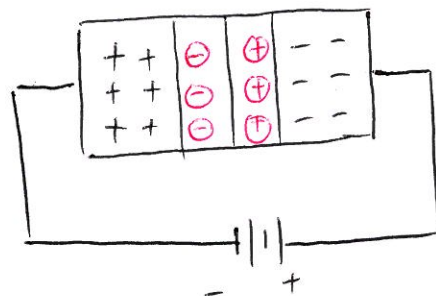


6) Transistor :

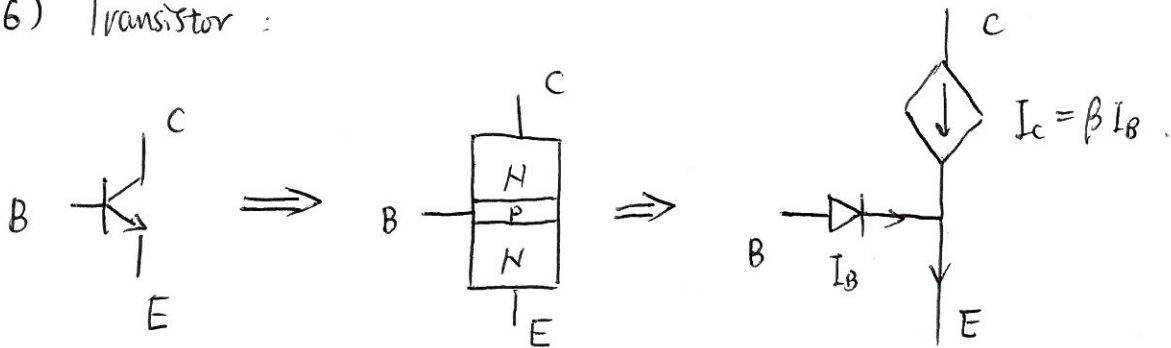

How does it work ?

layer P is very thin.

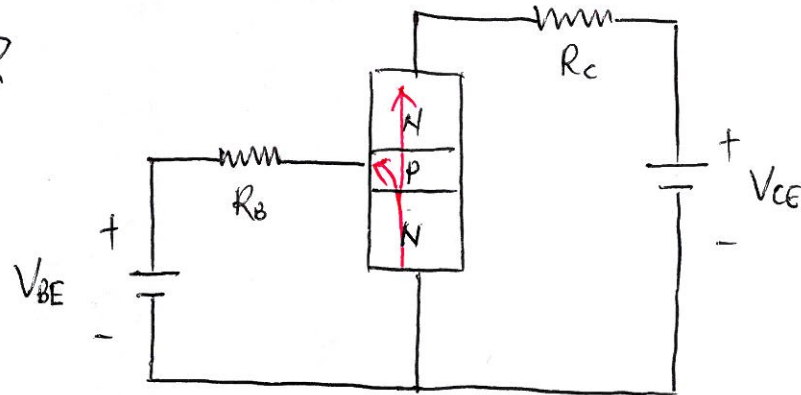


3. Voltage Control or Current control

We can use V_{BE} to control I_C
$$I_C = \beta \frac{V_{BE} - 0.7}{R_B}$$

But, I_C is linearly related to I_B , so normally we use current control


$$I_C = \beta I_B.$$

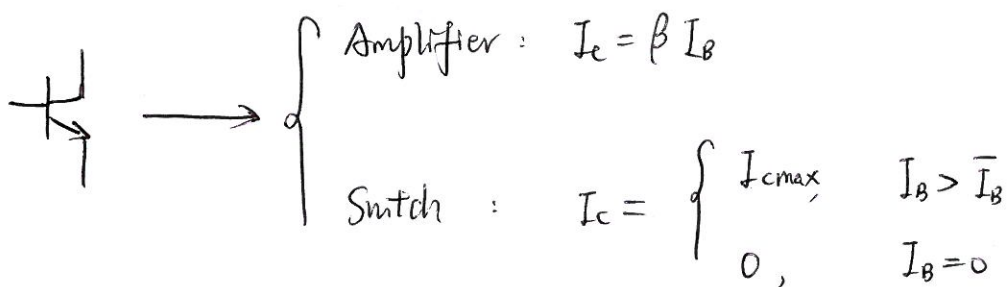4. A transistor can be used either as a switch or an amplifier.



Look at two cases.

1) Amplifier

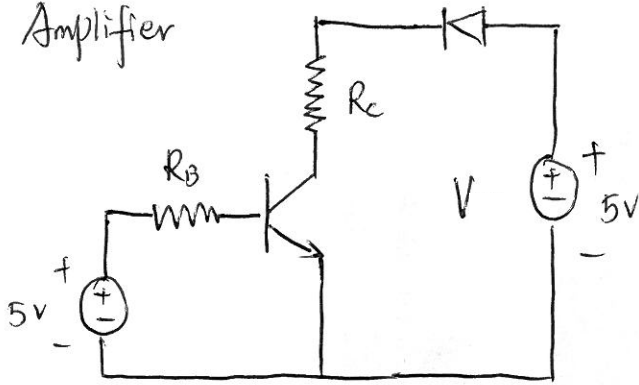


$$R_B = 1.08 \text{ M}\Omega$$

$$R_C = 170 \Omega$$

$$\beta = 100$$


Find I_B :

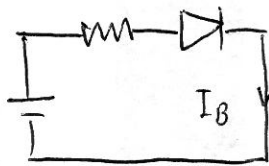

$$I_B = \frac{5 - 0.7}{1.08 \times 10^6} \approx 4 \mu\text{A}$$

$$I_C = \beta \cdot I_B = 100 \times 4 \times 10^{-6} = 0.4 \text{ mA}$$

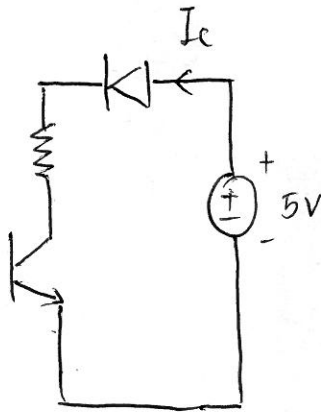Can we get $I_C = 0.4 \text{ mA}$ from V ?



What is the largest I_C ?

$$I_{C\text{max}} = \frac{5 - V_{CE} - 0.7}{170} < \frac{5 - 0.7}{170} = 25 \text{ mA}$$


$$0.4 < 25, \text{ so OK!}$$

2) Change $R_B = 10 \text{ k}\Omega$.


$$I_B = \frac{5 - 0.7}{10 \times 10^3} = 0.43 \text{ mA}$$

$$I_C = \beta \cdot I_B = 0.43 \times 100 = 43 \text{ mA} > 25 \text{ mA}$$

Not able to get it!

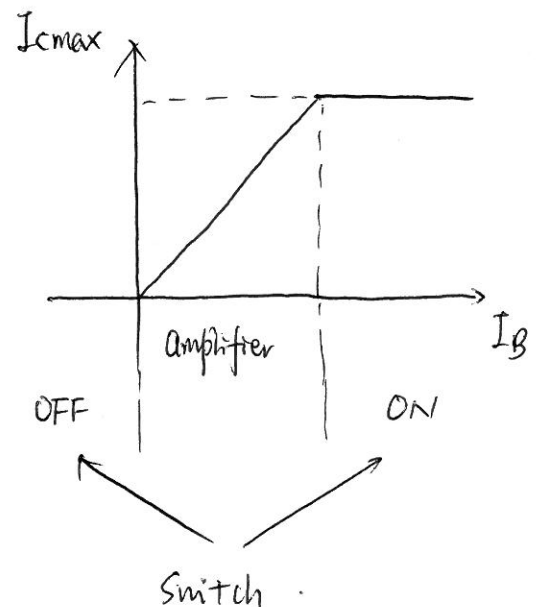

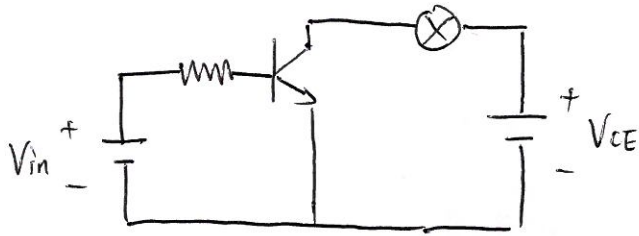
How to make the transistor work as an amplifier/switch ?



5. How to control the direction of the motor ?

Change the current going through the motor .

H-Bridge

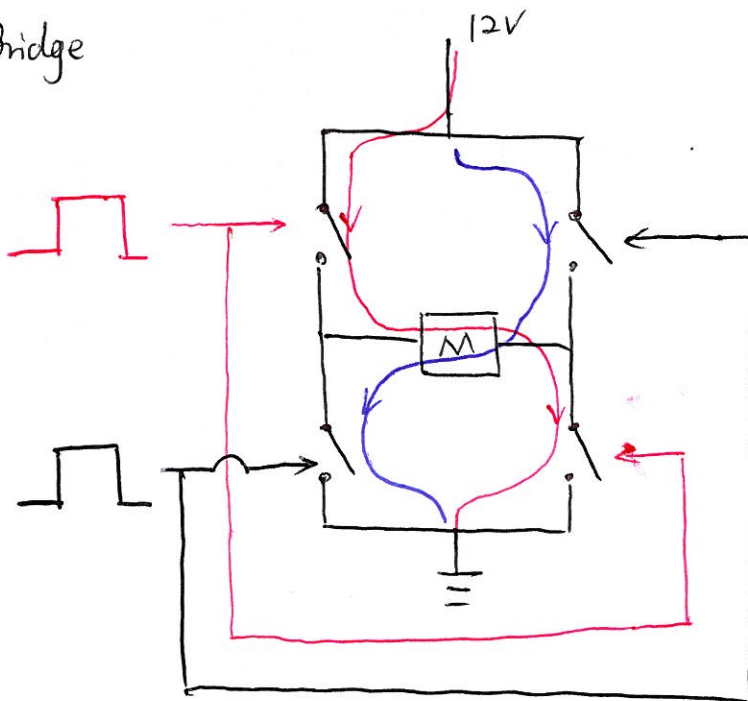

Those switches are transistors .

Challenge : How does micro-phone work ?